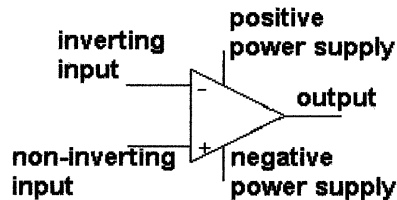


Problems

P 5.1 [a] The five terminals of the op amp are identified as follows:



- [b] The input resistance of an ideal op amp is infinite, which constrains the value of the input currents to 0. Thus, $i_n = 0$ A.
- [c] The open-loop voltage gain of an ideal op amp is infinite, which constrains the difference between the voltage at the two input terminals to 0. Thus, $(v_p - v_n) = 0$.
- [d] Write a node voltage equation at v_n :

$$\frac{v_n - 1}{2000} + \frac{v_n - v_o}{8000} = 0$$

But $v_p = 0$ and $v_n = v_p = 0$. Thus,

$$\frac{-1}{2000} - \frac{v_o}{8000} = 0 \quad \text{so} \quad v_o = -4 \text{ V}$$

P 5.2 $\frac{v_b - v_a}{20} + \frac{v_b - v_o}{160} = 0$, therefore $v_o = 9v_b - 8v_a$

- [a] $v_a = 1.5$ V, $v_b = 0$ V, $v_o = -12$ V
- [b] $v_a = 3.0$ V, $v_b = 0$ V, $v_o = -18$ V (sat)
- [c] $v_a = 1.0$ V, $v_b = 2$ V, $v_o = 10$ V
- [d] $v_a = 4.0$ V, $v_b = 2$ V, $v_o = -14$ V
- [e] $v_a = 6.0$ V, $v_b = 8$ V, $v_o = 18$ V (sat)
- [f] If $v_b = 4.5$ V, $v_o = 40.5 - 8v_a = \pm 18$


$$\therefore 2.8125 \leq v_a \leq 7.3125 \text{ V}$$

P 5.3 $v_o = (1)(9) = 9$ V; $i_{15k\Omega} = \frac{9}{15} = 0.6$ mA;

$$i_{6k\Omega} = \frac{9}{6} = 1.5 \text{ mA}; \quad i_{9k\Omega} = \frac{9}{9} = 1 \text{ mA}$$

$$\therefore i_o = -0.6 - 1.5 - 1 = -3.1 \text{ mA}$$

[d]

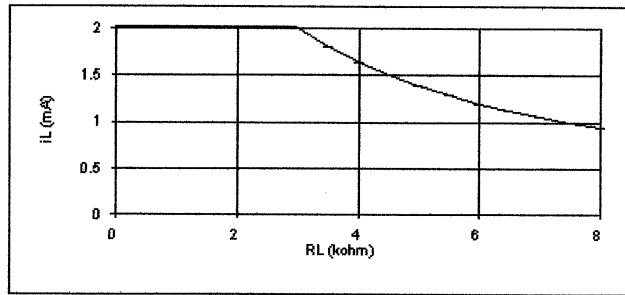

P 5.36 [a] Let v_{o1} = output voltage of the amplifier on the left. Let v_{o2} = output voltage of the amplifier on the right. Then

$$v_{o1} = \frac{-90}{15}(-0.5) = 3 \text{ V}; \quad v_{o2} = \frac{-120}{30}(0.4) = -1.6 \text{ V}$$

$$i_a = \frac{v_{o2} - v_{o1}}{1000} = -4.6 \text{ mA}$$

[b] $i_a = 0$ when $v_{o1} = v_{o2}$ so from (a) $v_{o2} = 3 \text{ V}$

Thus

$$\frac{-120}{30}(v_L) = 3$$

$$v_L = -\frac{90}{120} = -750 \text{ mV}$$

P 5.37 [a] $p_{16\text{k}\Omega} = \frac{(320 \times 10^{-3})^2}{(16 \times 10^3)} = 6.4 \mu\text{W}$

[b] $v_{16\text{k}\Omega} = \left(\frac{16}{64}\right)(320) = 80 \text{ mV}$

$$p_{16\text{k}\Omega} = \frac{(80 \times 10^{-3})^2}{(16 \times 10^3)} = 0.4 \mu\text{W}$$

[c] $\frac{p_a}{p_b} = \frac{6.4}{0.4} = 16$

[d] Yes, the operational amplifier serves several useful purposes:

- First, it enables the source to control 16 times as much power delivered to the load resistor. When a small amount of power controls a larger amount of power, we refer to it as *power amplification*.
- Second, it allows the full source voltage to appear across the load resistor, no matter what the source resistance. This is the *voltage follower* function of the operational amplifier.
- Third, it allows the load resistor voltage (and thus its current) to be set without drawing any current from the input voltage source. This is the *current amplification* function of the circuit.

P 6.4 [a] $v = L \frac{di}{dt}$

$$\frac{di}{dt} = 20[e^{-5t} - 5te^{-5t}] = 20e^{-5t}(1 - 5t)$$

$$v = (100 \times 10^{-6})(20)e^{-5t}(1 - 5t)$$

$$= 2e^{-5t}(1 - 5t) \text{ mV}, \quad t > 0$$

[b] $p = vi = 0.04te^{-10t}(1 - 5t)$

$$p(100 \text{ ms}) = 0.04(0.1)e^{-1}(1 - 0.5) = 735.76 \mu\text{W}$$

[c] absorbing

[d] $i(100 \text{ ms}) = 20(0.1)e^{-0.5} = 2e^{-0.5}$

$$w = \frac{1}{2}Li^2 = \frac{1}{2}(100 \times 10^{-6})(2e^{-0.5})^2 = 73.58 \mu\text{J}$$

[e] The energy is a maximum where the current is a maximum:

$$\frac{di_L}{dt} = 0 \quad \text{when} \quad 1 - 5t = 0 \quad \text{or} \quad t = 0.2 \text{ s}$$

$$i_{\max} = 20(0.2)e^{-1} = 4e^{-1} \text{ A}$$

$$w_{\max} = \frac{1}{2}(100 \times 10^{-6})(4e^{-1})^2 = 108.27 \mu\text{J}$$

P 6.5 [a] $0 \leq t \leq 2 \text{ s} :$

$$v = -25t$$

$$i = \frac{1}{2.5} \int_0^t -25x \, dx + 0 = -10 \frac{x^2}{2} \Big|_0^t$$

$$i = -5t^2 \text{ A}$$

$$2 \text{ s} \leq t \leq 6 \text{ s} :$$

$$v = -100 + 25t$$

$$i(2) = -20 \text{ A}$$

$$\begin{aligned} \therefore i &= \frac{1}{2.5} \int_2^t (25x - 100) \, dx - 20 \\ &= 10 \int_2^t x \, dx - 40 \int_2^t dx - 20 \\ &= 5(t^2 - 4) - 40(t - 2) - 20 \\ &= 5t^2 - 40t + 40 \text{ A} \end{aligned}$$

$$6 \text{ s} \leq t \leq 10 \text{ s} :$$

$$v = 200 - 25t$$

$$i(6) = 5(36) - 240 + 40 = -20 \text{ A}$$

$$i = \frac{1}{2.5} \int_6^t (200 - 25x) dx - 20$$

$$= 80 \int_6^t dx - 10 \int_6^t x dx - 20$$

$$= 80(t - 6) - 10(t^2 - 36)/2 - 20 = 80t - 5t^2 - 320 \text{ A}$$

$$10 \text{ s} \leq t \leq 12 \text{ s} :$$

$$v = 25t - 300$$

$$i(10) = 800 - 500 - 320 = -20 \text{ A}$$

$$i = \frac{1}{2.5} \int_{10}^t (25x - 300) dx - 20 \quad t \geq 12 \text{ s} :$$

$$= 10 \int_{10}^t x dx - 120 \int_{10}^t dx - 20$$

$$= 5(t^2 - 100) - 120(t - 10) - 20$$

$$= 5t^2 - 120t + 680 \text{ A}$$

$$v = 0$$

$$i(12) = 5(12)^2 - 120(12) + 680 = -40 \text{ A}$$

$$i = \frac{1}{2.5} \int_{12}^t 0 dx - 40$$

$$= -40 \text{ A}$$

[b] For $0 \leq t \leq 2 \text{ s}$, $v = -25t \text{ V}$; $i = -5t^2 \text{ A}$

$$v = 0 \quad \text{when} \quad t = 0 \quad \text{so} \quad i = 0 \text{ A}$$

$$\text{For } 2 \leq t \leq 6 \text{ s}, \quad v = -100 + 25t \text{ V}; \quad i = 5t^2 - 40t + 40 \text{ A}$$

$$v = 0 \quad \text{when} \quad t = 4 \text{ s} \quad \text{so} \quad i = 5(4)^2 - 40(4) + 40 = -40 \text{ A}$$


$$\text{For } 6 \leq t \leq 10 \text{ s}, \quad v = 200 - 25t \text{ V}; \quad i = -5t^2 + 80t - 320 \text{ A}$$

$$v = 0 \quad \text{when} \quad t = 8 \text{ s} \quad \text{so} \quad i = -5(8)^2 + 80(8) - 320 = 0 \text{ A}$$

$$\text{For } 10 \leq t \leq 12 \text{ s}, \quad v = 25t - 300 \text{ V}; \quad i = 5t^2 - 120t + 680 \text{ A}$$

$$v = 0 \quad \text{when} \quad t = 12 \text{ s} \quad \text{so} \quad i = 5(12)^2 - 120(12) + 680 = -40 \text{ A}$$
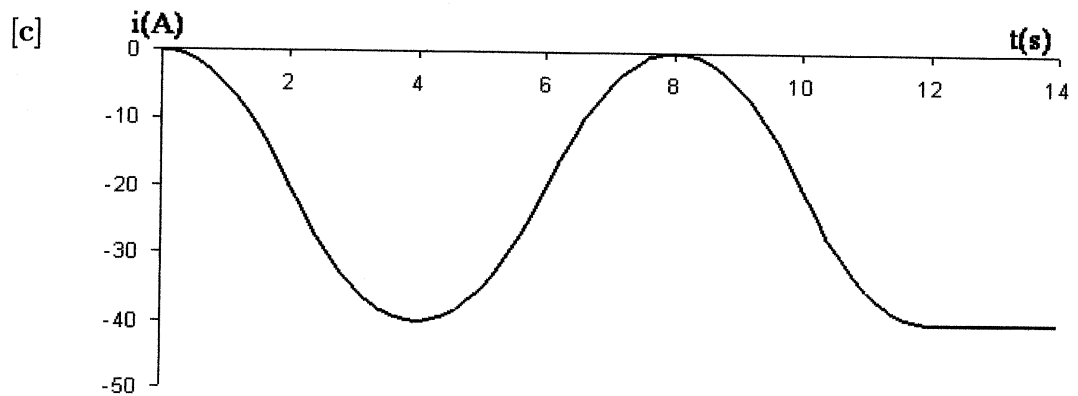
$$\text{For } t \geq 12 \text{ s}, \quad v = 0; \quad i = -40 \text{ A}$$



P 6.6 [a] $v_L = L \frac{di}{dt} = [56 \cos 140t + 92 \sin 140t]e^{-20t}$ mV

$$\therefore \frac{dv_L}{dt} = [11,760 \cos 140t - 9680 \sin 140t]e^{-20t} \text{ mV/s}$$

$$\frac{dv_L}{dt} = 0 \quad \text{when} \quad \tan 140t = \frac{11,760}{9680} = 1.21$$

$$\therefore t = 6.30 \text{ ms}$$

Also $140t = 0.8821 + \pi$ etc.

Because of the decaying exponential v_L will be maximum the first time the derivative is zero.

[b] $v_L(\text{max}) = [56 \cos 0.8821 + 92 \sin 0.8821]e^{-0.12602} = 93.997$ mV

$$v_L \text{ max} \approx 94 \text{ mV}$$

Note: When $t = \frac{0.8821 + \pi}{140}$; $v_L = -60$ mV

P 6.7 [a] $i = \frac{1000}{50} \int_0^t 250 \sin 1000x \, dx - 5$

$$= 5000 \int_0^t \sin 1000x \, dx - 5$$

$$= 5000 \left[\frac{-\cos 1000x}{1000} \right]_0^t - 5$$

$$= 5(1 - \cos 1000t) - 5$$

$$i = -5 \cos 1000t \text{ A}$$

$$\begin{aligned}
 \text{P 6.18 [a]} \quad v &= 5 \times 10^6 \int_0^{250 \times 10^{-6}} 100 \times 10^{-3} e^{-1000t} dt - 60.6 \\
 &= 500 \times 10^3 \frac{e^{-1000t}}{-1000} \Big|_0^{250 \times 10^{-6}} - 60.6 \\
 &= 500(1 - e^{-0.25}) - 60.6 = 50 \text{ V}
 \end{aligned}$$

$$w = \frac{1}{2} C v^2 = \frac{1}{2} (0.2) (10^{-6}) (50)^2 = 250 \mu\text{J}$$

$$\text{[b]} \quad v = 500 - 60.6 = 439.40 \text{ V}$$

$$w = \frac{1}{2} (0.2) \times 10^{-6} (439.40)^2 = 19.31 \text{ mJ} = 19,307.24 \mu\text{J}$$

$$\text{P 6.19 [a]} \quad w(0) = \frac{1}{2} C [v(0)]^2 = \frac{1}{2} (0.40) \times 10^{-6} (25)^2 = 125 \mu\text{J}$$

$$\text{[b]} \quad v = (A_1 t + A_2) e^{-1500t}$$

$$v(0) = A_2 = 25 \text{ V}$$

$$\frac{dv}{dt} = -1500 e^{-1500t} (A_1 t + A_2) + e^{-1500t} (A_1)$$

$$= (-1500 A_1 t - 1500 A_2 + A_1) e^{-1500t}$$

$$\frac{dv}{dt}(0) = A_1 - 1500 A_2$$

$$i = C \frac{dv}{dt}, \quad i(0) = C \frac{dv(0)}{dt}$$

$$\therefore \frac{dv(0)}{dt} = \frac{i(0)}{C} = \frac{90 \times 10^{-3}}{0.40 \times 10^{-6}} = 225 \times 10^3$$

$$\therefore 225 \times 10^3 = A_1 - 1500(25)$$

$$\text{Thus, } A_1 = 2.25 \times 10^5 + 3.75 \times 10^4 = 262,500 \frac{\text{V}}{\text{s}}$$

$$\text{[c]} \quad v = (262,500t + 25) e^{-1500t}$$

$$i = C \frac{dv}{dt} = 0.40 \times 10^{-6} \frac{d}{dt} (262,500t + 25) e^{-1500t}$$

$$i = \frac{d}{dt} [(0.105t + 10 \times 10^{-6}) e^{-1500t}]$$

$$= (0.105t + 10 \times 10^{-6}) (-1500) e^{-1500t} + e^{-1500t} (0.105)$$

$$= (-157.5t - 15 \times 10^{-3} + 0.105) e^{-1500t}$$


$$= (0.09 - 157.5t) e^{-1500t} \text{ A}, \quad t \geq 0$$

$$= (90 - 157,500t) e^{-1500t} \text{ mA}, \quad t \geq 0$$

P 6.25 $\frac{1}{21} + \frac{1}{28} = \frac{7}{84} \therefore C_{eq} = 12 \mu\text{F}$

$-10\text{V} - 5\text{V} = -15\text{V}$


$24 + 12 = 36 \mu\text{F}$

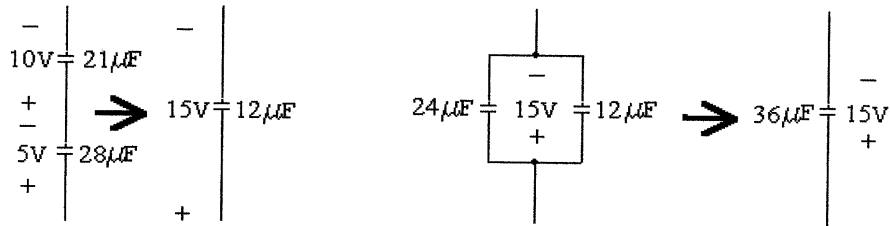

$\frac{1}{36} + \frac{1}{36} = \frac{2}{36} \therefore C_{eq} = 18 \mu\text{F}$

$-15\text{V} + 2\text{V} = -13\text{V}$


$12 + 20 = 32 \mu\text{F}$

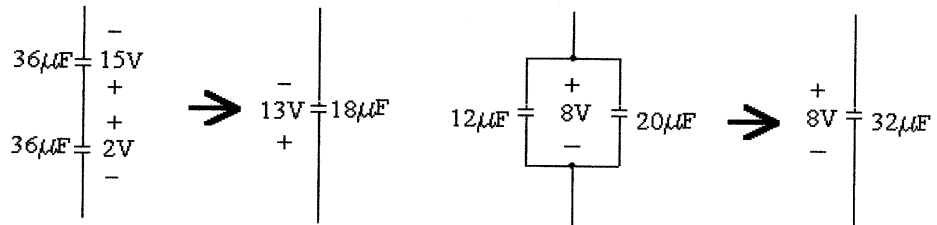

$18 + 14 = 32 \mu\text{F}$

$\frac{1}{32} + \frac{1}{32} = \frac{2}{32} \therefore C_{eq} = 16 \mu\text{F}$

$8\text{V} - 13\text{V} = -5\text{V}$

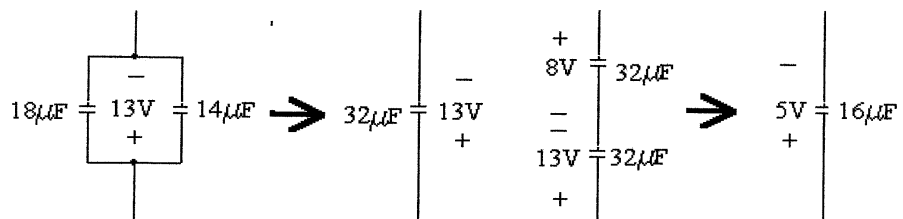

P 6.32

$$\begin{aligned}
 v_2(t) &= 20 \times 10^{-3} \frac{di_o}{dt} \\
 &= (20 \times 10^{-3})(50 \times 10^{-3}) \{e^{-8000t}[-6000 \sin 6000t + 12,000 \cos 6000t] \\
 &\quad + (-8000e^{-8000t})[\cos 6000t + 2 \sin 6000t]\} \\
 &= e^{-8000t} \{4 \cos 6000t - 22 \sin 6000t\} \text{ V}
 \end{aligned}$$

$$\therefore v_2(0) = 4 \text{ V}$$

$$i_0(0) = 50 \text{ mA}$$

$$v_R(0) = 320(50 \times 10^{-3}) = 16 \text{ V}$$

$$v_1(0) = 16 + 4 = 20 \text{ V}$$

$$\begin{aligned}
 \text{P 6.33} \quad v_c &= \frac{-10^6}{20} \int_0^t e^{-80x} \sin 60x \, dx - 300 \\
 &= 5e^{-80t} [80 \sin 60t + 60 \cos 60t] + 300 - 300 \\
 &= 400e^{-80t} \sin 60t + 300e^{-80t} \cos 60t \text{ V} \\
 v_L &= 5 \frac{di_o}{dt} \\
 &= 5[-80e^{-80t} \sin 60t + 60e^{-80t} \cos 60t] \\
 &= -400e^{-80t} \sin 60t + 300e^{-80t} \cos 60t \text{ V} \\
 v_o &= v_c - v_L \\
 &= (300e^{-80t} \cos 60t - 300e^{-80t} \cos 60t + 400e^{-80t} \sin 60t + \\
 &\quad 400e^{-80t} \sin 60t) \\
 &= 800e^{-80t} \sin 60t \text{ V}
 \end{aligned}$$

$$\text{P 6.34} \quad [\text{a}] \quad 5 \frac{di_g}{dt} + 40 \frac{di_2}{dt} + 90i_2 = 0$$

$$40 \frac{di_2}{dt} + 90i_2 = -5 \frac{di_g}{dt}$$

$$[\text{b}] \quad i_2 = e^{-t} - 5e^{-2.25t} \text{ A}$$

$$\frac{di_2}{dt} = -e^{-t} + 11.25e^{-2.25t} \text{ A/s}$$

$$i_g = 10e^{-t} - 10 \text{ A}$$