

King Fahd University of Petroleum & Minerals  
 Electrical Engineering Department  
 EE201- 07 Electric Circuits  
 Quiz # 4

Name:	I.D#
Serial Number:	

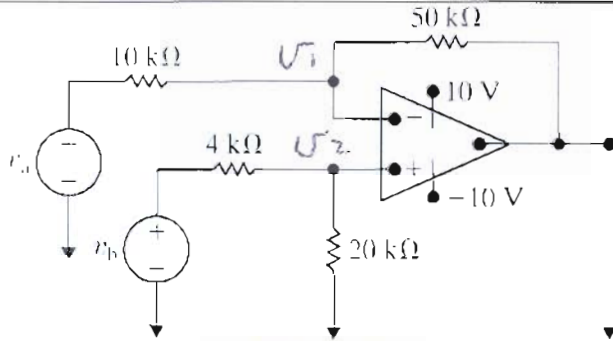


Figure 05-13-01A02-5-5  
 Copyright © 2008 Pearson Prentice Hall, Inc.

In the difference amplifier shown,  $v_b = 4.0$  V.  
 What range of values for  $v_a$  will result in linear operation?

$$v_2 = \left( \frac{20}{4 + 20} \right) 4 = \frac{10}{3} \text{ V}$$

$$v_1 = v_2 = \frac{10}{3} \text{ V}$$

Nodal Voltage Eq.

$$\frac{v_1 - v_a}{10} + \frac{v_1 - v_o}{50} = 0$$

$$v_a = \frac{20 - v_o}{5}$$

$$v_{a1} = \frac{20 + 10}{5} = 6 \text{ V}$$

$$v_{a2} = \frac{20 - 10}{5} = 2 \text{ V}$$

$$\boxed{2 \leq v_a \leq 6}$$