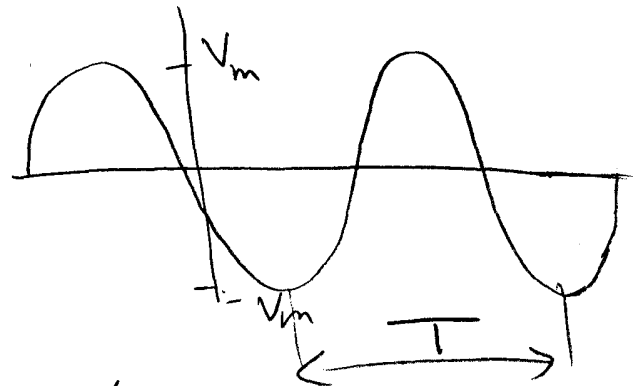


Background.

- The Sinusoidal Source

- sinusoidal voltage source
- sinusoidal current source.



$$v(t) = V_m \cos(\omega t + \phi)$$

Amplitude

frequency

Phase angle

$$\omega = 2\pi f = \frac{2\pi}{T}$$

"The value of $v(0) = V_m \cos(\phi)$ "

$T \equiv$ Period (seconds)

$$f = \frac{1}{T} \text{ (Hz)}$$

- RMS \equiv Root Mean Square

$$V_{rms} = \frac{V_m}{\sqrt{2}} \leftarrow \text{Amplitude}$$

- The phasor

- Euler's identity

$$e^{\pm j\theta} = \cos\theta \pm j\sin\theta \Rightarrow$$

$$\begin{aligned} \cos\theta &= \text{R}\{e^{j\theta}\} \\ \sin\theta &= \text{I}\{e^{j\theta}\} \end{aligned}$$

- For a sinusoidal voltage

$$v(t) = V_m \cos(\omega t + \phi)$$

$$= V_m \text{R}\{e^{j(\omega t + \phi)}\}$$

$$= V_m \text{R}\{e^{j\omega t} e^{j\phi}\}$$

$$v(t) = \text{R}\{ \underbrace{V_m e^{j\phi}}_{\text{complex number}} e^{j\omega t} \}$$

complex number
"Phasor"
representation

• Phasor transform

Polar Form $\vec{V} = V_m e^{j\phi} = \mathcal{R}\{V_m \cos(\omega t + \phi)\}$

Rectangular Form $\vec{V} = V_m \cos \phi + j V_m \sin \phi$

the phasor transform transfers the sinusoidal function from the time domain to the complex-number domain.

• Angle Notation

$\vec{V} = V_m e^{j\phi} = V_m \angle \phi$ change from Radian to degrees.

• Polar Form vs. Rectangular Form

Let $\vec{V} = x + jy$

$\Rightarrow V_m = \sqrt{x^2 + y^2}$

and $\phi = \tan^{-1}(\frac{y}{x})$

• Multiplication and Division

Let $\vec{V}_1 = V_1 e^{j\phi_1} = V_1 \angle \phi_1$

$\vec{V}_2 = V_2 e^{j\phi_2} = V_2 \angle \phi_2$

$\therefore \vec{V}_1 \cdot \vec{V}_2 = V_1 V_2 \angle \phi_1 + \phi_2$

$\frac{\vec{V}_1}{\vec{V}_2} = \frac{V_1}{V_2} \angle \phi_1 - \phi_2$

• Addition and Subtraction

$\vec{V} = \vec{V}_1 + \vec{V}_2$

$= V_1 \angle \phi_1 + V_2 \angle \phi_2$

① Change to Rectangular "Complex numbers" $\Rightarrow = V_1 \cos \phi_1 + j V_1 \sin \phi_1 + V_2 \cos \phi_2 + j V_2 \sin \phi_2$

② Add complex number $\Rightarrow = \underbrace{[V_1 \cos \phi_1 + V_2 \cos \phi_2]}_{\text{Real part}} + j \underbrace{[V_1 \sin \phi_1 + V_2 \sin \phi_2]}_{\text{Imaginary part}}$

$\vec{V} = V_m \angle \phi$

11.1 Balanced Three-Phase Voltages Lecture 1 P.3


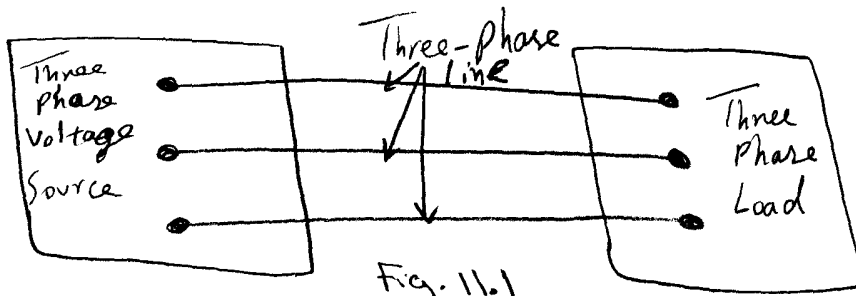


Fig. 11.1

- A Balanced Three-phase Voltages Consist of

- Three sinusoidal voltages ~~that~~.

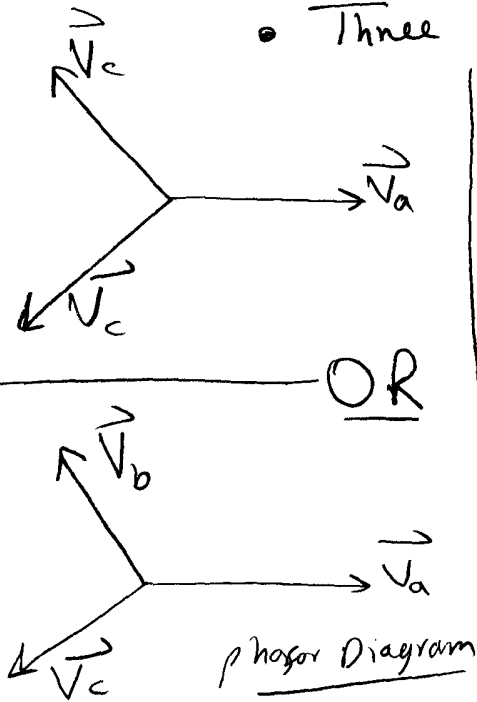

$$\left. \begin{aligned} \vec{V}_a &= V_m \angle 0^\circ \\ \vec{V}_b &= V_m \angle -120^\circ \\ \vec{V}_c &= V_m \angle +120^\circ \end{aligned} \right\} \text{Positive Phase Sequence}$$


$$\left. \begin{aligned} \vec{V}_a &= V_m \angle 0^\circ \\ \vec{V}_b &= V_m \angle +120^\circ \\ \vec{V}_c &= V_m \angle -120^\circ \end{aligned} \right\} \text{Negative Phase Sequence}$$

- Important Notes:


- The sum of balanced-three phase voltages is zero $\Rightarrow \vec{V}_a + \vec{V}_b + \vec{V}_c = 0 \rightarrow$ verify from phasor Diagram
- If we know the phase sequence and one voltage in the set, we know the entire set.

11.2 Three-Phase Voltage Sources

Y-Connected Source

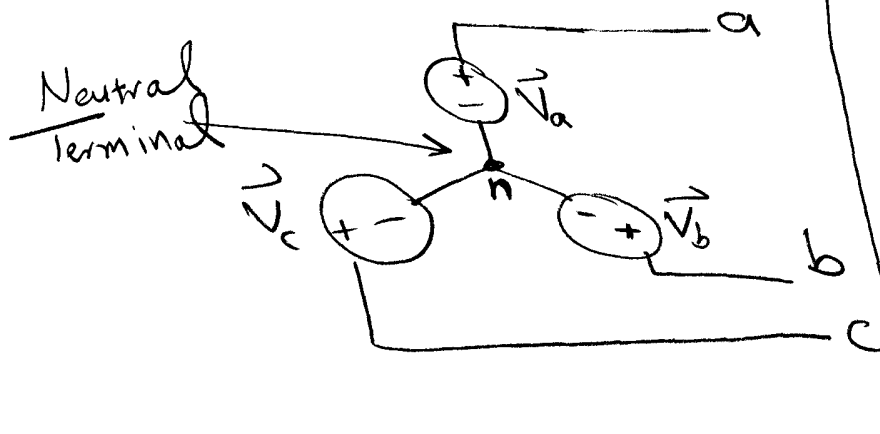


Δ-Connected Source

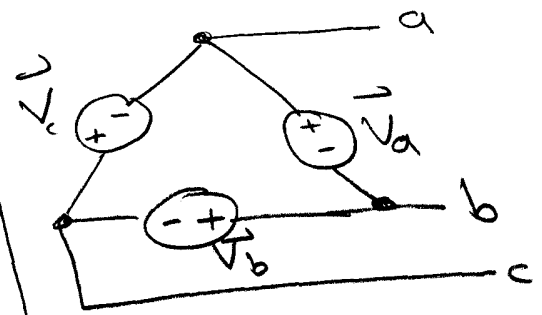


— Three-phase source model with winding impedance

Y-Connected

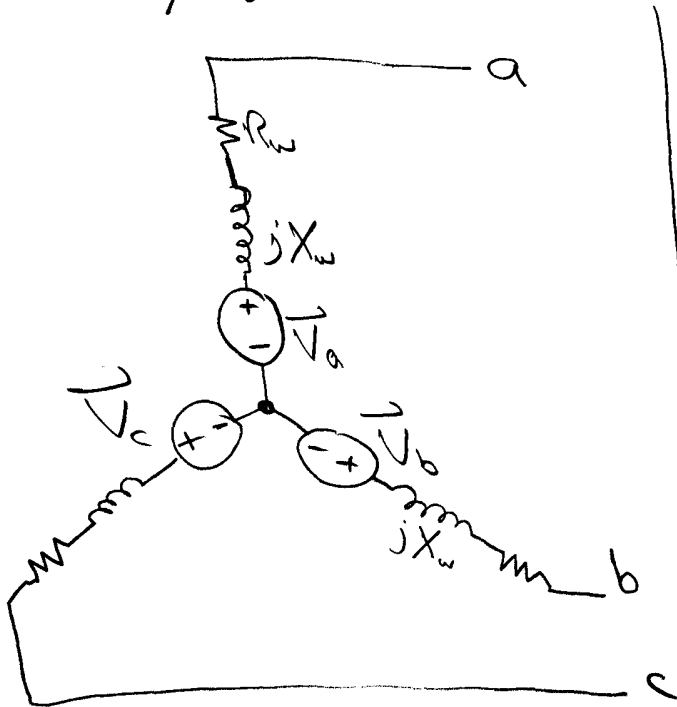

Δ-Connected

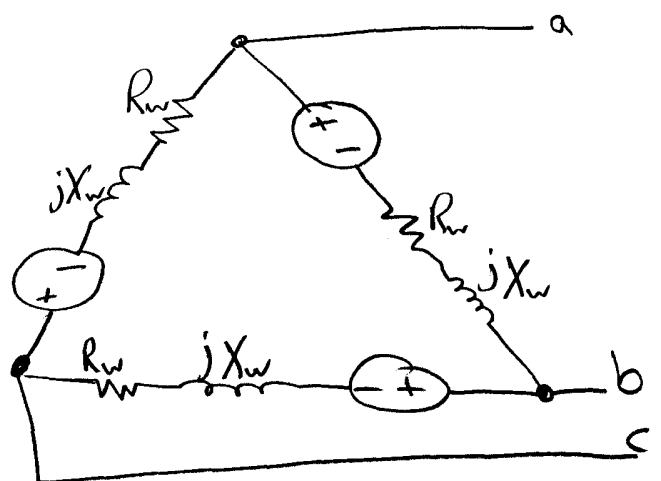


Since three-phase sources and loads can be either Y or Δ connected, there are four possible configurations:

Source	Load
Y	Y
Y	Δ
Δ	Y
Δ	Δ

11.3 Analysis of Y - Y Circuit

- We begin by analyzing the Y - Y circuit, the remaining three arrangements can be reduced to a Y - Y equivalent circuit.

- A three-phase Y - Y system.

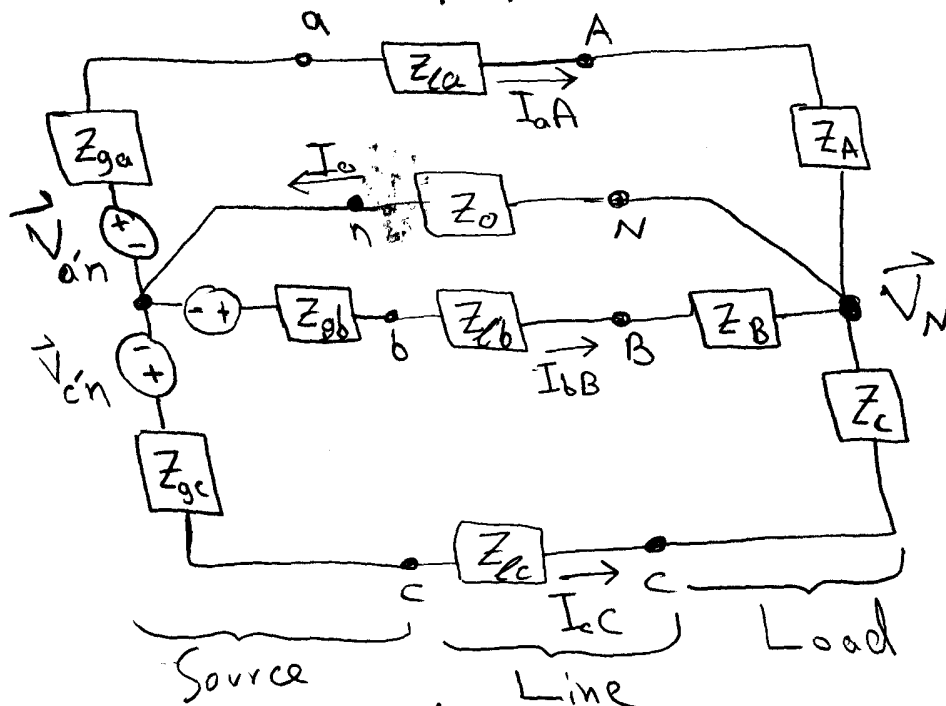

The node voltage equation at node N is:

$$\frac{\vec{V}_N}{Z_0} + \frac{\vec{V}_N - \vec{V}_{a'n}}{Z_{L1} + Z_{A1}} + \frac{\vec{V}_N - \vec{V}_{b'n}}{Z_{L2} + Z_{B2}} + \frac{\vec{V}_N - \vec{V}_{c'n}}{Z_{L3} + Z_{C3}} = 0$$

- For a balanced three-phase circuit,

we have the following conditions:

- 1- The voltage sources form a set of balanced three-phase voltages.
- 2- The impedance of each phase of the voltage source is the same $\Rightarrow Z_{g_a} = Z_{g_b} = Z_{g_c}$
- 3- The impedance of each line conductor is the same.
 $\Rightarrow Z_{l_a} = Z_{l_b} = Z_{l_c}$
- 4- The impedance of each phase of the load is the same
 $\Rightarrow Z_A = Z_B = Z_C$

Thus, the three phase Y-Y system is:

$$\vec{V}_N \left(\frac{1}{Z_0} + \frac{3}{Z_\phi} \right) = \frac{\vec{V}_{a'n} + \vec{V}_{b'n} + \vec{V}_{c'n}}{Z_\phi}$$

where,

Single Phase Impedance $\rightarrow Z_\phi = Z_A + Z_{l_a} + Z_{g_a} = Z_B + Z_{l_b} + Z_{g_b} = Z_C + Z_{l_c} + Z_{g_c}$

Since $\vec{V}_{a'n} + \vec{V}_{b'n} + \vec{V}_{c'n} = 0$

$$\Rightarrow \vec{V}_N = 0$$


When the circuit is balanced,
the three line currents are

$$\vec{I}_{aA} = \frac{\vec{V}_{an}}{Z_{\phi}}$$

$$\vec{I}_{bB} = \frac{\vec{V}_{bn}}{Z_{\phi}}$$

$$\vec{I}_{cC} = \frac{\vec{V}_{cn}}{Z_{\phi}}$$

- Single-Phase Equivalent Circuit

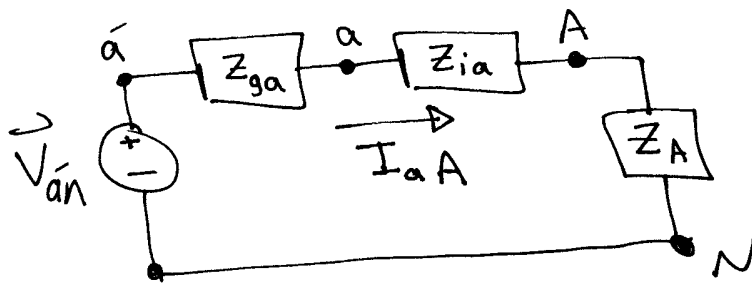


- If we analyse A single-phase, we
can get the values of other phases

- Note that the current in the neutral conductor is

$$I_o = I_{aA} + I_{bB} + I_{cC}$$
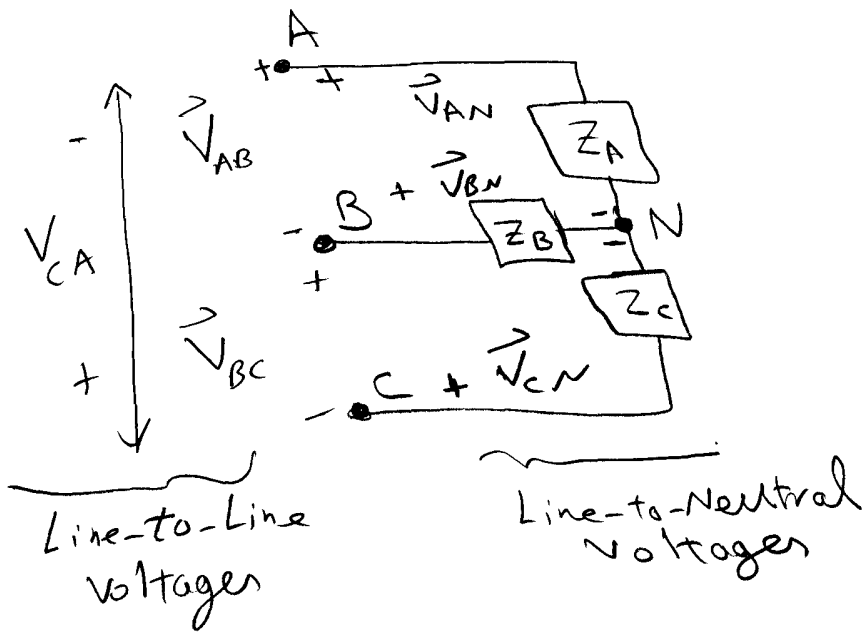
$$= 0 \Rightarrow \text{for a balanced three-phase circuit.}$$



Q- What is the relation between Line-to-Line and Line-to-Neutral voltages?

- Assume a positive phase sequence, Let the line-to-neutral voltages be:

$$\left. \begin{aligned} \vec{V}_{AN} &= V_{\phi} \angle 0^\circ \\ \vec{V}_{BN} &= V_{\phi} \angle -120^\circ \\ \vec{V}_{CN} &= V_{\phi} \angle +120^\circ \end{aligned} \right\} \begin{array}{l} V_{\phi} \text{ is the magnitude} \\ \text{of the line-to-neutral} \\ \text{voltage.} \end{array}$$

- Using Kirchhoff's voltage Law, the line-to-line voltages are:

$$\vec{V}_{AB} = \vec{V}_{AN} - \vec{V}_{BN} = V_{\phi} \angle 0^\circ - V_{\phi} \angle -120^\circ = \sqrt{3} V_{\phi} \angle 30^\circ$$


$$\vec{V}_{BC} = \vec{V}_{BN} - \vec{V}_{CN} = \sqrt{3} V_{\phi} \angle -90^\circ$$

$$\vec{V}_{CA} = \vec{V}_{CN} - \vec{V}_{AN} = \sqrt{3} V_{\phi} \angle 150^\circ$$

- Thus, Line-to-Line voltages

- Perform a balanced three-phase voltages
- the magnitude is $\sqrt{3}$ by the line-to-neutral.
- the phase is 30° plus the line-to-neutral phase.

- phasor Diagrams

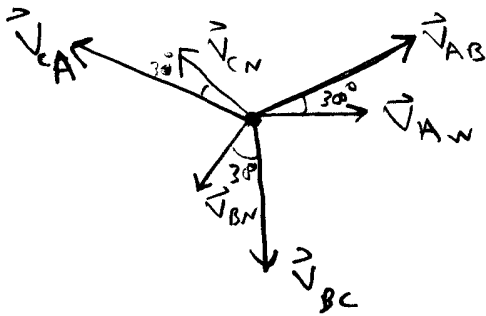

- Terminology

Line voltage: refers to the voltage across any pair of lines

(V_ϕ) Phase voltage: refers to the voltage across a single phase

Line current: refers to the current in a single line


(I_ϕ) Phase current: refers to the current in a single phase

" ϕ letter used to denote phase"

- Example 11.1 in class assignment

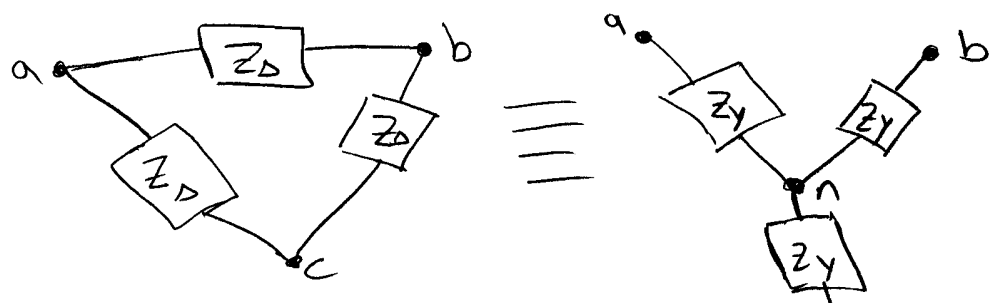
11.4 Analysis of the Y-Δ Circuit

— Δ Connected Load can be transformed to Y connected Load.



$Z_Y = \frac{Z_{\Delta}}{3}$ → See section 9.6

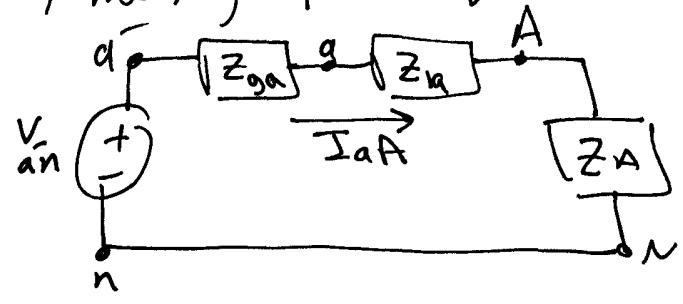— Then, the single phase equivalent circuit is




* Note that the phase voltages are the same as the line voltages.

— What is the Relation between phase currents and Line currents?

Line Currents: $\vec{I}_{aA}, \vec{I}_{bB},$ and \vec{I}_{cC}
 Phase Currents: $\vec{I}_{AB}, \vec{I}_{BC}$ and \vec{I}_{CA}

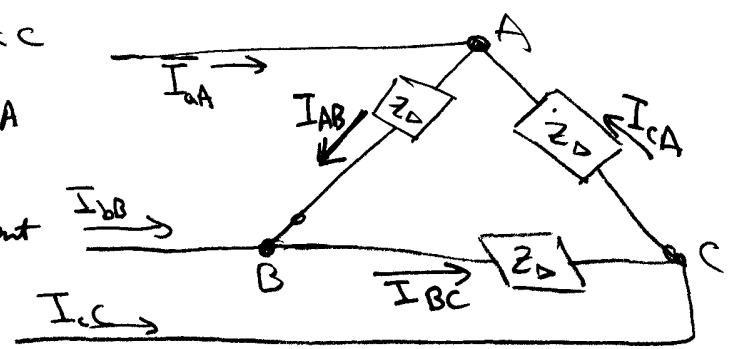— First Find the line currents From the Single phase equivalent Circuit as shown above.



— There is a Relation between Line and Phase currents.

Let the phase currents be:

$$\vec{I}_{AB} = I_{\phi} \angle 0^{\circ}, \quad \vec{I}_{BC} = I_{\phi} \angle -120^{\circ} \quad \text{and} \quad \vec{I}_{CA} = I_{\phi} \angle 120^{\circ}$$

then the line currents will be:


$$\begin{aligned} \vec{I}_{aA} &= \vec{I}_{AB} - \vec{I}_{CA} = I_{\phi} \angle 0^{\circ} - I_{\phi} \angle 120^{\circ} \\ &= \sqrt{3} I_{\phi} \angle -30^{\circ} \end{aligned}$$

line current lags phase current by 30°

Similarly,

$$\vec{I}_{bB} = \sqrt{3} I_{\phi} \angle -150^{\circ}$$

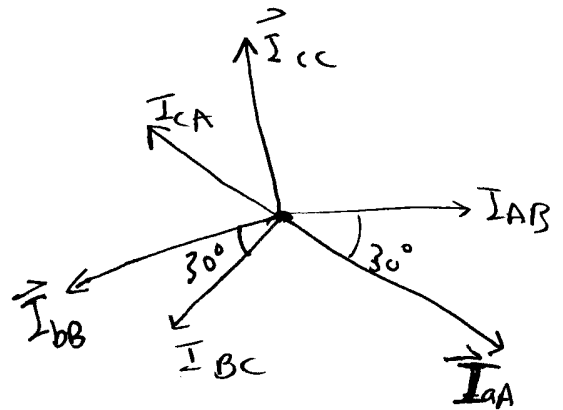
$$\vec{I}_{cC} = \sqrt{3} I_{\phi} \angle 90^{\circ}$$



See Example 11.2

11.5 Power Calculations in Balanced Three-Phase Circuits.

Background

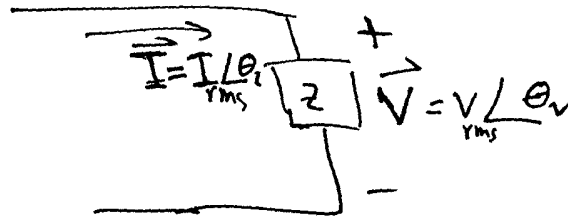

The complex power is

$$S = P + jQ$$

Complex Power \rightarrow $S = P + jQ$
 Average Power \rightarrow P
 Reactive Power \rightarrow Q

$$|S| \equiv \text{volt-amps}$$

$$P \equiv \text{Watts}$$

$$Q = \text{var}$$

$$S = \vec{V} \vec{I}^* \text{ --- conjugate}$$

$$= V_{rms} I_{rms} \angle (\theta_v - \theta_i)$$

$$|S| = \sqrt{P^2 + Q^2}$$

Average Power $\Rightarrow P = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$

Reactive Power $\Rightarrow Q = V_{rms} I_{rms} \sin(\theta_v - \theta_i)$

Power factor $\Rightarrow \text{pf} = \cos(\theta_v - \theta_i)$

Reactive factor $\Rightarrow \text{rf} = \sin(\theta_v - \theta_i)$

Average Power in a Balanced Y load


The Power in the a-phase,

$$P_A = |V_{AN}| |I_{aA}| \cos(\theta_{v_A} - \theta_{i_A})$$

similarly, at other phases

$$P_B = |V_{BN}| |I_{bB}| \cos(\theta_{v_B} - \theta_{i_B})$$

$$P_C = |V_{CN}| |I_{cC}| \cos(\theta_{v_C} - \theta_{i_C})$$

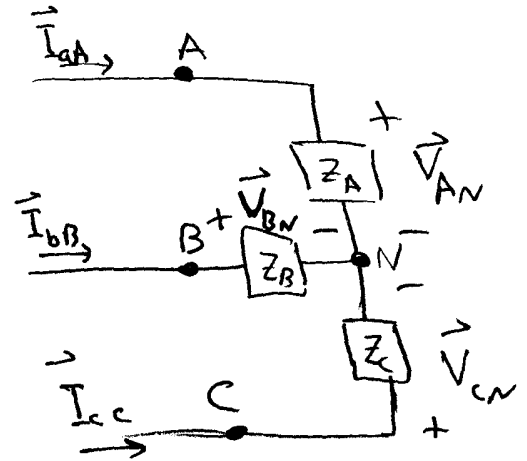

in a Balanced three-phase system;

$$V_\phi = |V_{AN}| = |V_{BN}| = |V_{CN}|$$

and $I_\phi = |I_{aA}| = |I_{bB}| = |I_{cC}|$

$$\theta_\phi = \theta_{v_A} - \theta_{i_A} = \theta_{v_B} - \theta_{i_B} = \theta_{v_C} - \theta_{i_C}$$

Per phase Power $\Rightarrow P_\phi$

$$P_A = P_B = P_C = P_\phi = V_\phi I_\phi \cos \theta_\phi$$

The total power is

$$P_T = 3 P_\phi = 3 V_\phi I_\phi \cos \theta_\phi$$

Phase Voltage Phase Current

In Terms of Line currents and Voltages

Average Real Power \rightarrow

$$P_T = 3 \left(\frac{V_L}{\sqrt{3}} \right) I_L \cos \theta_\phi$$

$$= \sqrt{3} V_L I_L \cos \theta_\phi$$

$$\text{Reactive Power} \Rightarrow Q_\phi = V_\phi I_\phi \sin \theta_\phi$$

$$\text{Total reactive Power} \Rightarrow Q_T = 3 Q_\phi = \sqrt{3} V_L I_L \sin \theta_\phi$$

$$\text{Complex Power} \Rightarrow S_\phi = P_\phi + j Q_\phi = \vec{V}_\phi \vec{I}_\phi^*$$

$$\text{Total complex Power} \Rightarrow S_T = 3 S_\phi = \sqrt{3} V_L I_L \angle \theta_\phi^\circ$$

For Balanced Δ load:


For a balanced Δ load;

Average Power per phase

$$P_\phi = V_\phi I_\phi \cos \theta_\phi$$

Total power
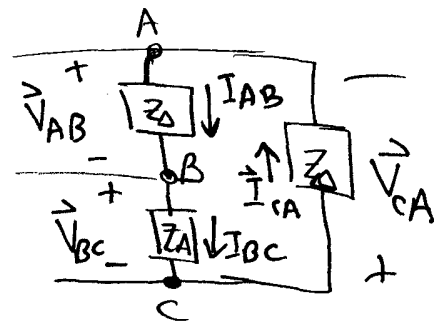
$$\begin{aligned} P_T &= 3 V_\phi I_\phi \cos \theta_\phi \\ &= 3 \frac{1}{2} \left(\frac{I_L}{\sqrt{3}} \right) \cos \theta_\phi \\ &= 3 V_L I_L \cos \theta_\phi \end{aligned}$$



Total Reactive Power

$$Q_T = 3 Q_\phi = 3 V_\phi I_\phi \sin \theta_\phi$$


Complex Power per phase:

$$S_\phi = P_\phi + j Q_\phi = \vec{V}_\phi \vec{I}_\phi^*$$

$$S_T = 3 S_\phi = \sqrt{3} V_L I_L \angle \theta_\phi^\circ$$

See Examples 11.3, 11.4, 11.5.

8.1 Parallel RLC Circuit

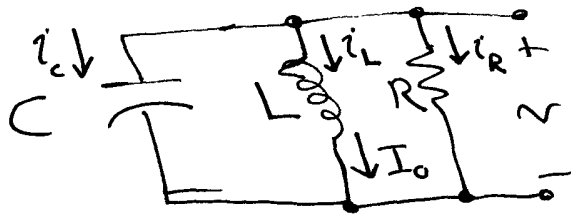

"Second-Order"
Circuits

$$\frac{v}{R} + \frac{1}{L} \int_0^t v dt + I_0 + C \frac{dv}{dt} = 0$$

↑
constant
"initial
condition"

Differentiate once

$$\frac{1}{R} \frac{dv}{dt} + \frac{v}{L} + C \frac{d^2 v}{dt^2} = 0$$

Second Order
Differential
Equation

$$\Rightarrow \frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{v}{LC} = 0$$

How can we solve this?

— It makes sense to assume that the solution will be exponential. why?

Thus, Assume that

$$v = A e^{st} \quad ; \text{ where } A \text{ and } s \text{ are unknown constants}$$

$$\Rightarrow A s^2 e^{st} + \frac{A s}{RC} e^{st} + \frac{A e^{st}}{LC} = 0$$

or

$$A e^{st} \left(s^2 + \frac{s}{RC} + \frac{1}{LC} \right) = 0$$

the roots are;

$$\boxed{s^2 + \frac{s}{RC} + \frac{1}{LC} = 0}$$

⇒ Characteristic equation,

The roots are:

$$s_1 = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$s_2 = -\frac{1}{2RC} - \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

Thus we have two solutions:

$$v_1 = A_1 e^{s_1 t} \quad \text{and} \quad v_2 = A_2 e^{s_2 t}$$

Their sum is also a solution:

$$v = v_1 + v_2 = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

∴ The Natural Response of parallel RLC circuit is

$$\boxed{v = A_1 e^{s_1 t} + A_2 e^{s_2 t}} \quad \leftarrow \text{Natural Response of parallel RLC}$$

Let $\alpha = \frac{1}{2RC}$ and $\omega_0 = \frac{1}{\sqrt{LC}}$

∴ The roots of the characteristic equation are:

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

Case 1

$$\alpha^2 > \omega_0^2 \Rightarrow s_1 \text{ and } s_2 \text{ are Real} \\ \Rightarrow \text{overdamped}$$

$\alpha \Rightarrow$ Neper frequency
"rad/s"

$\omega_0 \Rightarrow$ Resonant radian frequency.
"rad/s"

Case 2

$$\alpha^2 < \omega_0^2 \Rightarrow s_1 \text{ and } s_2 \text{ are complex conjugates} \\ \Rightarrow \text{Underdamped}$$

Case 3

$$\alpha^2 = \omega_0^2 \Rightarrow s_1 \text{ and } s_2 \text{ are Real and equal} \\ \Rightarrow \text{critically damped.}$$

8.2 Forms of the Natural Response of a Parallel RLC Circuit

Case 1 Overdamped Voltage Response

The natural response is in this form:

$$v = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

Q) How to find the constants A_1 and A_2 ?


- We can find them from the initial conditions, which are the values of $v(0^+)$ and $\frac{dv}{dt}(0^+)$.
- These values are determined from $\frac{dv}{dt}$ the initial voltage on the capacitor V_0 and the initial current in the inductor I_0 .

Thus, $v(0^+) = A_1 + A_2$; ~~where~~ $v(0^+)$ is the initial voltage in the capacitor V_0

$$\frac{dv(0^+)}{dt} = s_1 A_1 + s_2 A_2 ; \text{ where } \frac{dv(0^+)}{dt} = \frac{i_c(0^+)}{C}$$

and $i_c(0^+) = -\frac{V_0}{R} - I_0$

Example 8.2:

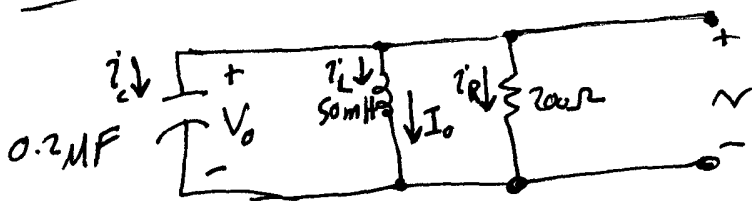

For the above circuit, $v(0^+) = 12 \text{ V}$ and $i_L(0^+) = 30 \text{ mA}$

- Find the initial current in each branch of the circuit
- Find the initial value of $\frac{dv}{dt}$
- Find the expression for $v(t)$
- Sketch $v(t)$ in the interval $0 \leq t \leq 250 \text{ ms}$

Underdamped Voltage Response

Lecture 3 P. 4

* s_1 and s_2 are complex conjugates

$$\text{Let } s_1 = -\alpha + j\sqrt{\omega_0^2 - \alpha^2}$$

$$= -\alpha + j\omega_d \quad ; \quad \omega_d \equiv \text{damped frequency}$$

$$s_2 = -\alpha - j\omega_d = -\alpha - j\sqrt{\omega_0^2 - \alpha^2}$$

* the underdamped voltage response is

$$v(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t \quad \leftarrow \begin{array}{l} \text{Voltage} \\ \text{Natural Response} \\ \text{"Underdamped"} \end{array}$$

Proof

From Euler identity:

$$e^{\pm j\theta} = \cos \theta \pm j \sin \theta$$

$$\text{Thus } v(t) = A_1 e^{(-\alpha + j\omega_d)t} + A_2 e^{(-\alpha - j\omega_d)t}$$

$$= A_1 e^{-\alpha t} e^{j\omega_d t} + A_2 e^{-\alpha t} e^{-j\omega_d t}$$

$$= e^{-\alpha t} (A_1 \cos \omega_d t + j A_1 \sin \omega_d t + A_2 \cos \omega_d t - j A_2 \sin \omega_d t)$$

$$= e^{-\alpha t} [(A_1 + A_2) \cos \omega_d t + j(A_1 - A_2) \sin \omega_d t]$$

$$\text{Let } B_1 = A_1 + A_2 \text{ and } B_2 = j(A_1 - A_2)$$

Since A_1 and A_2 are complex conjugates

$\Rightarrow B_1$ and B_2 are Real

$$\text{Thus, } v(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$$

* To Find B_1 and B_2 .

From the initial conditions,

$$v(0^+) = v_0 = B_1$$


$$\frac{dv(0^+)}{dt} = \frac{i_c(0^+)}{C} = -\alpha B_1 + \omega_d B_2$$

* Closer look at the underdamped Response.

$$v = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$$

damping factor

damped Freq.

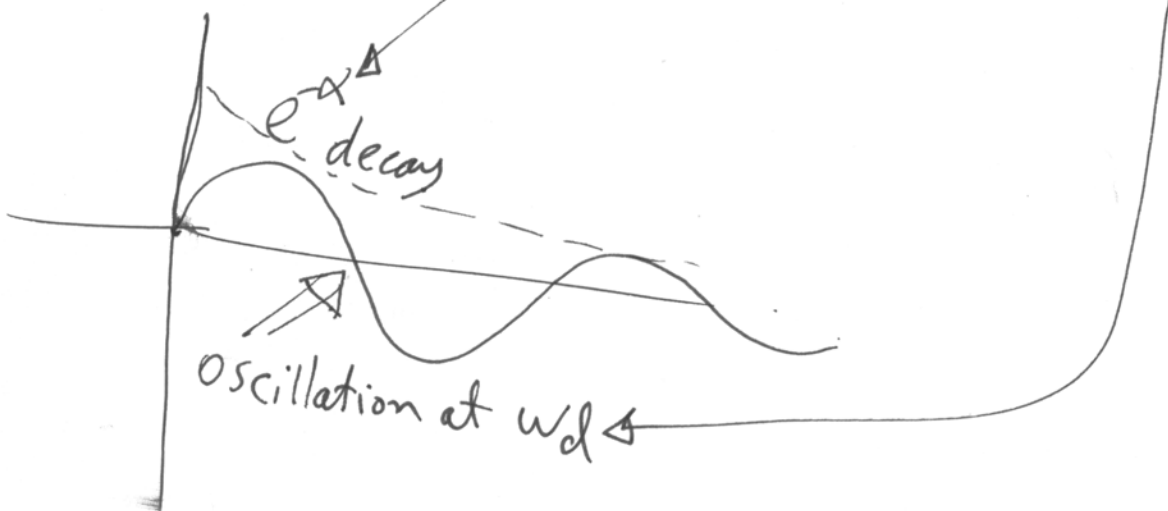

The Critically Damped Voltage Response

When $\omega_0 = \alpha \Rightarrow s_1$ and s_2 are real and equal

$$s_1 = s_2 = -\alpha = -\frac{1}{2RC}$$

$$\Rightarrow v = (A_1 + A_2) e^{-\alpha t} = A_0 e^{-\alpha t}$$

However, this equation can't satisfy two independent initial conditions.

Thus, the correct Response for critically damped Parallel RLC circuit is

$$v(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$

← This is from differential equation theory.


To Find D_1 and D_2 , solve:

$$v(0^+) = v_0 = D_2$$

$$\frac{dv(0^+)}{dt} = \frac{i_c(0^+)}{C} = D_1 - \alpha D_2$$

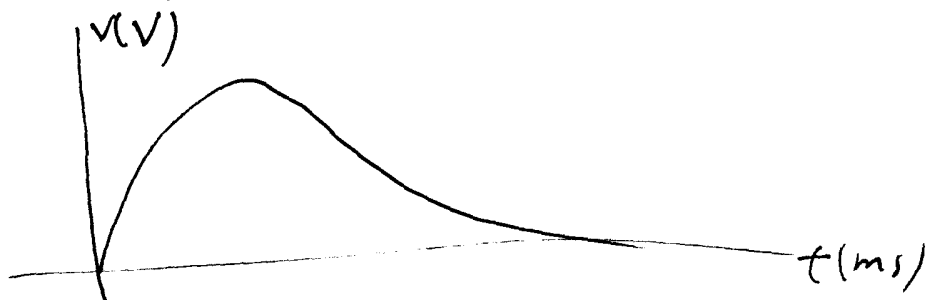Example 8.5



$$v(t) = 98,000 t e^{-1000 t} \text{ V}$$



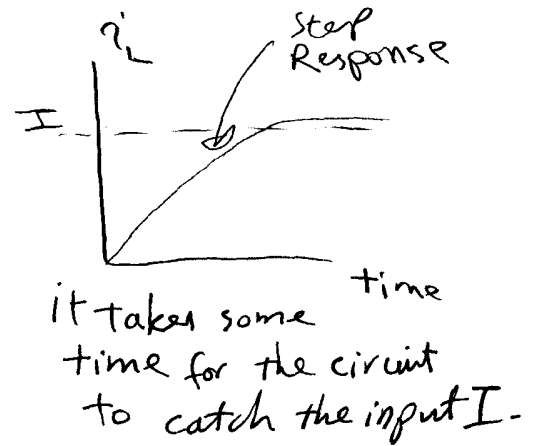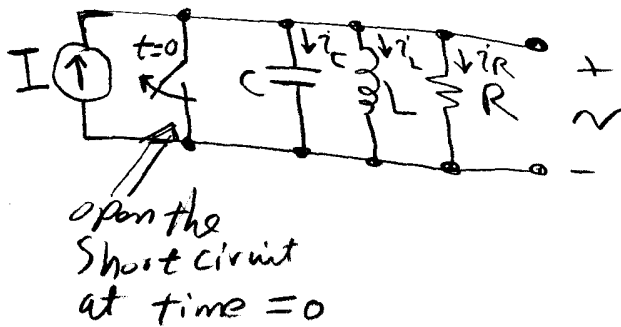8.3 The step Response of a Parallel RLC Circuit.

What is the step Response?

It is the response of an RLC circuit caused by the sudden input of a dc current.



* We focus on the current in the inductive branch $\{ i_L \}$.

* We assume that the initial energy is zero.

* The inductor current i_L :

From Kirchhoff's Current Law,

$$i_L + i_R + i_C = I$$

or

$$i_L + \frac{v}{R} + C \frac{dv}{dt} = I$$

Since $v = L \frac{di_L}{dt} \Rightarrow \frac{dv}{dt} = L \frac{d^2 i_L}{dt^2}$

\Rightarrow

$$\frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{i_L}{LC} = \frac{I}{LC}$$

- Similar to the natural Response

Lecture 4 P.2

① - Find the roots of the characteristic Equation

$$s^2 + \frac{s}{R_c} + \frac{1}{LC} = 0 \Rightarrow s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$
$$\alpha = \frac{1}{2R_c}, \omega_0 = \frac{1}{\sqrt{LC}}$$

② - Based on the roots $\{s_1, s_2\}$, we have three possible cases.

Case 1: $i_L = I + A_1 e^{s_1 t} + A_2 e^{s_2 t} \Rightarrow$ Overdamped

Case 2: $i_L = I + B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t \Rightarrow$ Underdamped

Case 3: $i_L = I + D_1 e^{-\alpha t} + D_2 e^{-\alpha t} \Rightarrow$ Critically Damped

③ Find the constant from the initial conditions.


at $i_L(0)$ and $\frac{di_L(0)}{dt}$.

* Solve Examples 8.6, 8.7, 8.8, 8.9, and 8.10

+ Solve Assessment Problem 8.6

8.4 The Natural and Step Response of a series RLC Circuit.

Part 1: The Natural Response

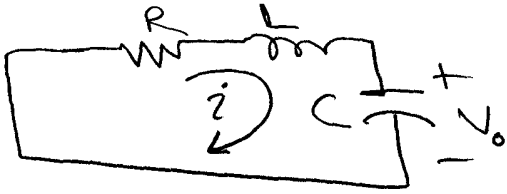

— Summing the voltages inside the loop:

$$Ri + L \frac{di}{dt} + \frac{1}{C} \int i d\tau + V_0 = 0$$

— Differentiate and Rearrange terms:

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0$$

— The Characteristic equation for series RLC is

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

$$\Rightarrow s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

where, $\alpha = \frac{R}{2L}$ rad/s \Rightarrow Neper freq.

$\omega_0 = \frac{1}{\sqrt{LC}}$ rad/s \Rightarrow Resonant freq.


— Three possible cases:

Overdamped: $i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$

Underdamped: $i(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$

Critically damped: $i(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$

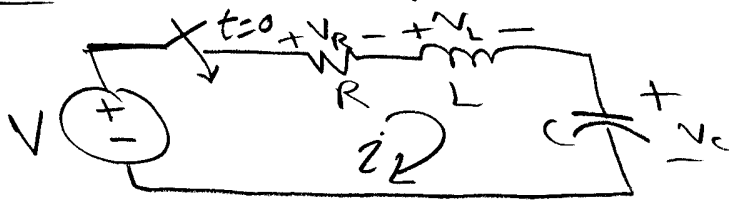Part 2: Step Response of a Series RLC Circuit



— Applying Kirchhoff's voltage Law,

$$V = Ri + L \frac{di}{dt} + v_C$$

$$\text{since } i = C \frac{dv_C}{dt} \Rightarrow \frac{di}{dt} = C \frac{d^2 v_C}{dt^2}$$

$$\Rightarrow \frac{d^2 v_C}{dt^2} + \frac{R}{L} \frac{dv_C}{dt} + \frac{v_C}{LC} = \frac{V}{LC}$$

— Three possible solutions:

$$\text{Overdamped: } v_C = V_f + A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\text{Underdamped: } v_C = V_f + B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$$

$$\text{Critically damped: } v_C = V_f + D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$

— Solve Example 8.11 and 8.12

— Solve Assessment Problem 8.7, 8.8.