


- What is a Filter?

Filters are frequency-Selective Circuits. They can pass some frequencies in a certain band and can stop others.


- Discussion: - think about applications for Filters.  
- what Filters are used for?

14.1 There are four basic types of Filters

1 Low Pass Filters [Ideal]

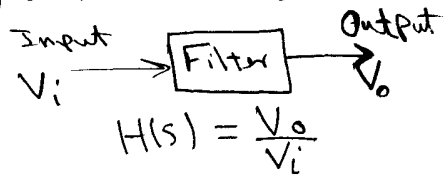


Magnitude Response

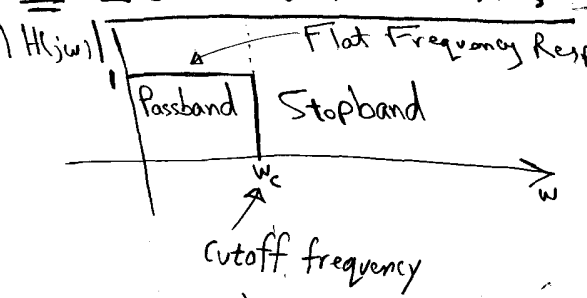

Note: Ideal Filters

Phase Response


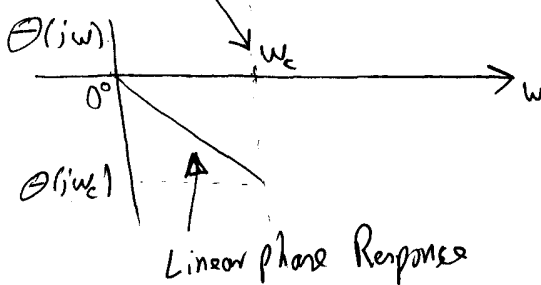


Def:



Passband: the band of frequencies that pass through the circuit.

Stopband: the band of frequencies that attenuate and get blocked by the circuit



2 High Pass Filters [Ideal]

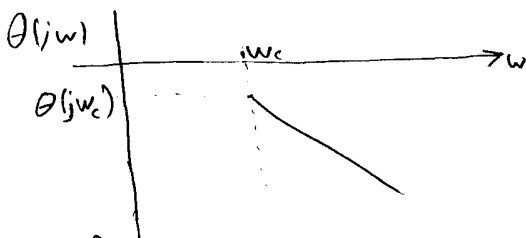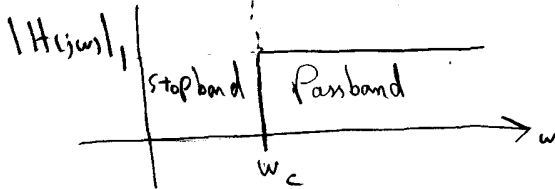


3 Bandpass filter [Ideal]

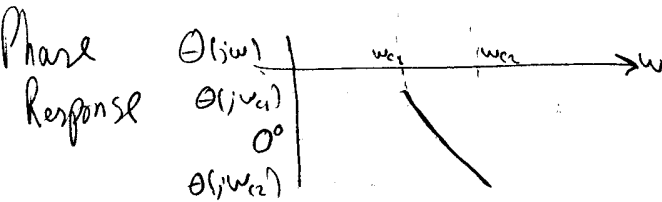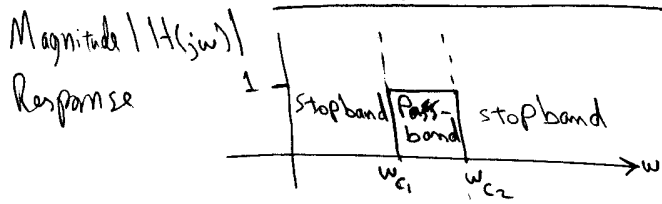

4 Bandreject Filter [Ideal]

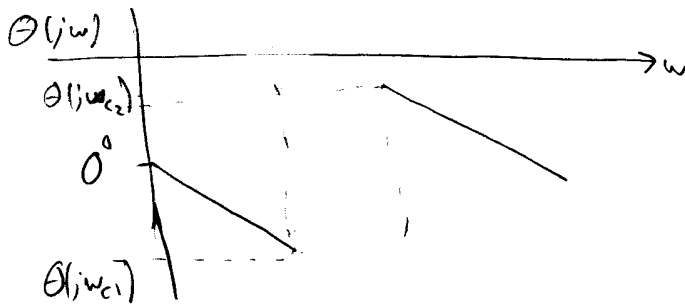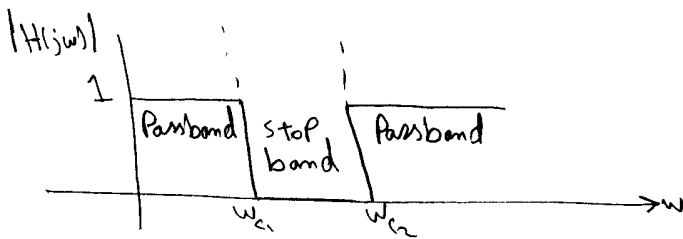


Series RL Circuit:

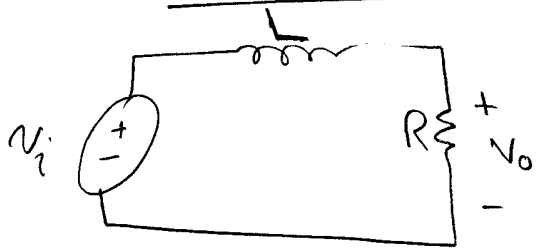

The impedance of the inductor is  $j\omega L$

at  $\omega = 0$

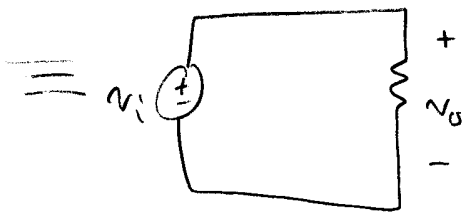

$$v_o = v_i$$

$$\Rightarrow |H(j\omega)|_{\omega=0} = \frac{v_o}{v_i} = 1$$

$\theta(j\omega)|_{\omega=0} = 0 \Rightarrow$  No phase shift


increasing  $\omega$  Low frequency  $\Rightarrow$  inductor impedance increases  $\Rightarrow$  voltage drop  $\Rightarrow v_o < v_i$  Passband

In addition, phase shift increases


At High frequency  $\Rightarrow$  there will be high voltage drop across the inductor  $\Rightarrow v_o \ll v_i$  Stop band

In addition  $\Rightarrow$  more phase shift

At  $\omega = \infty$

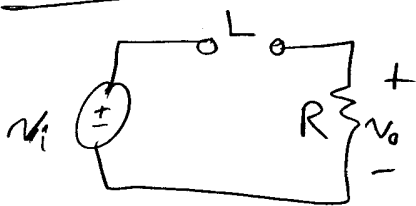

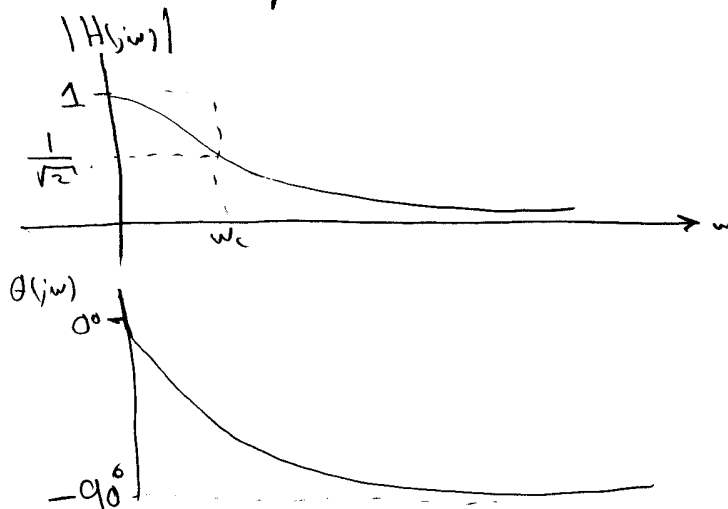$\Rightarrow$  The inductor impedance will be open  $\Rightarrow v_o = 0$



Cutoff frequency [the Half Power Frequency]


The definition for cutoff frequency widely used is the frequency for which the transfer function magnitude is decreased by the factor  $\frac{1}{\sqrt{2}}$  from its maximum value

$$|H(j\omega_c)| = \frac{1}{\sqrt{2}} A_{\max}$$

Thus, the output voltage in the passband ~~band~~ is at least 70.7% of the maximum possible amplitude.

In addition, the average power delivered to a load is at least 50% of the maximum average power.

⇒ It is called the half power frequency.

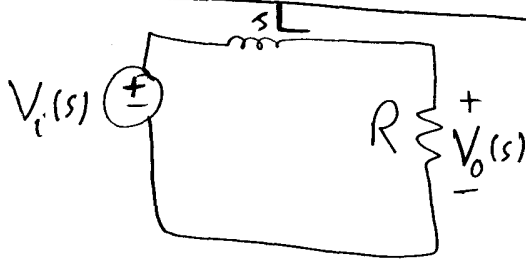Transfer Function of the series RL Circuit

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{R}{sL + R} = \frac{R/L}{s + R/L}$$

$$H(j\omega) = \frac{R/L}{j\omega + R/L} \neq \cancel{R/L}$$

$$\therefore |H(j\omega)| = \frac{R/L}{\sqrt{\omega^2 + (R/L)^2}} \equiv \text{Magnitude Response}$$

$$\text{and } \theta(j\omega) = -\tan^{-1}\left(\frac{\omega L}{R}\right) \equiv \text{Phase Response}$$

# Low-Pass Filters


P. 5

At the cutoff frequency,  $\omega_c$ , is

$$|H(j\omega_c)| = \frac{1}{\sqrt{2}} |1| = \frac{R/L}{\sqrt{\omega_c^2 + (R/L)^2}}$$

$$\Rightarrow \boxed{\omega_c = \frac{R}{L}}$$

## A Series RC Circuit

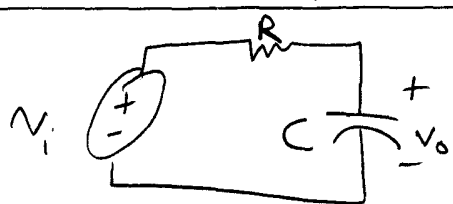

### Transfer Function

$$H(s) = \frac{1/RC}{s + \frac{1}{RC}}$$

$$|H(j\omega)| = \frac{1/RC}{\sqrt{\omega^2 + (\frac{1}{RC})^2}}$$

cutoff freq.

$$\omega_c = \frac{1}{RC}$$

### Qualitative Analysis

To have a quick understanding of the circuit characteristics, examine it by inspection.



- ① at zero frequency ( $\omega=0$ )
  - $\Rightarrow$  capacitor's impedance is infinite
  - $\Rightarrow v_o = v_i$
- ② Increasing the frequencies
  - $\Rightarrow$  the impedance of the capacitor decreases
  - $\Rightarrow$  voltage divides
  - $\Rightarrow v_o < v_i$
- ③ Infinite frequency ( $\omega=\infty$ )
  - $\Rightarrow$  the impedance of the capacitor is zero
  - $\Rightarrow$  short circuit
  - $\Rightarrow v_o = 0$

In General, the transfer function of a low-pass filter is

$$H(s) = \frac{\omega_c}{s + \omega_c}$$

# 14.3 High-Pass Filters

## The series RC Circuit

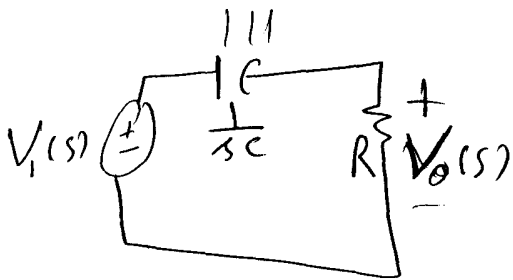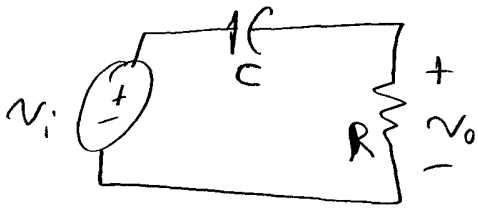

$$H(s) = \frac{R}{\frac{1}{sC} + R} = \frac{s}{s + 1/RC}$$

$$H(j\omega) = \frac{j\omega}{j\omega + 1/RC}$$

$$\Rightarrow |H(j\omega)| = \frac{\omega}{\sqrt{\omega^2 + (1/RC)^2}}$$


$$\theta(j\omega) = 90^\circ - \tan^{-1}\omega RC$$

the cutoff Freq.

$$\omega_c = \frac{1}{RC}$$
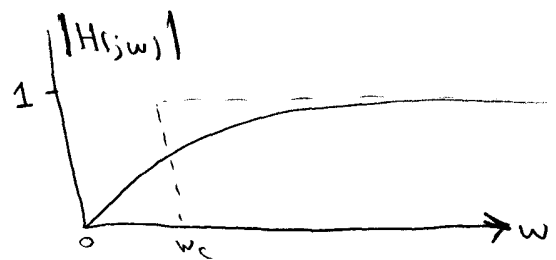
## Qualitative Analysis

- ① at  $\omega=0 \Rightarrow$  capacitor behaves like open circuit  
 $\Rightarrow$  no current flow  
 $\Rightarrow v_o = 0$
- ② Increasing  $\omega \Rightarrow$  capacitor's impedance decreases  
 $\Rightarrow$  voltage is divided  
 $\Rightarrow v_o$  increases
- ③ at  $\omega=\infty \Rightarrow$  capacitor is short  
 $\Rightarrow v_o = v_i$




See Example 14.3 For Series RL High-Pass Filter

In General, The transfer function for a high-pass filter is

$$H(s) = \frac{s}{s + \omega_c}$$

# 14.4 Bandpass Filters

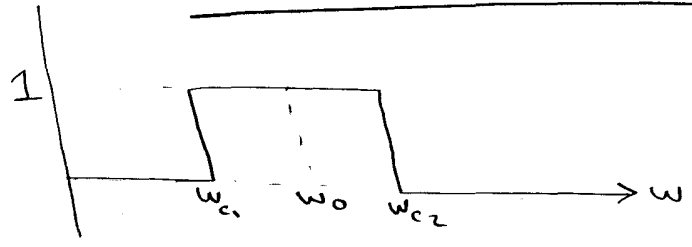


Def:  $\omega_0 \equiv$  Center frequency or resonant frequency

Bandwidth ( $\beta$ ) =  $\omega_{c2} - \omega_{c1}$

Quality Factor  $Q = \frac{\omega_0}{\beta}$

## Series RLC Circuit

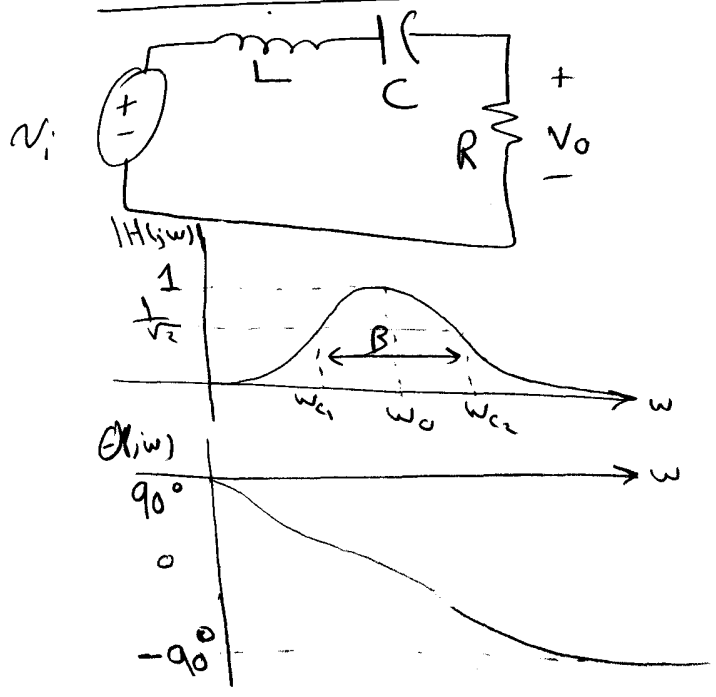


## Qualitative Analysis

① at  $\omega = 0 \Rightarrow$  Inductor is short and capacitor is open  
 $\Rightarrow$  No current flow  
 $\Rightarrow v_0 = 0$

② Increasing  $\omega$

- The impedance of the inductor is positive ( $+j\omega L$ ) and the impedance of the capacitor is negative ( $-\frac{j}{\omega C}$ )
- There will be a voltage drop across the inductor and capacitor and  $v_0 < v_i$
- At some frequency ( $\omega_0$ ), the impedance of the inductor will cancel the impedance of the capacitor. Therefore,  $v_0 = v_i$ . This is at the resonant frequency.
- Increasing  $\omega$  further, voltage drop is created across the inductor and capacitor and  $v_0 < v_i$  again.

## Quantitative Analysis

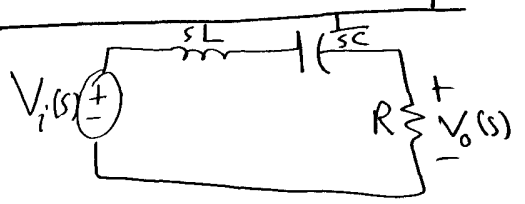

$$H(s) = \frac{R}{R + sL + \frac{1}{sC}}$$

$$= \frac{\frac{R}{L}s}{s^2 + (\frac{R}{L})s + \frac{1}{LC}}$$

$$|H(j\omega)| = \frac{\omega(\frac{R}{L})}{\sqrt{[\frac{1}{LC} - \omega^2]^2 + [\omega(\frac{R}{L})]^2}}$$

$$\phi(\omega) = 90^\circ - \tan^{-1}\left[\omega\left(\frac{R}{L}\right)\right]$$

③ at  $\omega = \infty$

- The inductor is open and the capacitor is short.  
 $\Rightarrow v_0 = 0$

# Bandpass Filters

P.8

## Center Frequency

the center frequency is the resonant frequency that makes the imaginary part zero.

$$j\omega_0 L + \frac{1}{j\omega_0 C} = 0$$

$$\Rightarrow \omega_0 = \sqrt{\frac{1}{LC}}$$

## Cutoff Frequency

$$|H(j\omega_c)| = \frac{1}{\sqrt{2}} |H_{max}|$$

$$\frac{\omega_c \left(\frac{R}{L}\right)}{\sqrt{\left[\frac{1}{LC} - \omega_c^2\right]^2 + \left(\omega_c \frac{R}{L}\right)^2}} = \frac{1}{\sqrt{2}}$$

$$\frac{1}{\sqrt{\left[\frac{1}{LC} - \omega_c^2\right]^2 + 1}} = \frac{1}{\sqrt{2}}$$

$$\frac{1}{\sqrt{\left[\left(\omega_c \frac{L}{R}\right) - \left(\frac{1}{\omega_c RC}\right)\right]^2 + 1}} = \frac{1}{\sqrt{2}}$$

$$\therefore \sqrt{\left[\frac{\omega_c L}{R} - \frac{1}{\omega_c RC}\right]^2 + 1} = \sqrt{2}$$

$$\left[\frac{\omega_c L}{R} - \frac{1}{\omega_c RC}\right]^2 + 1 = 2$$

$$\left[\frac{\omega_c L}{R} - \frac{1}{\omega_c RC}\right]^2 = 1$$

$$\Rightarrow \frac{\omega_c L}{R} - \frac{1}{\omega_c RC} = \pm 1$$

$$\boxed{\omega_c^2 L \pm \omega_c R - \frac{1}{C} = 0}$$

the two frequencies  $\{\omega_{c1}, \omega_{c2}\}$  must be positive

$$\Rightarrow \omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)}$$

$$\omega_{c2} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)}$$

what is the relation between the center freq. and cutoff freq?

$$\boxed{\omega_0 = \sqrt{\omega_{c1} \cdot \omega_{c2}}}$$

Verify.

Bandwidth

$$B = \omega_{c2} - \omega_{c1}$$

$$= \frac{R}{L}$$

Quality Factor

$$Q = \frac{\omega_0}{B} = \frac{\sqrt{1/LC}}{R/L} = \sqrt{\frac{L}{CR^2}}$$



Note:

The transfer function of a bandpass filter is:


$$H(s) = \frac{BS}{s^2 + \beta s + \omega_0^2} = \frac{R/L \cdot s}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$



# 14.5 Bandreject Filters

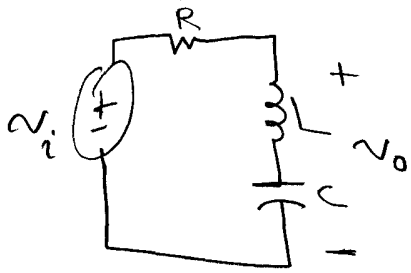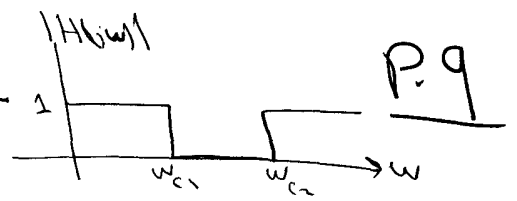

## Quantitative Analysis

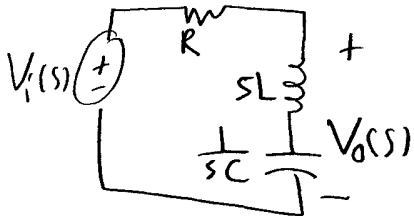

$$H(s) = \frac{sL + \frac{1}{sC}}{R + sL + \frac{1}{sC}}$$

$$= \frac{s^2 + \frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$= \frac{s^2 + \omega_0^2}{s^2 + \beta s + \omega_0^2}$$

$$|H(j\omega)| = \frac{|\frac{1}{LC} - \omega^2|}{\sqrt{(\frac{1}{LC} - \omega^2)^2 + (\frac{\omega R}{L})^2}}$$

$$\theta(j\omega) = -\tan^{-1} \left( \frac{\frac{\omega R}{L}}{\frac{1}{LC} - \omega^2} \right)$$

- Centre Freq.  $\omega_0 = \sqrt{\frac{1}{LC}}$
- Cutoff Freq.  $\omega_{c1} = \frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$
- $\omega_{c2} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$
- Bandwidth  $B = \frac{R}{L}$
- Quality Factor  $Q = \sqrt{L/C}$

## Qualitative Analysis

① at  $\omega = 0$

- Inductor is short
- Capacitor is open
- No voltage drop across the Resistor
- $\Rightarrow v_o = v_i$

② Increasing  $\omega$

- Inductor has positive impedance
- Capacitor has negative impedance
- voltage divides between the Resistor and the inductor and capacitor
- $v_o < v_i$

③ At Resonance ( $\omega_0$ )

- when  $\omega = \omega_0$ , the inductor's impedance will cancel the capacitor's impedance
- $\Rightarrow$  Both will act as short circuit with zero impedance
- $\Rightarrow v_o = 0$

④ Increasing  $\omega$

$$v_o < v_i \text{ same as part (2)}$$

⑤  $\omega = \infty$

- Inductor is open
- Capacitor is short
- No voltage drop across the Resistor
- $\Rightarrow v_o = v_i$

# Bode Diagrams

E.1, E.2, and E.4 only [Real Poles and Zeros]

$$H(s) = \frac{K(s+z_1)}{s(s+p_1)}$$

$$H(j\omega) = \frac{K(j\omega+z_1)}{j\omega(j\omega+p_1)}$$

$$H(j\omega) = \frac{Kz_1(1+j\omega/z_1)}{P_1(j\omega)(1+j\omega/P_1)}$$

Let  $K_0 = \frac{Kz_1}{P_1}$

$$H(j\omega) = \frac{K_0 |1+j\omega/z_1| \angle \psi_1}{|\omega| \angle 90^\circ |1+j\omega/P_1| \angle \beta_1}$$

$$= \frac{K_0 |1+j\omega/z_1|}{|\omega| |1+j\omega/P_1|} \angle (\psi_1 - 90^\circ - \beta_1)$$

Amplitude  $|H(j\omega)| = \frac{K_0 |1+j\omega/z_1|}{\omega |1+j\omega/P_1|}$

Phase  $\theta(\omega) = \psi_1 - 90^\circ - \beta_1$

Note that  $\psi_1 = \tan^{-1} \omega/z_1$

$\beta_1 = \tan^{-1} \omega/P_1$

## E.2 Straight Line Amplitude Plots

- In logarithmic value (decibel (dB)).

$$A_{dB} = 20 \log_{10} |H(j\omega)|$$

- why?

← Because addition and subtraction are easier than multiplication and division.

$$\begin{aligned} A_{dB} &= 20 \log_{10} \frac{K_0 |1+j\omega/z_1|}{\omega |1+j\omega/P_1|} \\ &= 20 \log_{10} K_0 + 20 \log_{10} |1+j\omega/z_1| \\ &\quad - 20 \log_{10} \omega - 20 \log_{10} |1+j\omega/P_1| \end{aligned}$$


Methodology: Plot each term above and then add them together to get  $A_{dB}$ .

Term 1:  $20 \log_{10} K_0$  is just a Horizontal Line.

Term 2:  $20 \log_{10} |1+j\omega/z_1|$


when  $\omega < z_1 \Rightarrow \text{Term 2} = 0$

when  $\omega \gg z_1 \Rightarrow \text{Term 2}$  is a Straight Line with a slope of 20 dB/decade.

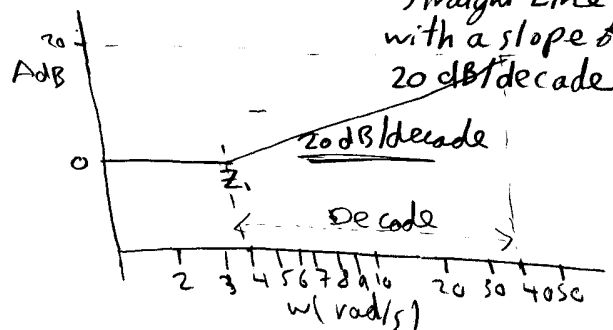

Term 3:  $-20 \log_{10} \omega$  is a straight line with -20 dB/decade

Term 4:  $-20 \log_{10} |1+j\omega/P_1|$

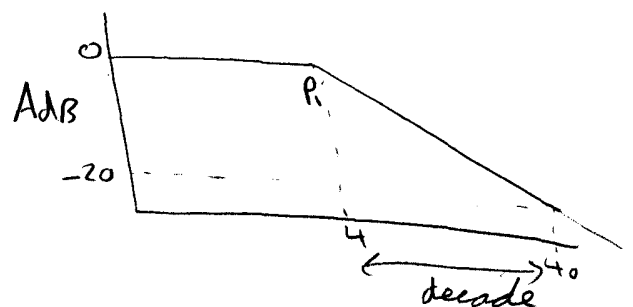

# Bode Diagrams

P. 11

Now add up all Plots to get the Amplitude Plot.

Example Let  $K_0 = \sqrt{10}$ ,  $Z_1 = 0.1 \text{ rad/s}$ ,  $P_1 = 5 \text{ rad/s}$

$$\Rightarrow A_{dB} = 20 \log_{10} \sqrt{10} + 20 \log_{10} \left| 1 + j \frac{\omega}{0.1} \right| - 20 \log_{10} \omega - 20 \log_{10} \left| 1 + j \frac{\omega}{5} \right|$$

