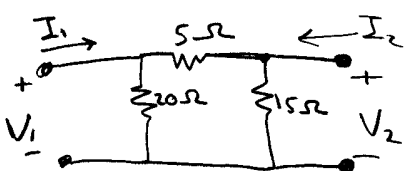


The Z Parameters "The impedance Parameter"

$$\left. \begin{aligned} Z_{11} &= \frac{V_1}{I_1} \Big|_{I_2=0} \Omega \\ Z_{12} &= \frac{V_1}{I_2} \Big|_{I_1=0} \Omega \\ Z_{21} &= \frac{V_2}{I_1} \Big|_{I_2=0} \Omega \\ Z_{22} &= \frac{V_2}{I_2} \Big|_{I_1=0} \Omega \end{aligned} \right\}$$

$$\left. \begin{aligned} \text{Then, } V_1 &= Z_{11} I_1 + Z_{12} I_2 \\ V_2 &= Z_{21} I_1 + Z_{22} I_2 \end{aligned} \right\}$$

Example



$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} = \frac{(20)(20)}{40} = 10 \Omega$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} \Rightarrow V_2 = \frac{V_1 (15)}{15+5} = 0.75 V_1$$

$$\Rightarrow Z_{21} = \frac{0.75 V_1}{\left(\frac{V_1}{10}\right)} \Big|_{I_2=0} = 7.5 \Omega$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} = \frac{(15)(25)}{40} = 9.375 \Omega$$

For  $Z_{12}$ , when port 1 is open,  $I_1$  is zero and the voltage  $V_1$  is

$$V_1 = \frac{V_2}{5+20} (20) = 0.8 V_2$$

The Y parameters "The admittance"

$$\left. \begin{aligned} Y_{11} &= \frac{I_1}{V_1} \Big|_{V_2=0} S \\ Y_{12} &= \frac{I_1}{V_2} \Big|_{V_1=0} S \\ Y_{21} &= \frac{I_2}{V_1} \Big|_{V_2=0} S \\ Y_{22} &= \frac{I_2}{V_2} \Big|_{V_1=0} S \end{aligned} \right\}$$

$$\left. \begin{aligned} \text{Then, } I_1 &= Y_{11} V_1 + Y_{12} V_2 \\ I_2 &= Y_{21} V_1 + Y_{22} V_2 \end{aligned} \right\}$$

The a parameters "Transmission"

$$a_{11} = \frac{V_1}{V_2} \Big|_{I_2=0}, \quad a_{12} = \frac{-V_1}{I_2} \Big|_{V_2=0}$$

$$a_{21} = \frac{I_1}{V_2} \Big|_{I_2=0}, \quad a_{22} = \frac{-I_1}{I_2} \Big|_{V_2=0}$$

$$\left. \begin{aligned} \text{Then, } V_1 &= a_{11} V_2 - a_{12} I_2 \\ I_1 &= a_{21} V_2 - a_{22} I_2 \end{aligned} \right\}$$

The b parameters "Transmission"

$$b_{11} = \frac{V_2}{V_1} \Big|_{I_1=0}, \quad b_{12} = \frac{-V_2}{I_1} \Big|_{V_1=0}$$

$$b_{21} = \frac{I_2}{V_1} \Big|_{I_1=0}, \quad b_{22} = \frac{-I_2}{I_1} \Big|_{V_1=0}$$

$$\left. \begin{aligned} \text{Then, } V_2 &= b_{11} V_1 - b_{12} I_1 \\ I_2 &= b_{21} V_1 - b_{22} I_1 \end{aligned} \right\}$$

The h parameters "hybrid"

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0}, \quad h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0}$$

$$h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0}, \quad h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0} \text{ S}$$

$$\text{Then, } V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

The g parameters "hybrid"

$$g_{11} = \frac{I_1}{V_1} \Big|_{I_2=0} \text{ S}, \quad g_{12} = \frac{I_1}{I_2} \Big|_{V_1=0}$$

$$g_{21} = \frac{V_2}{V_1} \Big|_{I_2=0}, \quad g_{22} = \frac{V_2}{I_2} \Big|_{V_1=0} \Omega$$

See Example 18.2

- What is the relation between the two-port parameters?

You can convert between any parameter to another.

See table 18.1

Solve ~~example~~ 18.3

Reciprocal Two-Port Circuit

The circuit is reciprocal ~~if~~

$$Z_{12} = Z_{21}$$

$$Y_{12} = Y_{21}$$

$$\Delta a = 1$$

$$\Delta b = 1$$

$$h_{12} = -h_{21}$$


$$g_{12} = -g_{21}$$

$$\left. \begin{array}{l} \Delta a = a_{11}a_{22} \\ \quad - a_{12}a_{21} \\ \Delta b = b_{11}b_{22} \\ \quad - b_{12}b_{21} \end{array} \right\}$$

# 18.3

# Analysis of the

# Terminated Two-Port Circuit

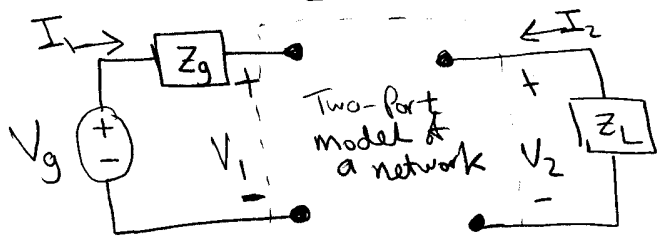

The analysis involves finding the following six characteristics.

1.  $Z_{in} = \frac{V_1}{I_1} \equiv$  the input impedance
2.  $I_2 \equiv$  the output current
3.  $(V_{Th}, Z_{Th}) \equiv$  Thevenin Voltage and Impedance
4.  $\frac{I_2}{I_1} \equiv$  current gain
5.  $\frac{V_2}{V_1} \equiv$  voltage gain
6.  $\frac{V_2}{V_g} \equiv$  voltage gain

## The Z Parameters

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad \text{--- (1)}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \text{--- (2)}$$

$$V_1 = V_g - I_1 Z_g \quad \text{--- (3)}$$

$$V_2 = -I_2 Z_L \quad \text{--- (4)}$$

① The input impedance

To Find the input impedance  $Z_{in} = \frac{V_1}{I_1}$

From (4) and (2)

$$-I_2 Z_L = Z_{21} I_1 + Z_{22} I_2$$

$$\Rightarrow I_2 = \frac{-Z_{21} I_1}{Z_L + Z_{22}} \quad \text{--- (5)}$$

Substitute into (1),

$$V_1 = Z_{11} I_1 + Z_{12} \left( \frac{-Z_{21} I_1}{Z_L + Z_{22}} \right)$$

$$\frac{V_1}{I_1} = Z_{in} = Z_{11} - \frac{Z_{12} Z_{21}}{Z_L + Z_{22}}$$

② The output current

From (3) and (1)

$$V_g - I_1 Z_g = Z_{11} I_1 + Z_{12} I_2$$

$$\infty I_1 = \frac{V_g - Z_{12} I_2}{Z_{11} + Z_g} \quad \text{--- (6)}$$

Substitute into (5)

$$I_2 = \frac{-Z_{21}}{Z_L + Z_{22}} \left( \frac{V_g - Z_{12} I_2}{Z_{11} + Z_g} \right)$$

$$I_2 (Z_L + Z_{22})(Z_{11} + Z_g) = -Z_{21} V_g + Z_{21} Z_{12} I_2$$

$$\infty I_2 = \frac{-Z_{21} V_g}{(Z_L + Z_{22})(Z_{11} + Z_g) - Z_{12} Z_{21}}$$

③ Thevenin Voltage and Impedance

The Thevenin Voltage equals

$V_2$  when  $I_2 = 0$

$$\text{From (2)} \Rightarrow V_2 = Z_{21} I_1 = Z_{21} \frac{V_1}{Z_{11}}$$

$$\text{From (3)} V_1 = V_g - I_1 Z_g$$

$$\text{From (6)} I_1 = \frac{V_g - Z_{12} I_2}{Z_{11} + Z_g}$$

$$\begin{aligned} \infty V_2 &= \frac{Z_{21}}{Z_{11}} \left( \frac{V_g - V_g Z_g}{Z_{11} + Z_g} \right) \\ &= \frac{Z_{21}}{Z_{11}} \left( \frac{Z_{11} V_g + Z_g V_g - V_g Z_g}{Z_{11} + Z_g} \right) \end{aligned}$$

$$V = \frac{Z_{21}}{Z_{11}} V_g$$

The Thevenin impedance is defined as  $\frac{V_2}{I_2}$  when  $V_g$  is shorted.

Thus, From (3)  $V_1 = -I_1 Z_g$

and from (6)  $I_1 = \frac{-Z_{12} I_2}{Z_{11} + Z_g}$

Substitute into (2),

$$V_2 = Z_{21} \left( \frac{-Z_{12} I_2}{Z_{11} + Z_g} \right) + Z_{22} I_2$$

$$\frac{V_2}{I_2} = Z_{22} - \frac{Z_{12} Z_{21}}{Z_{11} + Z_g}$$

(4) The current gain

$$\frac{I_2}{I_1} = \frac{-Z_{21}}{Z_L + Z_{22}}$$

(5) The voltage gain ( $V_2/V_1$ )

From (2) and (4)

$$V_2 = Z_{21} I_1 + Z_{22} \left( \frac{-V_2}{Z_L} \right) \quad (7)$$

From (1) and (4)

$$I_1 = \frac{V_1}{Z_{11}} + \frac{Z_{12} V_2}{Z_{11} Z_L} \quad (8)$$

Solve (7) and (8), we get

$$\begin{aligned} \frac{V_2}{V_1} &= \frac{Z_{21} Z_L}{Z_{11} Z_L + Z_{11} Z_{22} - Z_{12} Z_{21}} \\ &= \frac{Z_{21} Z_L}{Z_{11} Z_L + \Delta Z} \end{aligned}$$

(6) Voltage gain ( $V_2/V_g$ )

Combine (1) and (3)

$$I_1 = \frac{Z_{12} V_2}{Z_L (Z_{11} + Z_g)} + \frac{V_g}{Z_{11} + Z_g} \quad (9)$$

Combine (9) and (4) and (2)

$$\begin{aligned} V_2 &= \frac{Z_{21} Z_{12} V_2}{Z_L (Z_{11} + Z_g)} + \frac{Z_{21} V_g}{Z_{11} + Z_g} \\ &\quad - \frac{Z_{22}}{Z_L} V_2 \end{aligned}$$

$$\Rightarrow \frac{V_2}{V_g} = \frac{Z_{21} Z_L}{(Z_{11} + Z_g)(Z_{22} + Z_L) - Z_{12} Z_{21}}$$

A summary of all equations for the two-port parameters is shown in Table 18.2