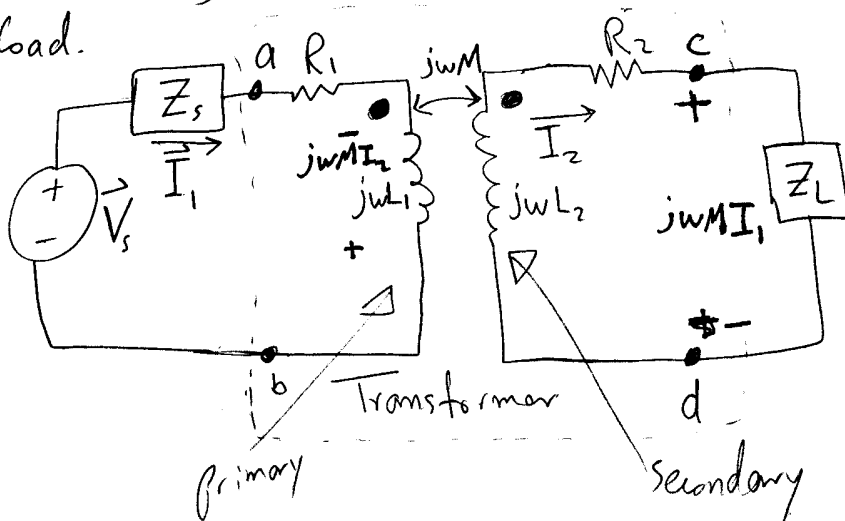


Two Common Types

- 1- Linear transformer  $\Rightarrow$  Communication Circuits  
Block dc signals and Match impedances.
- 2- Ideal transformer  $\Rightarrow$  model ferromagnetic transformers  
in power systems.

9.10 Linear Transformer

The following system use a transformer to connect a source to a load.



$R_1$  = the resistance  
of the primary  
winding.

$R_2$  = the resistance  
of the secondary  
winding.

$L_1$  = self-inductance  
of the primary  
winding.

$L_2$  = self-inductance  
of the secondary  
winding.

$M$  = mutual inductance.

$$\vec{V}_s = \vec{I}_1 Z_s + \vec{I}_1 R_1 + \vec{I}_1 j\omega L_1 - j\omega M I_2$$

$$= (Z_s + R_1 + j\omega L_1) \vec{I}_1 - j\omega M I_2 \rightarrow \textcircled{1}$$

$$0 = -j\omega M I_1 + (R_2 + j\omega L_2 + Z_L) \vec{I}_2 \rightarrow \textcircled{2}$$

Let  $Z_{11} = Z_s + R_1 + j\omega L_1$  and  $Z_{22} = R_2 + j\omega L_2 + Z_L$

Solving the above two equations:

$$\vec{I}_1 = \frac{Z_{22}}{Z_{11}Z_{22} + \omega^2 M^2} \vec{V}_s$$

$$\text{and } \vec{I}_2 = \frac{j\omega M}{Z_{11}Z_{22} + \omega^2 M^2} \vec{V}_s = \frac{j\omega M}{Z_{22}} \vec{I}_1$$

— The impedance seen by the internal source voltage is

$$\frac{V_s}{I_1} = Z_{int} = \frac{Z_{11}Z_{22} + \omega^2 M^2}{Z_{22}} = \underbrace{Z_{11}}_{\text{Primary winding}} + \frac{\omega^2 M^2}{Z_{22}} \underbrace{\text{Secondary winding}}$$

— The impedance at the terminals of the source  
Reflected Impedance

$$Z_{ab} = Z_{int} - Z_s = Z_{11} + \frac{\omega^2 M^2}{Z_{22}} - Z_s = R_1 + j\omega L_1 + \frac{\omega^2 M^2}{(R_2 + j\omega L_2 + Z_L)}$$

— Reflected Impedance

The Third Term in  $Z_{ab}$  is called the reflected impedance.

$$Z_r = \frac{\omega^2 M^2}{\underbrace{(R_2 + j\omega L_2 + Z_L)}_{Z_{22}}} \Rightarrow \text{it shows how the primary side sees the secondary side coil and load impedance.}$$

↑  
Load impedance only appears here.

# Transformer

## ch. 9

P. 3

$$\text{Let } Z_L = R_L + jX_L$$

$$\Rightarrow Z_r = \frac{\omega^2 M^2}{R_2 + R_L + j(\omega L_2 + X_L)}$$

$$= \frac{\omega^2 M^2 [(R_2 + R_L) - j(\omega L_2 + X_L)]}{(R_2 + R_L)^2 + (\omega L_2 + X_L)^2}$$

$$= \frac{\omega^2 M^2}{|Z_{22}|^2} [(R_2 + R_L) - j(\omega L_2 + X_L)]$$


$$= \left( \frac{\omega^2 M^2}{|Z_{22}|^2} \right) Z_{22}^* \quad \text{conjugate}$$

Scalar factor.

Solve Example 9.13

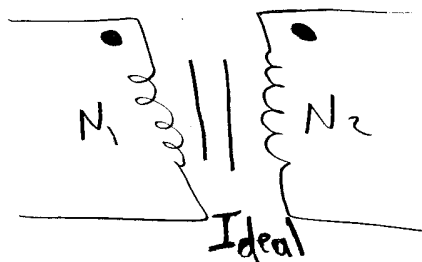9.11 The Ideal TransformerAssumptions:

- ① The coefficient of coupling is unity ( $k=1$ )
- ② The self-inductance of each coil is infinite ( $L_1=L_2=\infty$ )
- ③ The coil losses ~~are~~ are negligible.



The graphic symbol for an ideal transformer.

Note: The core is a magnetic material ||

\* Voltage relation for an ideal transformer

$$\frac{\vec{V}_1}{N_1} = \frac{\vec{V}_2}{N_2}$$

\* Current Relationship for an ideal transformer

$$\vec{I}_1 N_1 = \vec{I}_2 N_2$$

Dot convention for ideal transformers

- If the coil voltages  $\vec{V}_1$  and  $\vec{V}_2$  are both positive or negative at the dot-marked terminal, use a plus sign

$$\text{sign} \Rightarrow \left| \frac{V_1}{N_1} \right| = \left| \frac{V_2}{N_2} \right|$$

otherwise





$$\Rightarrow \left| \frac{V_1}{N_1} \right| = - \left| \frac{V_2}{N_2} \right|$$

- If the coil currents  $\vec{I}_1$  and  $\vec{I}_2$  are both directed into ~~the~~ or out of the dot marked terminal,

use a minus sign  $\Rightarrow |I_1 N_1| = - |I_2 N_2|$


otherwise

$$\Rightarrow |I_1 N_1| = |I_2 N_2|$$

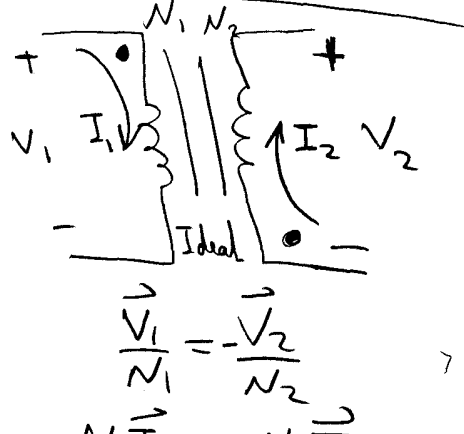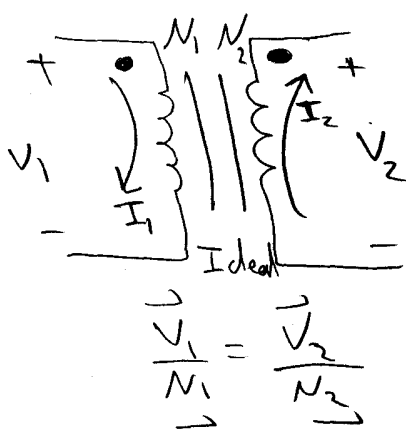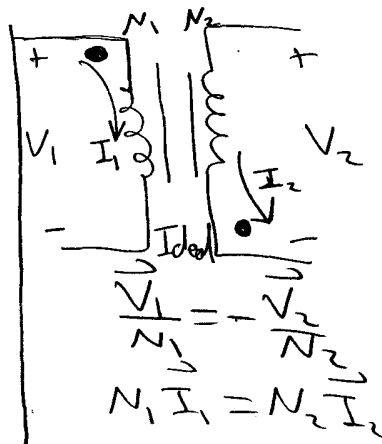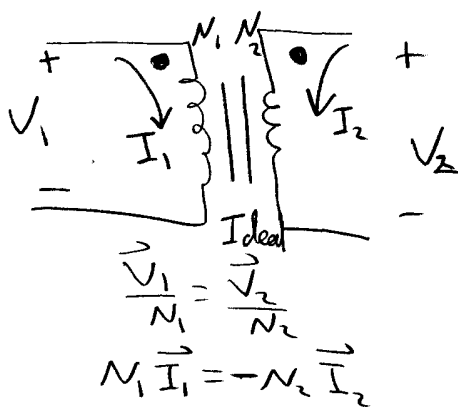


Turn Ratio

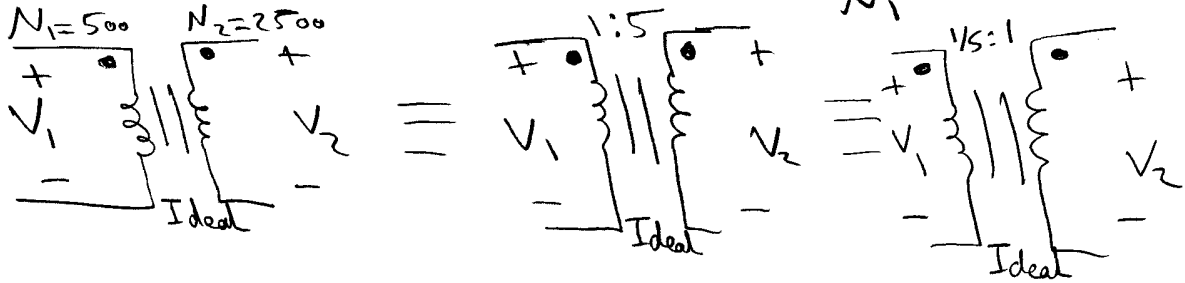The turn ratio is defined as  $a = \frac{N_2}{N_1}$



Solve Example 9.14 in Textbook

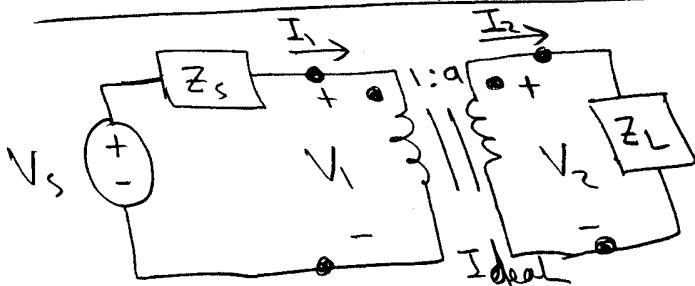What is the Impedance seen by the source?



since  $\vec{V}_1 = \frac{V_2}{a}$   
 and  $\vec{I}_1 = a \vec{I}_2$

$\Rightarrow Z_{in} = \frac{V_1}{I_1} = \frac{1}{a^2} \frac{V_2}{I_2}$

$\Rightarrow Z_{in} = \frac{1}{a^2} Z_L$

impedance seen by the source      load impedance

∴ Ideal transformer can be used for impedance matching  
 1. to lower or raise the impedance level.