

King Fahd University Of Petroleum & Minerals
 Department of Electrical Engineering
2009-2010 First Semester (091)

EE204 – HW # 2

Ser	Name	ID#	SEC#

1. Node-Voltage Method

- 1) Label the four nodes
- 2) Take d as reference node.
- 3) Label the remaining non-reference nodes by voltages.
- 4) express the voltage across every resistor in terms of the node voltages and choose the polarity

- 5) choose the direction of the current in each resistor based on passive sign convention.

- 6) The Voltage source is taken as supernode.

$$V_b - V_a = 1 \quad \dots \quad (1)$$

KCL at node C ::



$$V_C + V_C - V_a = -1$$

$$\therefore 2V_C - V_a = -1 \quad \dots \quad (2)$$

KCL at the supernode

$$V_a + V_b - (V_C - V_a) = 1$$
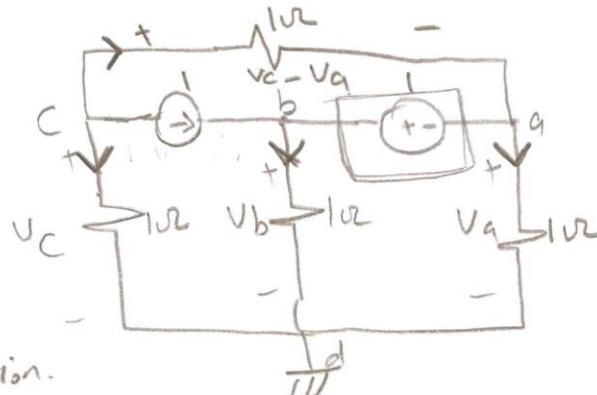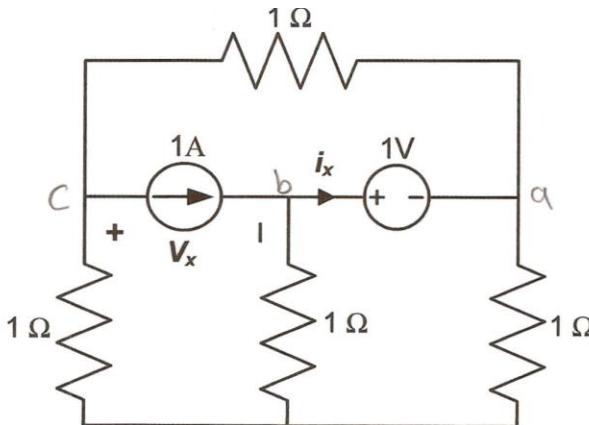
$$\therefore 2V_a + V_b - V_C = 1 \quad \dots \quad (3)$$



from (1) $V_b = 1 + V_a$
 & substitute in (3)

$$2V_a + 1 + V_a - V_c = 1$$

$$3V_a - V_c = 0 \Rightarrow V_c = 3V_a$$

substitute for V_c in (2)

$$6V_a - V_a = -1$$

$$\therefore 5V_a = -1 \Rightarrow V_a = -\frac{1}{5}$$


$$V_c = -\frac{3}{5} V$$

$$V_x = V_c - V_b = -\frac{3}{5} - \frac{1}{5} = -\frac{4}{5} V$$

$$i_x = 1 - V_b = 1 - \frac{4}{5} = \frac{1}{5} A$$

2. Mesh-Current Method:

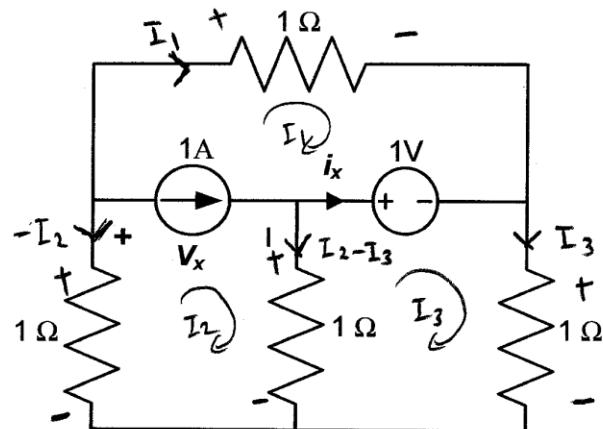- 1) Define the mesh currents
- 2) Choose a direction for the current in each resistor
- 3) Write the total current through each resistor.
- 4) Label the voltage across each resistor according to the passive sign convention



$$I_2 - I_1 = 1 \quad \text{--- (1)}$$

KVL for mesh current 3 (M3)

$$I_3 - (I_2 - I_3) = -1$$

$$2I_3 - I_2 = -1 \quad \text{--- (2)}$$

KVL for (M1 + M2) :-

$$(I_2 - I_3) - (-I_2) + I_1 = 1$$

$$2I_2 - I_3 + I_1 = 1 \quad \text{--- (3)}$$

from (1) $I_1 = I_2 - 1$

Substitute in (3)

$$2I_2 - I_3 + I_2 - 1 = 1$$

$$3I_2 - I_3 = 2 \quad \text{--- *}$$

from (2)

$$I_2 = 2I_3 + 1$$

Substitute in *

$$3(2I_3 + 1) - I_3 = 2$$

$$6I_3 + 3 - I_3 = 2$$

$$5I_3 = -1 \Rightarrow I_3 = -\frac{1}{5} \text{ A}$$

$$I_2 = -\frac{2}{5} + 1 \Rightarrow I_2 = \frac{3}{5} \text{ A}$$

$$I_1 = I_2 - 1 \Rightarrow I_1 = -\frac{2}{5} \text{ A}$$

$$\begin{aligned} \therefore V_x &= I_3 - I_1 \\ &= -\frac{1}{5} + \frac{2}{5} = \frac{1}{5} \text{ A} \end{aligned}$$

$$V_x + (I_2 - I_3) - (-I_2) = 0$$

$$V_x + 2I_2 - I_3 = 0 \Rightarrow V_x = I_3 - 2I_2$$

$$\therefore V_x = -\frac{1}{5} - \frac{6}{5} = -\frac{7}{5}$$

The power absorbed by $\text{top } 1\Omega$ resistor in the top 2Ω .

$$P = I_1^2 R = \left(-\frac{2}{5}\right)^2 (1) = \frac{4}{25} \text{ Watt} \quad (\text{from method 2})$$

Or from method 1,

$$P = \frac{(V_c - V_a)^2}{R} = \frac{\left(-\frac{3}{5} + \frac{1}{5}\right)^2}{1} = \left(-\frac{2}{5}\right)^2 = \frac{4}{25} \text{ Watt.}$$