

King Fahd University of Petroleum & Minerals
Electrical Engineering Department
EE-407; Exam-1(062); 31st of March, 2007

Prob.1	Prob.2	Prob.3	Total


Answer **ALL THE** questions. All questions carry **equal** marks.

Name:


I.D.

Q.1(a) Calculate the phase constant of a lossless line with a high dielectric constant, capacitance per unit length of 45 pF/m and a characteristic impedance of 50Ω. Assume the line is operating at 1 GHz.

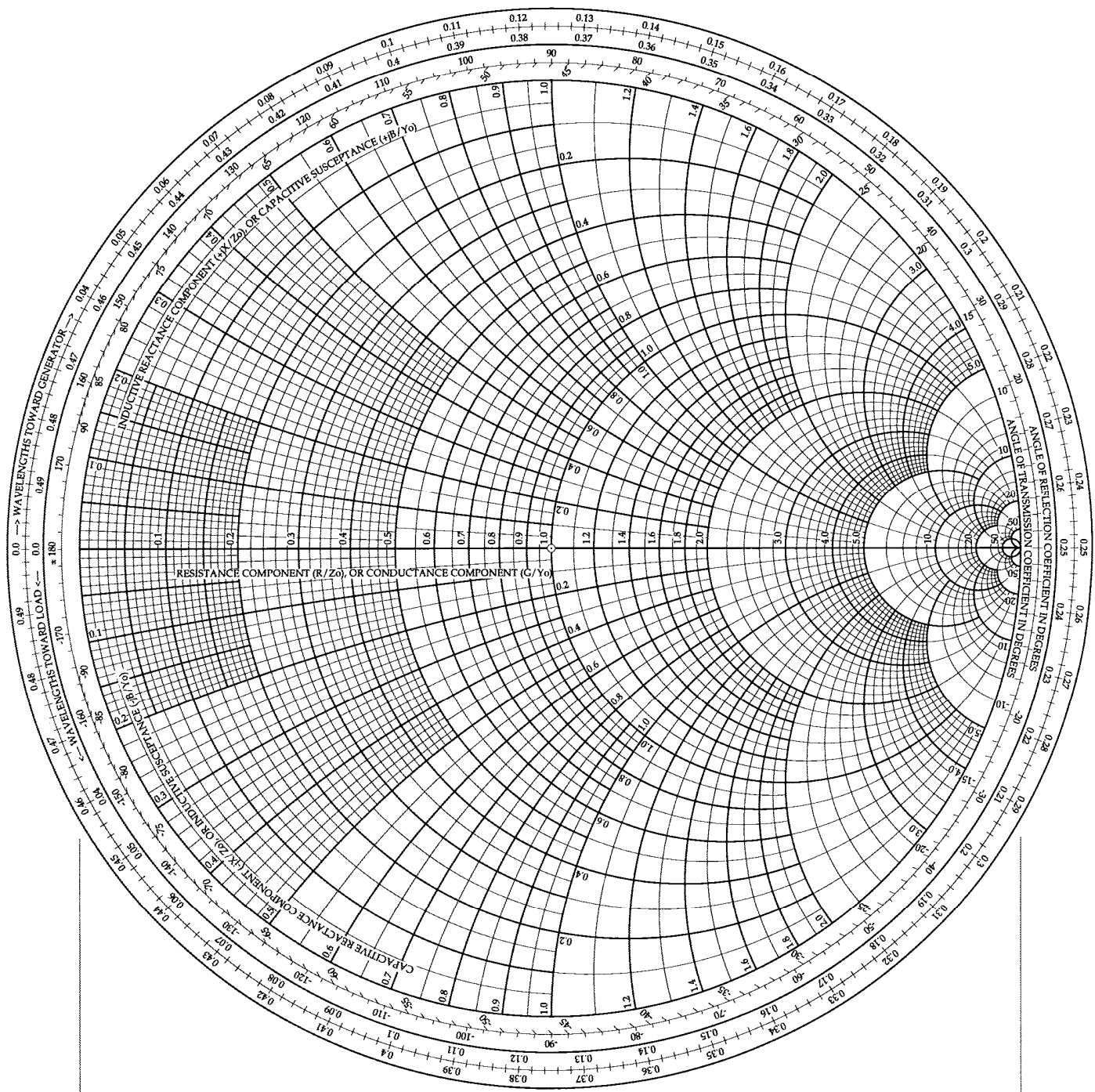Q.1(b) A load impedance of $Z_L=80+j20 \Omega$ is to be matched to a $Z_0=100\Omega$ transmission line using a matching section. **Find the required values** (' l ' and ' $\pm jX$ ') of the matching section. Finally **draw the circuit** to show the line, load and the matching section (**use the given Smith Chart of next page**)



RADIALLY SCALED PARAMETERS

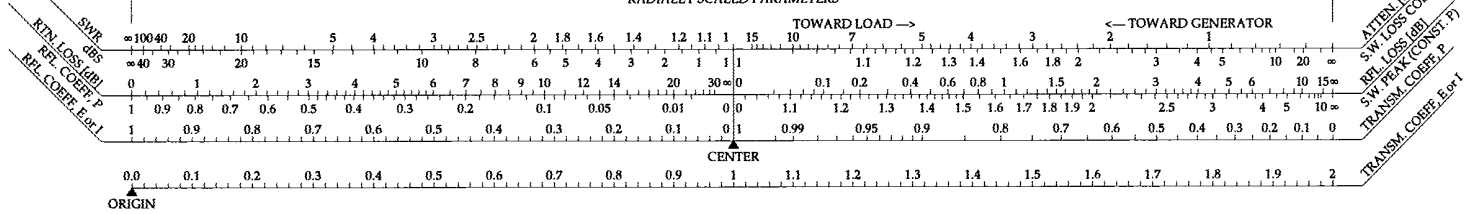

Q.2


A loss-less transmission line is 0.4λ long, has a characteristic impedance of 50Ω and is terminated in a load of $60+j35\Omega$. The transmission line is supplied by a matched source of $V_s=100\angle 0^\circ$. Without using the smith-chart,

- (i) Find the load reflection coefficient.
- (ii) Find the input reflection coefficient.
- (iii) Find the VSWR on the line.
- (iv) If the line becomes lossy, what equation will be used to find Input impedance?


Q.3

A loss-less transmission line of length '52 mm' and characteristic impedance of $Z_0=100\Omega$ is terminated in a load impedance of $Z_L=30+j50\Omega$. If $\lambda=\lambda_0$ and the propagating signal frequency, $f=0.75$ GHz, then use **smith-chart** to calculate;

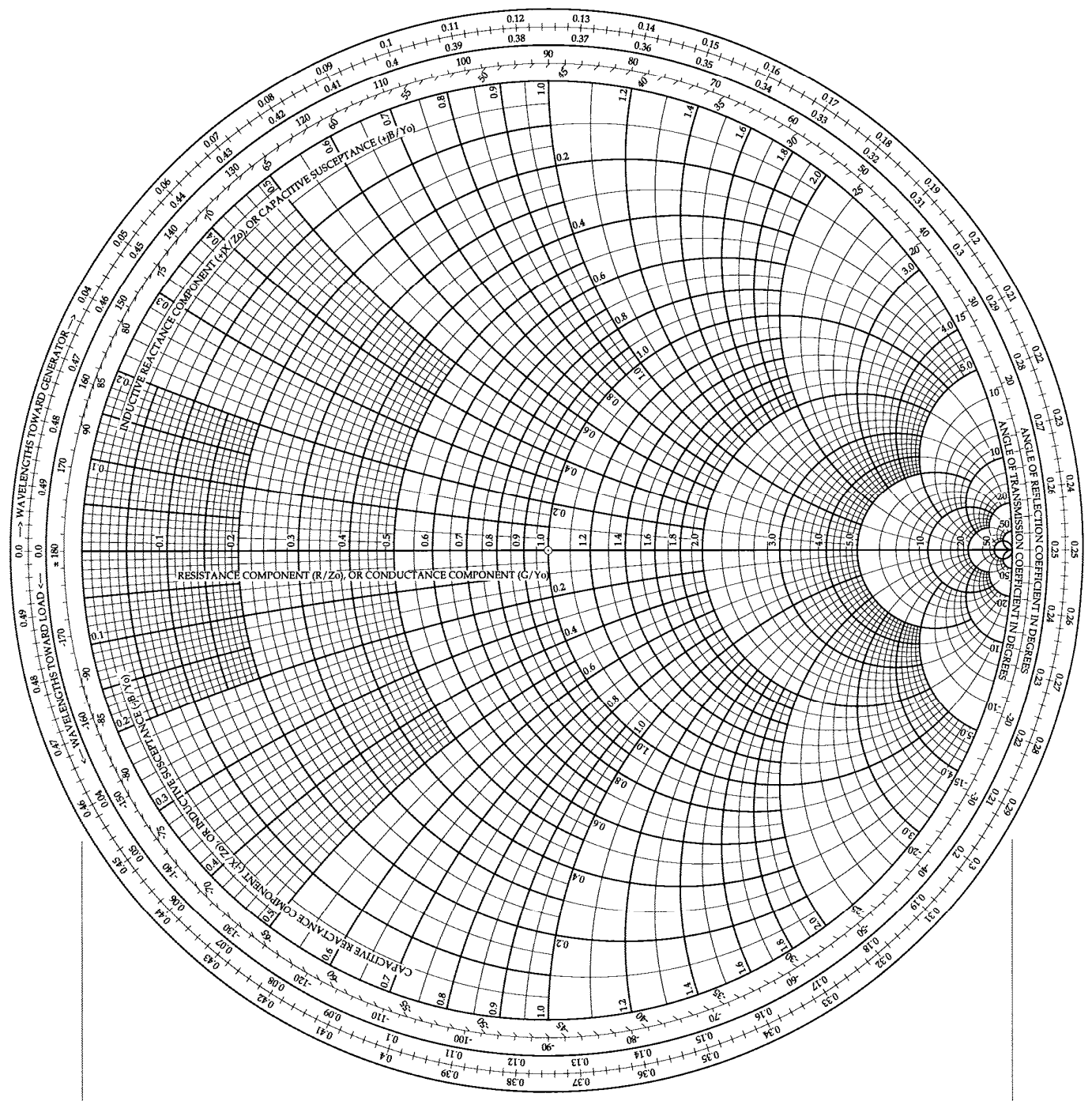- (i) the **load reflection coefficient** of the transmission line.
- (ii) the **VSWR** along the transmission line.
- (iii) the ' **Y_{in}** ' at '52 mm' away from the load.



RADIALLY SCALED PARAMETERS

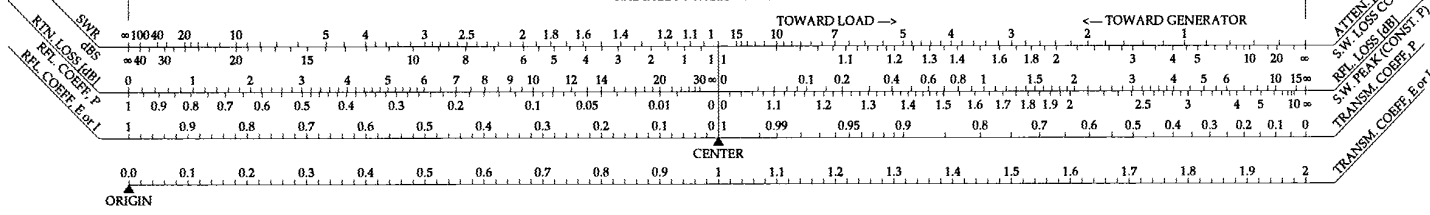

ORIGIN

CENTER