

**King Fahd University of Petroleum & Minerals**  
**Electrical Engineering Department**  
**EE-407; Exam-2**

Prob.1	Prob.2	Prob.3	Total

Answer **all THREE** question. All questions carry **equal** marks.

---

**Name:**

*I.D.*

---

**Q.1** Design a 0.5dB equal-ripple low-pass filter (where circuit begins with shunt element) with  $Z_0=50 \Omega$ , pass-band of 0 to 3 GHz and a minimum attenuation of 20 dB at 4.5 GHz.

(i) Draw the LC filter circuit


(ii) Find the values of the reactive elements (**with units**) of the filter.

**Q.2** Implement the filter solved in question 1 , using **stepped impedance method**, where the given printed board material has  $\epsilon_r=4.2$ ,  $h=0.79$  mm and negligible thickness of the copper conductor. Assume the filter has highest practical line impedance is  $120 \Omega$ , lowest practical line impedance is  $15 \Omega$ .

- (i) Find the electrical length (in degrees) of the microstrip segments realizing reactive elements of the filter.
- (ii) Find the width (in mm) of the microstrip segments realizing reactive elements of the filter.

**Q.3(a)** Draw a three finger lunge coupler and write one advantage of this coupler?

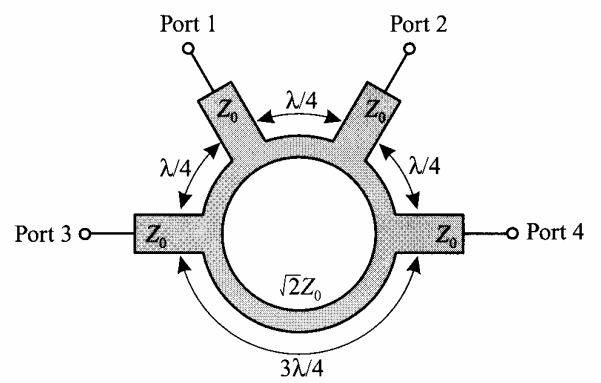**Q.3(b)** For the given hybrid-ring coupler, briefly explain, why  $\sqrt{2}Z_0$  is selected as the characteristics impedance of the circular section.



**Q.3(c)** For a four port **20 dB coupler** with **30 dB directivity**, find the **isolation** (in dB) if the input power of the coupler is 5 mW. Assume all ports are matched or connected with proper matching.

**Q.3(d)** If the coupler of question 3(c) is implemented in on a substrate with dielectric constant of '2.2' and thickness of '0.127 cm', find the required width of the microstrip sections to implement a '50  $\Omega$ ' device. Neglect the thickness of the copper conductor.

$$\left\{ \begin{array}{l} \text{Given:} \\ \epsilon_0 = 8.854e-12 \text{ unit} \\ \mu_0 = 1.2566e-6 \text{ unit} \end{array} \right.$$