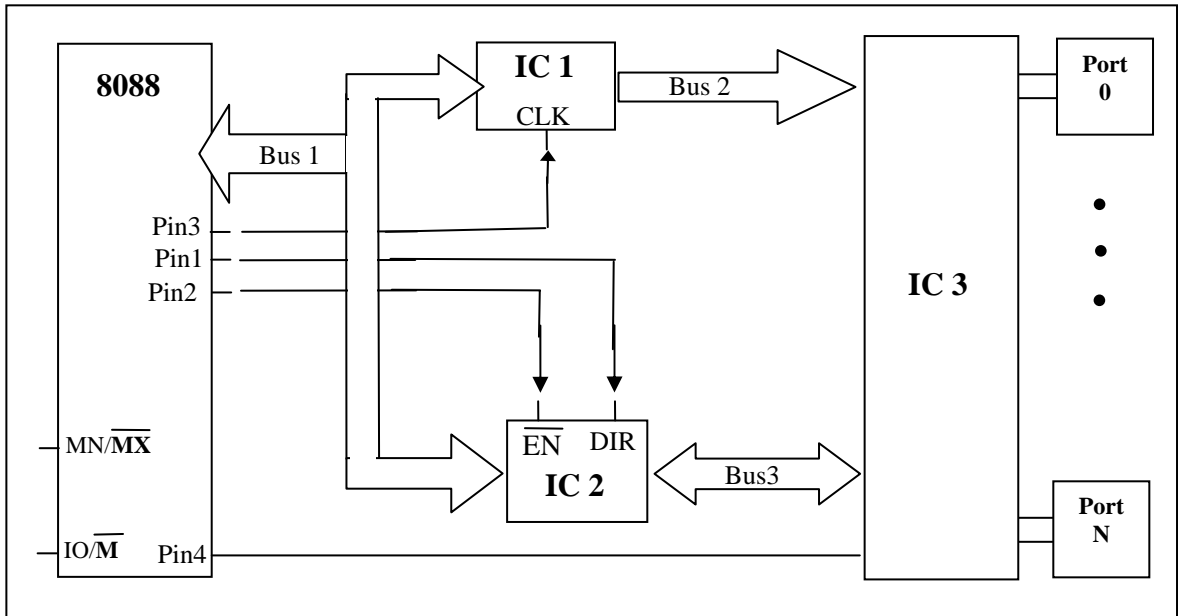


**Short Quiz - 5**  
**EE-390 1**  
**Set A**

Name: \_\_\_\_\_

ID No: \_\_\_\_\_

(1) In the given figure **8088** is performing a **Input-Output read** operation.  
 Answer the following questions:



Write approximate steps required during the bus-cycle to complete this operation:  
 (use proper names associated with Pin-1 to Pin-4, IC-1 to IC-3 and BUS-1 to 3)

Step 1: \_\_\_\_\_

Step 2: \_\_\_\_\_

---



---



---



---



---



---



---



---