Handout 2 for EE-203

Bipolar Junction Transistor (BJT)

Sheikh Sharif Iqbal

(Ref: Text book and KFUPM Online course of EE-203)

(Remember to solve all the related examples, exercises problems as given in the Syllabus)

Chapter 5: Bipolar Junction Transistor (BJT)

<u>**Text book</u>**: "Microelectronic Circuits by Sedra and Smith</u>

5.1: Device Structure and Physical Operation

- BJT is a three terminal device that can operate as "Amplifier" or as "Switch"
- Voltage between the two terminals is used to control the current in the third terminal
- BJT consist of three semiconductor regions: NPN or PNP



Active Mode of Operation of an NPN transistor:

<u>N-Type material</u>: Arsenic, Antimony and Phosphorus (group V materials)

<u>P-Type material</u>: Aluminum, Boron and Gallium (group III materials)



Fig 5.3: Forward current flow in an *NPN* transistor biased to operate in the active mode (Very small reverse current, due to drift of thermally generated minority carriers, are not shown.)

- The EMITTER is heavily doped and have high density of electrons. But the base is thin, lightly doped and has low density of holes. So, the current flow (i_E) between the forward biased emitter-base junction is mainly due to electronics flowing from emitter to base. This process emits free electrons into the base.
- Among the emitted electrons in BASE, around 5% <u>recombines</u> with available holes and escapes into external base lead as i_{B2} , $(i_B=i_{B1}+i_{B2} \Rightarrow i_{B1}$ is due to majority holes) Remaining 95% base electrons acts as a minority carriers and are swept away to collector region by the electric field of reverse biased collector-base junc. (fig)
- These electrons are then collected by more positive collector terminal that constitute collector current (i_c). THUS: (i_E) = (i_B) + (i_C)



$$\frac{\text{The Collector Current}}{i_{C} = I_{S} \cdot e^{\frac{V_{BE}}{V_{T}}}} \begin{cases} \frac{Base Current}{I_{S}}(i_{B}): \\ i_{B} = \frac{i_{C}}{\beta} = \frac{I_{S}}{\beta} \cdot e^{\frac{V_{BE}}{V_{T}}} \end{cases} \begin{cases} \frac{Emitter Current}{I_{E}}(i_{E}) \\ i_{B} = \frac{i_{C}}{\beta} = \frac{I_{S}}{\beta} \cdot e^{\frac{V_{BE}}{V_{T}}} \end{cases} \end{cases}$$

• Here, n = 1; Saturation current, $10^{-12} > I_S > 10^{-14} A$ <u>and</u> thermal voltage, $V_T = 25 \text{ mV}$

- Note that 'i_C' is independent of V_{CB} , for $V_{CB} \ge 0$. So collector behaves as an ideal constant current source where the current is determined by V_{BE} . (fig 2nd slide)
- Since, $i_C = \alpha i_E$; $i_C = \beta i_B$ and $\alpha = \beta/(\beta+1)$, where " β " is common emitter current gain constant for a particular BJT " α " is common base current gain
- So the Emitter Current is given by:

$$i_{\rm E} = i_{\rm C} + i_{\rm B} = \frac{\beta + 1}{\beta} \cdot i_{\rm C} = \frac{\beta + 1}{\beta} \cdot \left(I_{\rm S} \cdot e^{\frac{V_{\rm BE}}{V_{\rm T}}} \right)$$

Exercise BJT-1: For an NPN transistor having $I_s = 10^{-11} A$, $\beta = 100 \& V_T = 25 m V_{(at room temperature)}$ Calculate V_{BE} for $i_C = 1.5A$ (Solution: 0.643 V)





Note that the PNP transistors have V_{EB} ; whereas the NPN transistors has V_{BE}





5.2.3: Dependence of current, voltage, temperature and the Early Effect:

- The collector current ic without the early voltage effect is given by $i_C = I_S e^{v_{BE}/V_T}$ Increase in VCE causes the base width to decrease due to increased reverse biasing on
- collector-base junction.
- Since IS is inversely proportional to the base width, it increases with the decrease in base width.
- i_C is directly proportinal to Is and therefore increase in Is also increases the collector current. This is called early voltage effect and the new equation for i_C is given by

$$i_{C} = I_{S} e^{v_{BE}/V_{T}} \left(1 + \frac{v_{CE}}{V_{A}}\right) \qquad I_{S} = \frac{A_{E} q D_{n} n_{i}^{2}}{N_{A} W}$$

Therefore the output resistance seen into the collector is defined and is given by

 $r_{\mathcal{O}} = \left[\frac{\partial i_{\mathcal{C}}}{\partial v_{\mathcal{C}E}}\right] v_{BE} = \text{constant} = r_{\mathcal{O}} \approx \frac{\mathbf{V}_{\mathcal{A}}}{\mathbf{I}_{\mathcal{C}}} \qquad \frac{\text{Exercise BJT-2: If a BJT has}}{\mathbf{V}_{A} = 100 \text{v and } \mathbf{I}_{C} = 1 \text{mA, find } \mathbf{r}_{0}}$



5.3.3: <u>Q-point/Biasing point:</u> Location of biasing point affects maximum allowable signal swing

5.4: How to solve NPN or PNP BJT-DC circuits

- If not specified, assume that the transistor is working in active mode.
- Use the simple constant-V_{BE} model that is used for diode, i.e. take V_{BE}=0.7V for forward biased base-emitter junction.
- Analyze the circuit using current-voltage relationships for active mode operation.
- Check if the initial assumption of active mode operation was correct by verifying that the base-collector junction is reverse biased.
- If the active mode assumption was wrong than use the saturation mode current-voltage relationships for analysis.









Find the bias point detail of the following npn circuit, take $\beta = 100$



5.5: Biasing single stage BJT Amplifiers: - Operating point or Q-point (i_c and v_{ce})

Find the dc bias point (operating point) of the following circuit



Find the bias point detail of the following npn circuit, take $\beta = 100$



Design pnp BJT circuit such that VEC = 2.5V. Take $\beta = 60$

Applying KVL around the emitter collector loop Vcc = IERE + VEC => IE = 1.25mA IC = $\frac{\beta}{\beta + 1}$ IE = α IE = 1.23mA IB = $\frac{IC}{\beta}$ = 20.5 μ A Applying KVL around the emitter base loop Vcc = IERE + VEB + IBRB + VBB => RB = 190k Ω





For the collector feedback circuit, the BJT used is specified to have β values in the range of 20 to 200. For the two extreme values of β (β =20 and β =200) find I_E, V_E and V_B.

(Hint : Apply KVL in the loop starting from V_{CC} to R_F to V_{BE} to R_E to ground)



5.6: BJT Amplifiers, Small-Signal Operation and Models :

- In linear amplifier the output signal is equal to the input signal multiplied by a constant. The value of this constant is usually greater than unity.
- **To operate as an amplifier, the transistor must be biased in the active mode.**
- The biasing problem is that of establishing a proper value of constant dc current in the emitter or collector of transistor.
- The operation of transistor as an amplifier is highly influenced by the value of the bias current also called operating point



| Variable | Meaning |
|---|----------------------------|
| $\mathbf{I}_{\mathrm{C}}, \mathbf{V}_{\mathrm{CE}}$ | DC values |
| i _c , v _{ce} | Instantaneous ac values |
| <i>i</i> _C , <i>v</i> _{CE} | Total instantaneous values |

DC Analysis $I_{C} = I_{S} e^{V_{BE}/V_{T}} \qquad I_{E} = \frac{I_{C}}{\alpha}$ $I_{B} = \frac{I_{C}}{\beta} \qquad V_{C} = V_{CE} = V_{CC} - I_{C}R_{C}$

$$\begin{array}{c} \mathbf{v}_{BE} = \mathbf{I}_{\mathbf{E}} + \mathbf{i}_{\mathbf{c}} \\ \mathbf{v}_{BE} = \mathbf{I}_{\mathbf{E}} + \mathbf{i}_{\mathbf{c}} \\ \mathbf{v}_{BE} = \mathbf{I}_{\mathbf{E}} + \mathbf{i}_{\mathbf{c}} \\ \mathbf{v}_{BE} = \mathbf{I}_{\mathbf{E}} + \mathbf{i}_{\mathbf{E}} \\ \mathbf{v}_{E} = \mathbf{I}_{\mathbf{E}} +$$

5.6.6 and 5.6.7: Small-Signal Equivalent Circuit Models:



Two different versions of simplified <u>hybrid-Π model</u> for the small-signal operation of the BJT.
(a) represents the BJT as a voltage-controlled current source (a transconductance amplifier)
(b) represents the BJT as a current-controlled current source (a current amplifier).



Two slightly different versions of what is known as the <u>**T** model</u> of the BJT. The circuit in (**a**) is a voltage-controlled current source representation and that in (**b**) is a current-controlled current source representation. These models explicitly show the emitter resistance r_e rather than the base resistance r_{II} featured in the hybrid- π model.

Solve example 5.14

5.7.3:Common emitter Amplifier: DC analysis to find I_B , I_C , I_E , V_B , V_C and V_E



Lets assume the BJT is operating in Active Mode. Thus, $I_C = \alpha . I_E$, $I_C = \beta . I_B$ and $\alpha = \beta/(\beta+1)$ Since $I_E = I \text{ mA}$; $I_B = I_E/(\beta+1) \text{ mA}$; $V_B = 0 - I_B . R_B$; $V_E = V_B - 0.7$; Now $I_C = \alpha . I_E = (\beta . I_E)/(\beta+1)$; $V_C = V_{CC} - I_C . R_C$ and if <u>CBJ remains RB</u> then assumption is <u>OK</u>

Exercise-5: Find the <u>operating point</u> if $V_{CC}=V_{EE}=10V$, $R_C=8 \text{ k}\Omega$, $R_B=100 \text{ k}\Omega$, I=1mA & $\beta=100$ **Solution:** Q or operating point is, $I_C=0.99 \text{ mA}$; $V_{CE}=0.3 \text{ v}$ (as $V_B=-1v$, $V_C=2v$, $V_E=-1.7v$)

5.7.3:Common emitter Amplifier: AC analysis to find Gain, Input & output Impedances

 $R_C \lessapprox C_{C2}$ SYC 0 Vo $\begin{array}{c} + \\ + \\ - \\ \end{array} v_{\text{sig}} \end{array} \begin{vmatrix} + \\ + \\ v_i \\ - \\ \end{vmatrix} R_B \Biggr{} R_B \Biggr{} R_{ib}$ $\bigvee_{g_m v_\pi}$ C_{C1} $R_{\rm sig}$ SCFigure from text book AC analysis: short circuit capacitors. GND all DC voltage sources and ID/C all DC current sources The voltage gain, $A_v = \frac{v_o}{v_i} = -g_m(r_o \parallel R_C \parallel R_L)$ The output resistance, $R = P^{-11}$ since $v_{\pi} = v_i$ and $v_o = -g_m v_{\pi}(r_o \parallel R_C \parallel R_L)$ The output resistance, $R_{out} = R_C \parallel r_o$ overall voltage gain, $G_v = -\frac{(R_B \parallel r_\pi)}{(R_B \parallel r_\pi) + R_{sig}} g_m(r_o \parallel R_C \parallel R_L)$ For $R_B \gg r_{\pi}$, $G_v \cong -\frac{\beta(R_C \parallel R_L \parallel r_o)}{r_{\pi} + R_{\text{sig}}}$ as $G_v = A_v * \frac{v_i}{v_{\text{sig}}}$ <u>Exercise-6</u>: Find R_{in} , R_{out} , $A_v \& G_v$; if $R_{sig} = R_L = 5k\Omega$, $R_B = 100k$, $R_C = 8k$; $I_C = 1mA$, $I_B = 0.01mA$, $V_A = 100V$, $V_T = 25mV$ **Solution:** $R_i = 2.43 \text{ k}\Omega$; $R_{out} = 7.4 \text{ k}\Omega$, $A_v = -119 \text{ V/V}$, $G_v = -39 \text{ V/V}$ (as $r_{\pi} = 2.5K$, $g_m = 40 \text{ mA/V}$, $r_0 = 100k$)



The transistor shown has $\beta=100$ and $V_A=100V$.

 (a) Find the dc voltages at the base, emitter, and collector.

(b) Find g_m , r_{π} , and r_{\circ} .

(c) Draw the small signal equivalent circuit using hybrid- π model (with r_{\circ}) and find the voltage gain

(d) Neglect r_{o} and again find the voltage gain and find the percentage error between (c) and (d).



<u>Hint</u>: When performing dc analysis open circuit all the capacitors. Notice that IE=I=1mA. When performing small signal analysis short circuit all the capacitors and open circuit the dc current source I.

Answer: (a) -0.1V, -0.8V, +2V (b) 40mA/V, 2.5kΩ, 100kΩ (c) -77 (d) -80 +3.9%



5.7.4:Common emitter Amplifier with R_e (emitter resistor): Controlled voltage amp



Exercise-9: Find the <u>operating point</u> if $V_{CC}=V_{EE}=10V$, $R_C=8 k\Omega$, $R_B=100 k\Omega$, $I=1mA \& \beta=100$ Solution: operating point, $I_C=0.99 mA$; $V_{CE}=3.7 v$ (as $I_E=1mA$; $V_B=-1v$, $V_C=2v$, $V_E=-1.7v$)



The amplifier input resistance, $R_{in} = R_B \parallel R_{ib}$ - input resistance at the base, $R_{ib} \equiv \frac{v_i}{i_b}$, where $i_b = \frac{i_e}{\beta + 1}$, and $v_i = i_e (r_e + R_e)$ Thus, $R_{ib} = (\beta + 1)(r_e + R_e)$, **Remember**, $r_e = V_T / I_E$ & Resistance reflection rule $\Rightarrow R_{base} \approx (\beta + 1)R_{emitter}$ - input resistance looking into base is $(\beta + 1)$ times the total resistance in emitter.

Thus,
$$\frac{R_{ib} \text{ (with } R_e \text{ included)}}{R_{ib} \text{ (without } R_e)} = \frac{(\beta+1)(r_e+R_e)}{(\beta+1)r_e} = 1 + \frac{R_e}{r_e} \cong 1 + g_m R_e \quad \text{; Remember, } g_m = I_c/V_T$$

The output resistance $R_{out} = R_C$ (as r_o of T-model is neglected to ease solution process)

5.7.3:Common Emitter (CE) with Emitter Resistance (R_e): AC analysis (cont'd...)

The voltage gain
$$A_v \equiv \frac{v_o}{v_i} = \frac{-i_c(R_c \parallel R_L)}{i_e(r_e + R_e)} = -\frac{\alpha i_e(R_c \parallel R_L)}{i_e(r_e + R_e)} = -\frac{\alpha (R_c \parallel R_L)}{r_e + R_e}$$

 $A_v \cong -\frac{R_c \parallel R_L}{r_e + R_e}$, if $\alpha \cong 1$
The current gain $A_{is} = \frac{i_{os}}{i_i} = \frac{-\alpha i_e}{v_i/R_{in}} = -\frac{\alpha R_{in} i_e}{v_i} = -\frac{\alpha (R_B \parallel R_{ib})}{r_e + R_e}$

$$A_{is} = -\beta$$
, if $R_B \gg R_{ib}$, $\alpha \equiv 1$ and $R_{ib} = (\beta + 1)(r_e + R_e)$

The overall voltage gain
$$G_v = \frac{v_i}{v_{sig}} \cdot A_v = -\frac{R_{in}}{R_{sig} + R_{in}} \frac{\alpha(R_C \parallel R_L)}{r_e + R_e}$$

The resistance R_e in the emitter introduce a negative feedback \rightarrow see pg 474

- 1. The input resistance R_{ib} is increased by the factor $(1 + g_m R_e)$.
- 2. The voltage gain from base to collector, A_v , is reduced by factor $(1 + g_m R_e)$.
- 3. For the same nonlinear distortion, the input signal v_i can be increased by the factor $(1 + g_m R_e)$.
- 4. The overall voltage gain is less dependent on the value of β .

Exercise-10: if $I_E = 1$ mA, $I_C = 0.99$ mA, $R_e = 225\Omega$, $R_B = 100$ k Ω , $R_C = 8$ k Ω , $R_{sig} = R_L = 5$ k Ω , $\beta = 100$, $V_T = 25$ mV,

Neglect r_o to FIND R_{in} , R_{out} , A_{v} , $G_v \rightarrow Sol$: $R_i=20.16 \text{ k}\Omega$; $R_{out}=8 \text{ k}\Omega$, $A_v=-12.18 \text{ V/V}$, $G_v=-9.76 \text{ v/v}$

5.7.5:Common Base (CB) Amplifier: Unity-gain-current-amplifier or Current-buffer



AC analysis: For the AC equivalent circuit given in the figure in the next page,

The input resistance $R_{in} = r_e$ and output resistance $R_{out} = R_C$ (with r_o neglected) The low R_{in} cause the input signal to be severely attenuated,

as
$$\frac{v_i}{v_{\text{sig}}} = \frac{R_i}{R_{\text{sig}} + R_i} = \frac{r_e}{R_{\text{sig}} + r_e}$$



Finally, a very significant application of the CB circuit is as a unitygain current amplifier or **current buffer:** It accepts an input

5.7.5:Common Base (CB) Amplifier: Low Zin makes it not good voltage amplifier

Exercise-11: Determine the voltage gain of the circuit given in figure (a)



Hints: Draw the DC and AC (using T-model) equivalent circuits (as shown in figure) The DC solutions are also shown in figure (b). Calculated $\Rightarrow r_e = 27 \Omega$ The Gain of the circuit, calculated from figure (c) is, $A_v = v_o/v_i = 183.3 \text{ V/V}$

5.7.5:Common Collector (CC) Amplifier: Emitter Follower





Consider the CB amplifier shown in the figure. To what value must current source 'T' be set in order that the input resistance at emitter 'Ri' is equal to that of the source (namely 50 Ω)? What is the resulting voltage gain from the source to the load? Assume $\alpha=1$ and neglect early voltage effect.

<u>Hint</u>: Since $\alpha = 1$, therefore IE=IC=I. Using T-model, its easy to see that $R_i = r_e$. Find $r_e v_s$ in terms of I and put it equal to 50 to find I. Find the voltage gain $Av = v_a / v_s$ from the T-model. Answer: I = 0.5mA ; Av = 50



 $\frac{1}{\sqrt{1}}$ **Exercises-12**

C,

 $R_1 \lesssim 10 k\Omega$

Vcc=10V

 $R_C \gtrsim 10 k\Omega$

Rs

50Ω

C,

R.



5.143 and 5.141 \rightarrow Due on next week



Simulation Examples using the Spice software:

