

EE 407
Microwave Engineering

Lecture 3 & 4

Transmission line
characteristics


Dr. Sheikh Sharif Iqbal

References: Text books and Agilent notes


Behavior of basic Transmission media:

- At low frequencies: TL is considered to be a short wire with a negligible distributed resistance, represented as **lumped** for the purpose of analysis.

$$V_1 = V_2 + IR$$

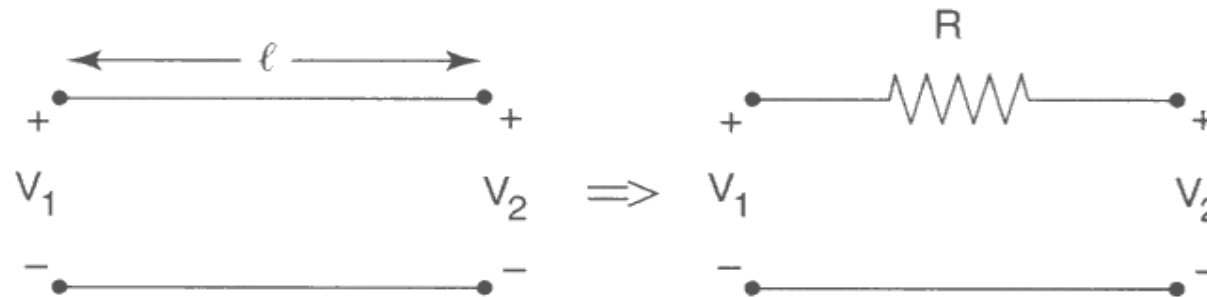

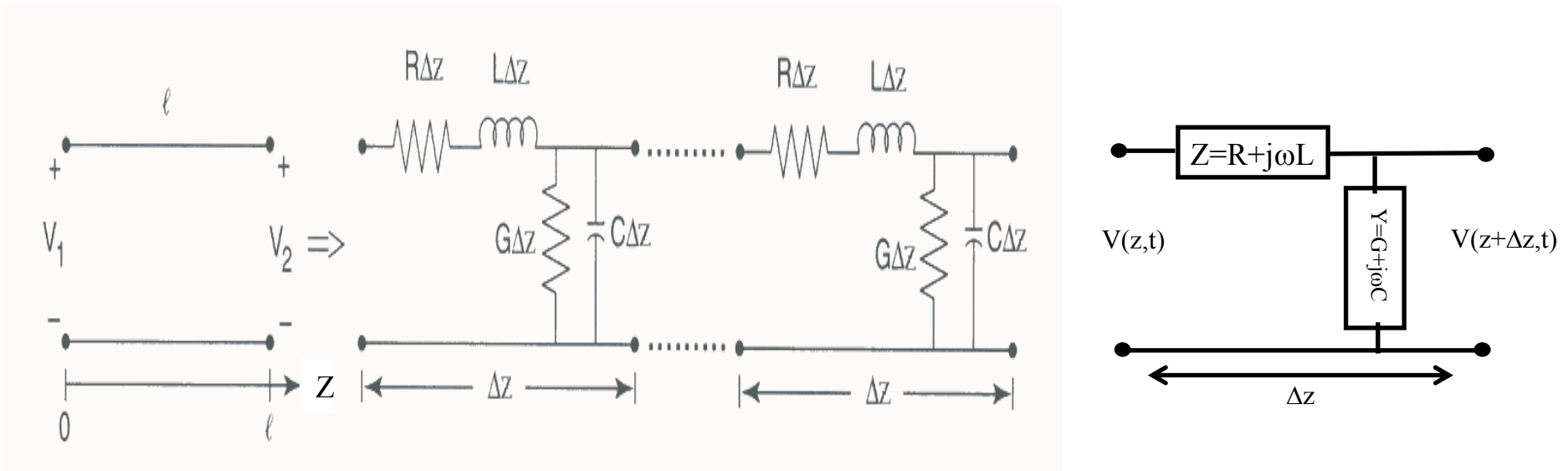- At high frequencies: analyzed by **M.E's** or **distributed** circuit model;



- $\mathbf{dV/dz = -ZI}$ and $\mathbf{dI/dz = -YV}$; where 'Z' & 'Y' are function of frequency

- Here, 'Z' & 'Y' are function of frequency only and $\Delta Z \rightarrow 0$;

$$\mathbf{dV/dz} = -\mathbf{Z I} \quad (\text{eq. 1})$$

$$\mathbf{dI/dz} = -\mathbf{Y V} ;$$

- Differentiating again gives: {as $Z \rightarrow Z(f)$ }

$$\mathbf{d^2V/dz^2} = -\mathbf{Z. dI/dz} = \mathbf{ZYV} \quad (\text{eq. 2})$$

$$\mathbf{d^2I/dz^2} = -\mathbf{Y.dV/dz} = \mathbf{YZI}$$

- If no reflected wave is present;

$$\mathbf{V} = \mathbf{V(z,t)} = \mathbf{V_0^+ e^{j\omega t - \gamma z}} \quad \text{and} \quad \mathbf{V^+} = \mathbf{V(z)} = \mathbf{V_0^+ e^{-\gamma z}} \quad (\text{eq. 3})$$

$$\mathbf{I} = \mathbf{I(z,t)} = \mathbf{I_0^+ e^{j\omega t - \gamma z}} \quad \text{and} \quad \mathbf{I^+} = \mathbf{I(z)} = \mathbf{I_0^+ e^{-\gamma z}}$$

- Substitute $V(z,t)$ and $I(z,t)$ into eq.2 and differentiating yields:

$$\gamma^2 \mathbf{V_0^+ e^{j\omega t - \gamma z}} = \mathbf{Z Y V_0^+ e^{j\omega t - \gamma z}} \quad (\text{eq. 4})$$

$$\gamma = \pm \sqrt{\mathbf{ZY}}$$

$$\gamma = \pm \sqrt{(\mathbf{R+j\omega L})(\mathbf{G+j\omega C})} \Rightarrow \text{called Propagation Constant.}$$

Again, $\gamma \equiv \alpha + j\beta$, where α =attenuation cons & β =phase cons= $2\pi/\lambda$.


• Substituting $V(z,t)$ and $I(z,t)$ into eq.1 gives:

$$-\gamma V_0^+ e^{j\omega t - \gamma z} = -Z I_0^+ e^{j\omega t - \gamma z}$$

$$\frac{V_0^+}{I_0^+} = \frac{Z}{\gamma} = \pm \sqrt{\frac{Z}{Y}} = \pm \sqrt{\frac{R + j\omega L}{G + j\omega C}} \quad \text{Again, } \frac{V_0^+}{I_0^+} = Z_0 = \pm \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

• **Note:** ‘+’ & ‘-’ is used for observer looking into the ‘load’ & ‘generator’

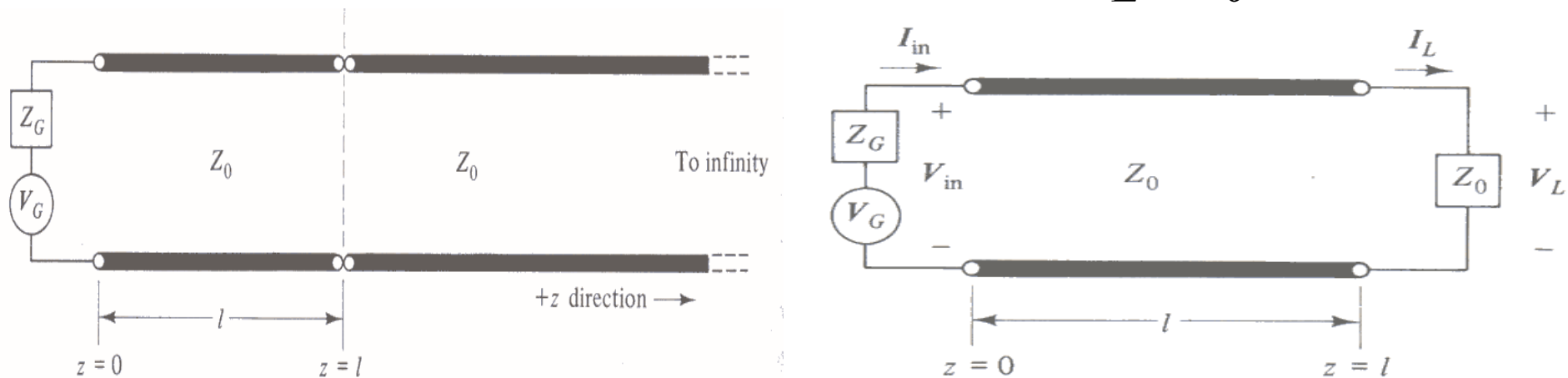
Infinitely long Transmission Line (or $Z_L = Z_0$):



- If ‘ $Z_L = Z_0$ ’ of TL \Rightarrow Matched \Rightarrow No reflection occurs $\Rightarrow \approx$ infinite line
- Time-average *incident power* & *loss/length* along the line (if ‘ Z_0 ’ is real)

$$P^+(z) = \frac{1}{2} [\text{Re} V^+(z) V^+(z)^*] = \frac{V_0^{+2}}{2Z_0} e^{-2\alpha z} \quad \alpha = \frac{-\Delta P / \Delta Z}{2P} = \frac{-(P_2 - P_1) / d}{2P_1}$$

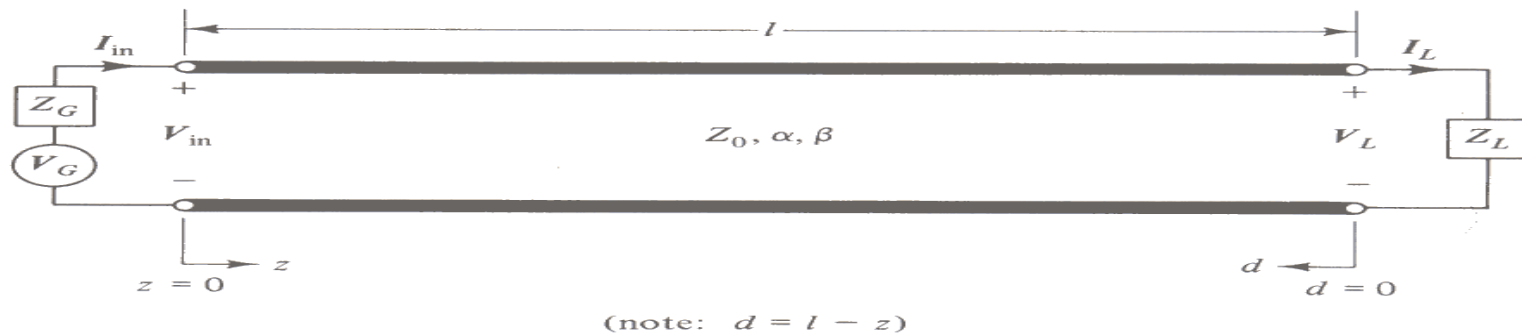Mismatched Transmission Line ($Z_L \neq Z_0$):



- If $Z_L = \infty$; when incident wave arrive at the O/C end, it must satisfy ;
 - (1) For the traveling wave: $V^+/I^+ = V^-/I^- = Z_0$ of the transmission line
 - (2) Ohm's law at O/C requires an infinite impedance as current is zero
- Creation of reflected waves (V^- , I^-) satisfies both requirements.
- Thus at any pt.of TL, $V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} = V^+ + V^-$ and $I(z) = I^+ - I^-$
- Load reflection coefficient, $\Gamma_L = V^-/V^+ = (V_0^- e^{\gamma l}) / (V_0^+ e^{-\gamma l}) = (V_0^-/V_0^+) \cdot e^{2\gamma l}$
- Thus, ref. coeff. Γ , at any point $d=(l-z)$ from the load end, is given by;

$$\Gamma = (V_0^- \cdot e^{\gamma(l-d)}) / (V_0^+ \cdot e^{-\gamma(l-d)}) = (V_0^- \cdot e^{+\gamma l} \cdot e^{-\gamma d}) / (V_0^+ \cdot e^{-\gamma l} \cdot e^{+\gamma d})$$

$$= [\{(V_0^- / V_0^+) \cdot e^{2\gamma l}\} e^{-\gamma l} \cdot e^{-\gamma d}] / (e^{-\gamma l} \cdot e^{+\gamma d}) = \Gamma_L \cdot e^{-2\gamma d} \quad (\text{eq. 5})$$
- Thus at $z=0$ (when $d=l$), $\Gamma_{in} = \Gamma_L \cdot e^{-2\gamma l} = \Gamma_L \cdot e^{-2(\alpha+j\beta)l} = |\Gamma_L| \cdot e^{-2\alpha l} \angle \phi_L - 2\beta l$

- Load ref. coeff. Γ_L can also be determined from Z_0 and Z_L values;
With $d=0$ (when $z=l$), $V_L = V^+ + V^- = V_0^+ e^{-\gamma l} + V_0^- e^{\gamma l} = V_0^+ e^{-\gamma l} [1 + \Gamma_L]$
Similarly, $I_L = I_0^+ e^{-\gamma l} [1 - \Gamma_L]$
- Since $Z_L = V_L / I_L = Z_0 \{(1 + \Gamma_L) / (1 - \Gamma_L)\}$ (eq. 6a)
- or $\Gamma_L = (Z_L - Z_0) / (Z_L + Z_0)$ (eq. 6b)
- Similarly, $\Gamma_G = (Z_G - Z_0) / (Z_G + Z_0)$ ‘where Z_G is the source impedance’

Transmission coefficient:

- Ratio of the transmitted voltage current over incident voltage or current
- Similar to “ Γ_L ”, using equation ‘ $V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} = V_{tr} e^{-\gamma z}$ ’ yields;
Transmission coefficient, $T = (2Z_L) / (Z_L + Z_0)$ (eq. 7)

Power Flow: For the circuit in previous figure, if Z_G is real;

- Input power : $P_{in} = \frac{V_G^2}{4Z_G} \frac{(1 - |\Gamma_G|^2)(1 - |\Gamma_{in}|^2)}{|1 - \Gamma_G \Gamma_{in}|^2}$
- Power delivered to load is: $P_L = \frac{V_G^2}{4Z_G} \frac{(1 - |\Gamma_G|^2)(1 - |\Gamma_L|^2)}{|1 - \Gamma_G \Gamma_L e^{-2\gamma l}|^2} e^{-2\alpha l}$

Standing wave ration (SWR):

- If both incident (V^+) and reflected (V^-) wave are present, the voltage at any point in line is the phasor sum of V^+ and V^- .
- Thus $|V_{\max}| = |V^+| + |V^-| = |V^+| + |\Gamma_L| \cdot |V^+| = |V^+| \{1 + |\Gamma_L|\}$
- and $V_{\min} = |V^+| - |V^-| = |V^+| \{1 - |\Gamma_L|\}$
- By definition, **VSWR** = $|V_{\max}| / |V_{\min}| = (1 + |\Gamma_L|) / (1 - |\Gamma_L|)$
or $|\Gamma_L| = (VSWR - 1) / (VSWR + 1)$
- In a lossless line, $1 < VSWR < \infty$ and is same everywhere along the line

Impedance Transformation: Impedance at pt. 'd' due to Z_L is;

$$Z_d = Z_0 \frac{1 + \Gamma_L e^{-2\gamma d}}{1 - \Gamma_L e^{-2\gamma d}} = Z_0 \frac{(Z_L + Z_0)e^{\gamma d} + (Z_L - Z_0)e^{-\gamma d}}{(Z_L + Z_0)e^{\gamma d} - (Z_L - Z_0)e^{-\gamma d}} \quad (\text{Using eq's 5, 6 \& Fig})$$

$$Z_d = Z_0 \frac{Z_L + Z_0 \tanh \gamma d}{Z_0 + Z_L \tanh \gamma d} \quad (\text{where, } \cosh \gamma z = (e^{\gamma z} + e^{-\gamma z})/2; \sinh \gamma z = (e^{\gamma z} - e^{-\gamma z})/2)$$

- In previous figure, if $d=l$, input impedance is; $Z_{in} = Z_0 \frac{Z_L + Z_0 \tanh \gamma l}{Z_0 + Z_L \tanh \gamma l}$
- For lossless case ($\alpha=0$), $\tanh \gamma l \Rightarrow j \tan \beta l$

- Special cases:

(1.a) Open Circuited TL: $Z_L = \infty$; $Z_{in(o/c)} = Z_0 \coth \gamma l$

(1.b) Short Circuited TL: $Z_L = 0$; $Z_{in(s/c)} = Z_0 \tanh \gamma l$

From these eq's: $\tanh \gamma l = \sqrt{(Z_{in(s/c)} / Z_{in(o/c)})}$ and $Z_0 = \sqrt{(Z_{in(o/c)} Z_{in(s/c)})}$

(2) Loss-free line: $\alpha = 0$ or $R = G = 0$; $\gamma = j\omega\sqrt{LC}$ and $Z_0 = \sqrt{L/C}$

(2) Low-loss line: $G \approx 0$ and $R \ll \omega L$; $\gamma = \{R\sqrt{C/L}\}/2 + j\omega\sqrt{LC}$
 $Z_0 = \sqrt{L/C} - \{jR\sqrt{1/LC}\}/(2\omega)$

- Example Problems (also solve the assignments given in the class):

(1) At 1 GHz, an air filled coaxial line has; $R = 4 \Omega/m$, $L = 450 \text{ nH/m}$,

$G = 7 \times 10^{-4} \text{ mho/m}$, $C = 50 \text{ pF/m}$. Find the related Z_0 , α , β , v_p and λ .

(2) For a loss-less TL, $L = 0.60 \mu\text{H/m}$, $C = 240 \text{ pF/m}$ and $\omega = 2\pi \times 10^8 \text{ rad/m}$.


(a) Find the related β and λ in the line. (assume air filled line)

(b) If the line length $l = \lambda/4$ and the line is terminated by $Z_L = -j100 \Omega$,


find the input impedance (Z_{in}) of the line. (Hint: $\beta = 2\pi/\lambda$)

Review


High-Frequency Device Characterization

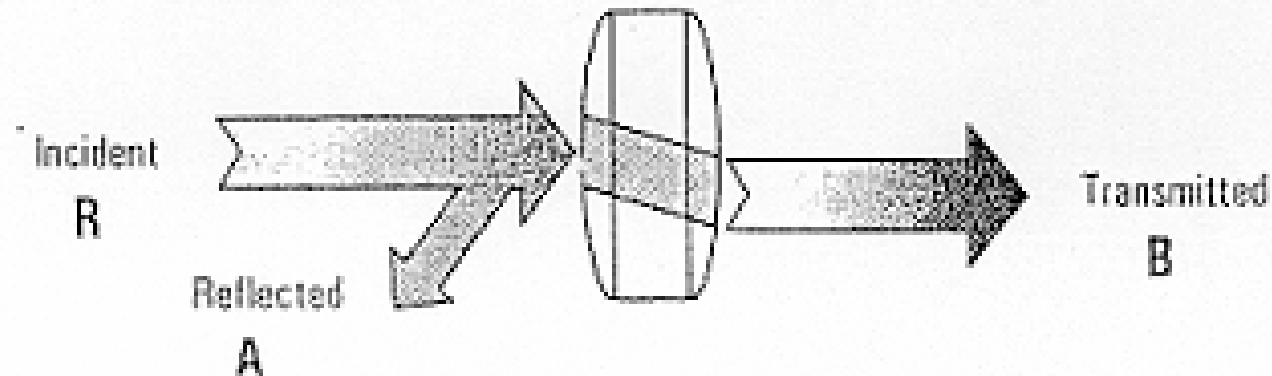

REFLECTION

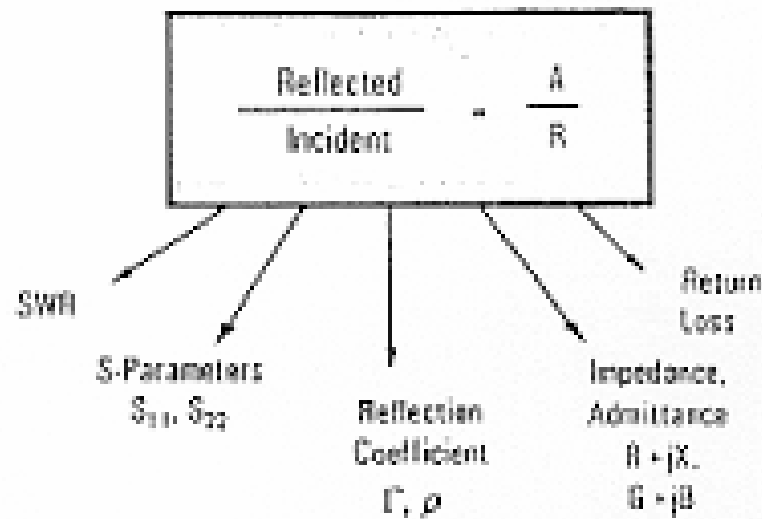

TRANSMISSION

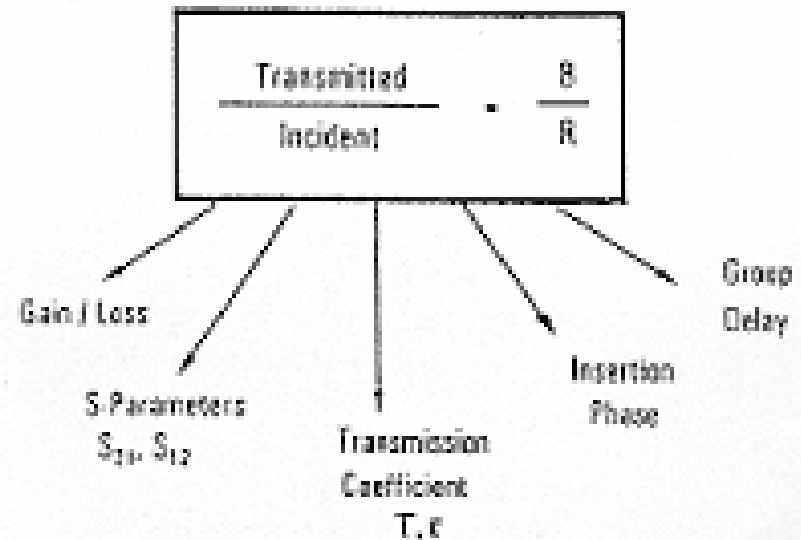

Review

Reflection Parameters

Reflection Coefficient $\Gamma = \frac{V_{\text{reflected}}}{V_{\text{incident}}} = \rho \angle \Phi = \frac{Z_L - Z_0}{Z_L + Z_0}$

Return loss $\triangleq -20 \log(\rho)$, $\rho = |\Gamma|$
 (Sign)



Voltage Standing Wave Ratio

$$\text{VSWR} = \frac{E_{\text{max}}}{E_{\text{min}}} = \frac{1 + \rho}{1 - \rho}$$

No reflection
 ($Z_L = Z_0$)

Full reflection
 ($Z_L = \text{open, short}$)

0	ρ	1
∞ dB	RL	0 dB
1	VSWR	∞