

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

Department of Electrical Engineering

EE 204 (062)

Final Exam
Monday June 11, 2007
7:00-9:30 pm
Location OAB

Student Name :

Student ID# :

Instructor's Name:


Select your instructor's name from the following:

- | | |
|--------------------------|-------------------------------|
| <input type="checkbox"/> | Mr. Tasadduq (sections 1 & 2) |
| <input type="checkbox"/> | Dr. Bakhashwain (section 3) |
| <input type="checkbox"/> | Mr. Johar (section 4) |
| <input type="checkbox"/> | Dr. Al-Ahmari (section 5) |
| <input type="checkbox"/> | Dr. Alakhdhar (section 6) |

	Maximum score	Score
Problem 1	20%	
Problem 2	20%	
Problem 3	20%	
Problem 4	20%	
Problem 5	20%	
Total	100%	


Problem 1:

For the circuit shown, determine the current $\mathbf{i(t)}$ and the voltage $\mathbf{v(t)}$.

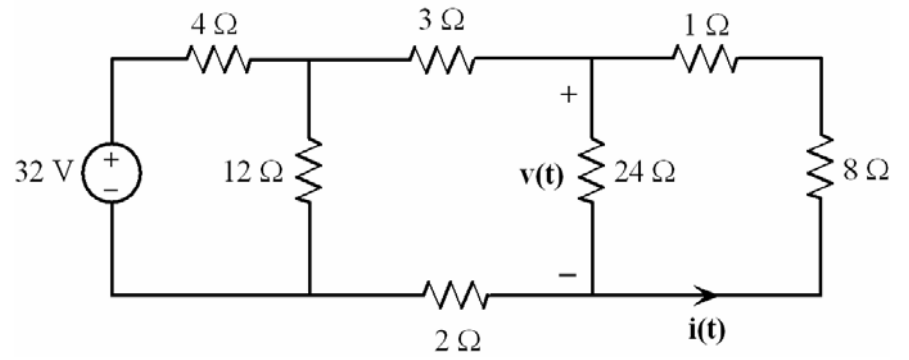

Problem 2:

Determine the voltage $v_o(t)$ in the circuit shown.

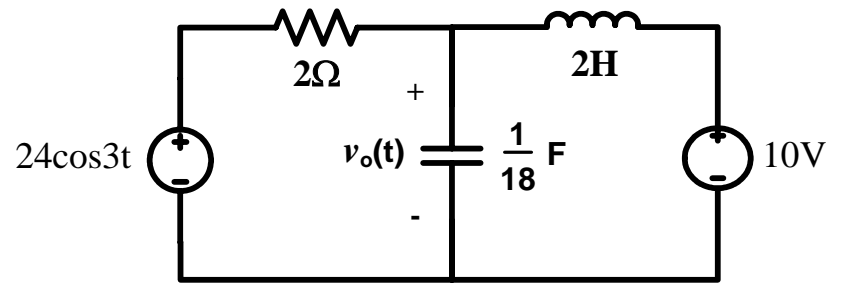

Problem 3:

The two loads \mathbf{Z}_1 & \mathbf{Z}_2 in the circuit shown are **described** by:

\mathbf{Z}_1 absorbs **12 kW** at **0.9 lagging** pf.


$\mathbf{Z}_2 = 4 + j 4 \Omega$.

a) Determine the current \hat{I}_1

$$\hat{V} = 240\sqrt{2}\angle 0^\circ \text{ V}$$

b) Determine the current \hat{I}_2

$$\omega = 10^3 \text{ rad/s}$$

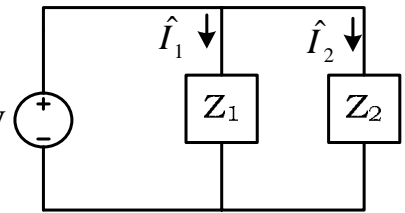

c) Determine the **complex power** \hat{P} delivered by the source.

d) Determine the **real power** P_{AV} delivered by the source.


e) Determine the **reactive power** Q delivered by the source.

Problem 4:

A balanced Y – Δ connected three phase system as shown, has $\mathbf{V}_{ab} = 208 \angle 45^\circ$ (rms).




The per phase impedance of the load is $\hat{Z}_L = 6\sqrt{2} \angle 45^\circ \Omega$. Find the following:

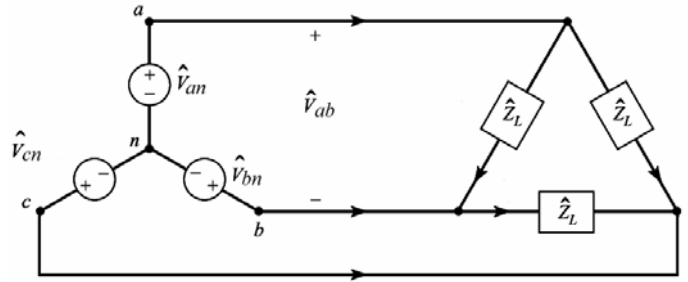- a) The **phase voltages** of the source.
- b) The **phase voltages** of the load.
- c) The **line currents**.
- d) The **total power** absorbed by the load.




Problem 5 (a,b,c and d):

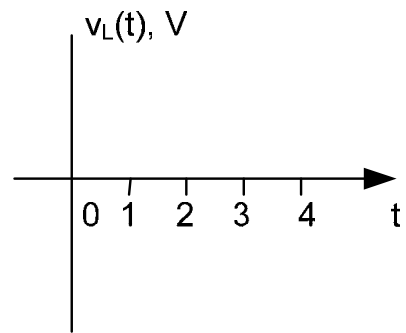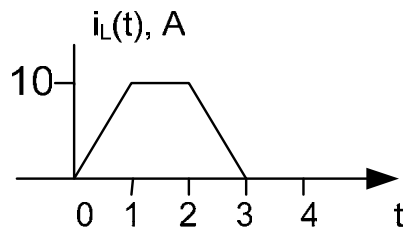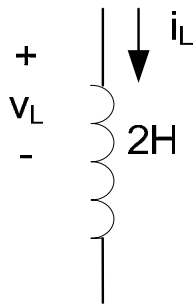a) The current $i_L(t)$ through the 2H inductor is shown. Sketch the voltage $v_L(t)$ for $0 \leq t \leq 4s$




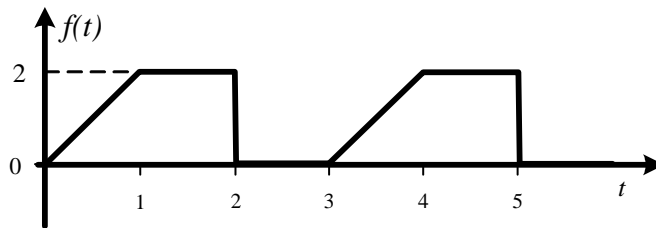b) Calculate the RMS (effective) value of the periodic function $f(t)$ shown in the figure below.



c) For the following circuit, the voltage v_x is:
(circle only the correct answer)

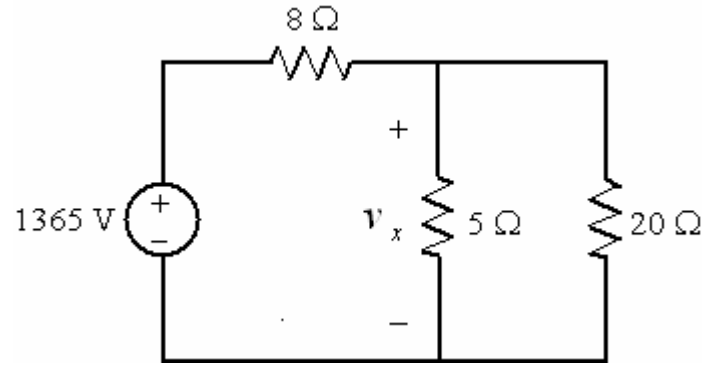- 1) 1092 V
- 2) 975 V
- 3) 525 V
- 4) 455 V
- 5) 273 V



d) The load in the circuit shown has a current $I_L=200\text{ A}$ at **pf=0.8** lagging, and a frequency **60Hz**. Calculate the value of the capacitor **C** to correct the power factor of the parallel combination of the capacitor and the load to unity (**pf=1**).

