

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

Department of Electrical Engineering

EE 204 (062)

Major Exam I
March 26, 2007

6:00-7:30 pm

Duration 1 and 1/2 hours

Student Name :

Student ID# :

Instructor Name:

Select your instructor's name from the following:

Mr. Tasadduq (sections 1 & 2)

Dr. Bakhashwain (section 3)

Mr. Johar (section 4)

Dr. Al-Ahmari (section 5)


Dr. Alakhdhar (section 6)

	Score
Problem 1	
Problem 2	
Problem 3	
Problem 4	
Total	

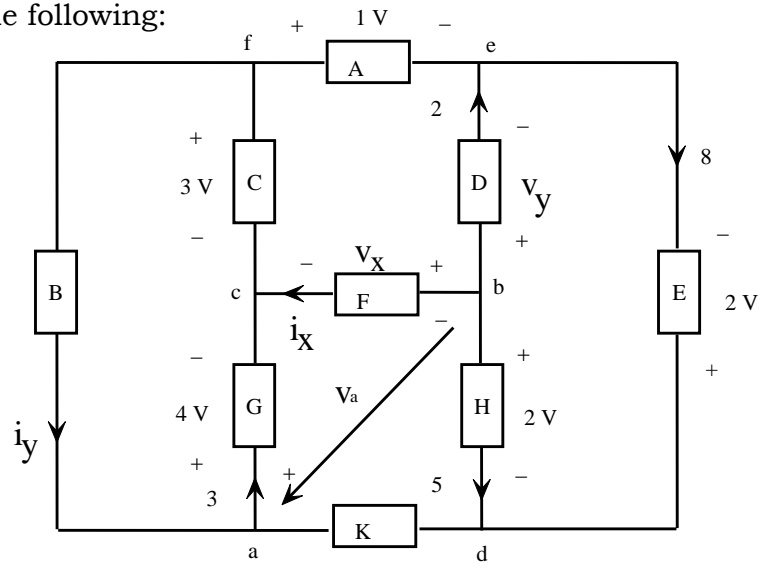Problem 1 (25%):


For the circuit shown determine the following:

- The voltage $\mathbf{v_x}$,
- The voltage $\mathbf{v_y}$,
- The voltage $\mathbf{v_{ab}}$,
- The current $\mathbf{i_x}$,
- The current $\mathbf{i_y}$, and
- The **power** delivered to the element B.




Problem 2 (25%):

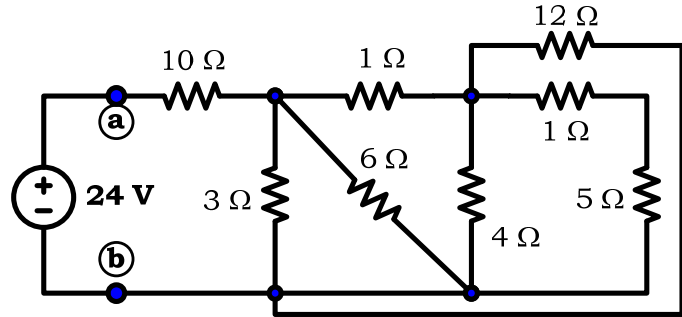- a) Find the **equivalent** resistance (R_{eq}) of the circuit to the right of a and b.
- b) Calculate the **power** absorbed by the **6- Ω** resistor.



Problem 3 (25%):

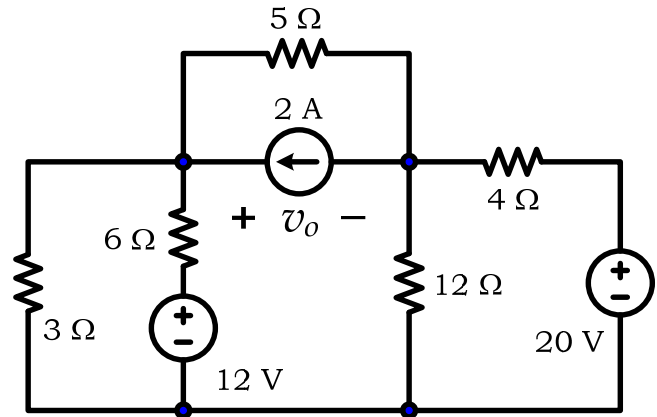- a) **Using source transformation**, simplify the circuit into a **single loop** containing only voltage sources, then
b) find the **voltage** U_o from the simplified circuit.



Problem 4 (25%):

Use the principle of superposition to find the voltage V_a and current I_1 .

