

# King Fahd University of Petroleum and Minerals

Electrical Engineering Department

EE 204: Fundamentals of Electric Circuits

Instructor: Umar M. Johar

Date: March 25, 2007

Term: 062

Quiz # 3

SR # \_\_\_\_\_

ID # \_\_\_\_\_

Name: \_\_\_\_\_

Sec # 4

For the circuit shown below, use **source transformation** to find the **voltage  $V_x$** .

