

Date: April 10, 2007

Term: 062

Quiz # 4

SR # \_\_\_\_\_

ID # \_\_\_\_\_

Name: \_\_\_\_\_

Sec # 4

For the circuit shown below, find the following.

- The **Thevenin** equivalent of the circuit to the left of a & b.
- The **Norton** equivalent of the circuit to the left of a & b.
- The **maximum power** that can be delivered to a resistor connected between a & b.

