

Date: April 22, 2007

Term: 062

Quiz # 5

SR # _____

ID # _____

Name: _____

Sec # 4

For the circuit shown below, **find the power of each source** in the circuit using **nodal analysis**.

