

Date: April 29, 2007

Term: 062

Quiz # 6

SR # \_\_\_\_\_

ID # \_\_\_\_\_

Name: \_\_\_\_\_

Sec # 4

For the circuit shown below, **find the power of each source** in the circuit using **Mesh analysis**.

