

Date: October 21, 2007

Term: 071

Quiz # 2

SR # _____

ID # _____

Name: _____

Sec # 1

1. Simplify the following circuit in to a single voltage source and a single resistor. Then, calculate the unknown current i_1 .

