

# King Fahd University of Petroleum and Minerals

Electrical Engineering Department

EE 208: Electrical Systems

Instructor: Umar M. Johar

## Home Work # 7

1. A balanced **Y – Y** three phase circuit has  $V_{an} = 130 \angle 20^\circ$ . The per phase **impedance** of the load is  $Z_p = 10 \Omega$ . Given that the line impedance is **zero**, find the following.
  - a. All **phase voltages** of the source.
  - b. All **line voltages** of the source.
  - c. All **phase voltages** of the load.
  - d. All **line voltages** of the load.
  - e. All **line currents**.
  - f. All **phase currents** of the load.
  - g. The **total power** absorbed by the load.
2. A  **$\Delta$ -load** has a **20- $\Omega$**  resistance in each of its phases. If this load is connected to a three-phase  **$\Delta$  – connected** generator having a line voltage  $V_{ab} = 208 \angle 0^\circ$  V and given that the line impedance is **zero**, find the following.
  - a. All **phase voltages** of the source.
  - b. All **line voltages** of the source.
  - c. All **phase voltages** of the load.
  - d. All **line voltages** of the load.
  - e. All **line currents**.
  - f. All **phase currents** of the load.
3. A balanced  **$\Delta – Y$**  three phase system has  $V_{ab} = 380 \angle 45^\circ$ . Each phase of the load is a **132.5  $\mu$ F capacitor**. Neglecting the **line impedance**, find the following. The frequency of the source is 60 Hz.
  - a. All **phase voltages** of the source.
  - b. All **line voltages** of the source.
  - c. All **phase voltages** of the load.
  - d. All **line voltages** of the load.
  - e. All **line currents**.
  - f. All **phase currents** of the load.
  - g. The **total reactive power** of the load.
4. A balanced **Y –  $\Delta$**  three phase system has  $V_{an} = 100 \angle 30^\circ$ . The per phase impedance of the load is  $Z_p = 3 \Omega$ . Given that the **line impedance** is **1 $\Omega$** , find the following.
  - a. All **phase voltages** of the source.
  - b. All **line voltages** of the source.
  - c. All **phase voltages** of the load.
  - d. All **line voltages** of the load.
  - e. All **line currents**.
  - f. All **phase currents** of the load.
  - g. The **total power** absorbed by the load.