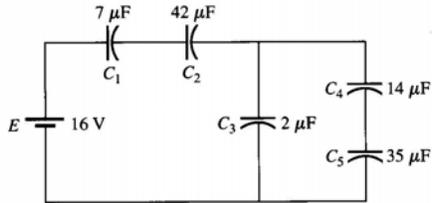


Question # 1 For the circuit shown below, find the following:


- the **total capacitance** seen by the voltage source
- the **energy** stored in C_2
- the **voltage** across C_5
- If $E = 10 \cos(10^4 t + 30^\circ)$ replaces the voltage source, find the **current** passing through this source.



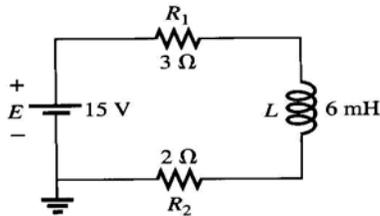Question # 2 For the circuit shown below,


- Find the **energy stored** in the inductor.
- If the **source E** is replaced by a **current source I_s** given by the equation stated below, find the **voltage** on the new source.

$$I_s = \begin{cases} (2 - 2e^{-500t}) & \text{for } t \geq 0 \\ 0 & \text{for } t < 0 \end{cases} \quad \&$$



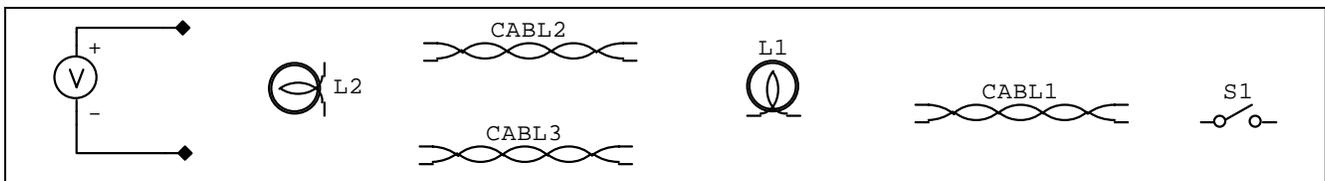Question # 5


- A given **10 kw** device needs an **AC voltage** source with a **peak value of 220 V** to operate. What is the **size** of the **circuit breaker** required to **protect** this device.
- Indicating the **coloring** of the wires, **show** one possible **connection** for each of the **two** circuits shown below. The two **ceiling** lamps are controlled by the switch shown. The receptacle is always available. **Use minimum colors and specify the type of each switch.**



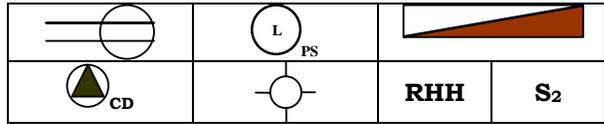Question # 3

- A **120-V** DC voltage source is connected to a **20-Ω** resistor through a **1500-ft** length wire. The wire has a diameter of $\frac{1}{4}$ -in and a resistivity of $2.825 \times 10^{-6} \Omega\text{-cm}$. Calculate the **power absorbed** by the resistor. (*Hint: 1 in = 2.54 cm and 1 ft = 12 in*)

- What does each of the following represent?



Question # 4 A balanced & **positive** sequenced **Y - Y** connected three phase system has a voltage $V_{ac} = 208 \angle 25^\circ$ V & a **per-phase** impedance of 10Ω . The lines connecting the source to the load have impedance of 2Ω each. Find the following for this system.

- The source **voltages** V_{ab} , V_{cb} & V_{bn}
- The **currents** I_{aA} , I_{cC} & I_{AN}
- The load **voltages** V_{CN} , V_{AB} & V_{CB}
- The **total true power** delivered to the load