
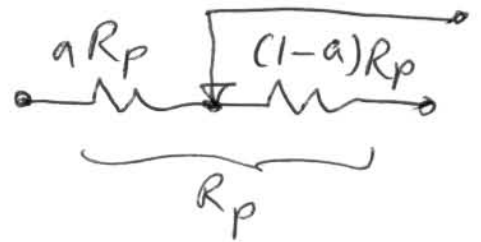


## Key to the project

The potentiometer can be drawn as shown.

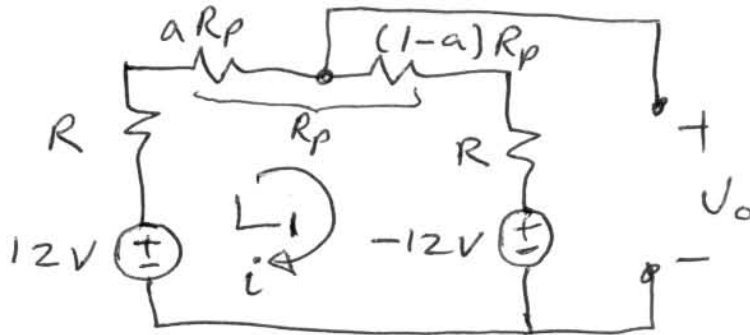

One possible solution can be



KVL for  $L_1$

$$-12 + [R + aR_p + (1-a)R_p + R]i - 12 = 0$$

$$i = \frac{24}{2R + R_p}$$

To reduce power consumption in the circuit, we must reduce the current by selecting  $R_p$  as large as possible (i.e. 50k $\Omega$ )

$$\therefore i = \frac{24}{2R + 50}$$

But  $V_o = 12 - [R + aR_p]i$

So  $V_o = 12 - \frac{24[R + aR_p]}{2R + 50}$ , for  $-5 \leq V_o \leq 5$   
for  $0 \leq a \leq 1$

For  $a=0$ ,  $V_o$  must be 5V

$$\therefore 5 = 12 - \frac{24R}{2R + 50} \Rightarrow \frac{24R}{2R + 50} = 7 \Rightarrow \boxed{R = 35k\Omega}$$

check; For  $a=1$ ,  $V_o$  must be -5V

$$V_o = 12 - \frac{24[35 + 50]}{2(35) + 50} = -5V \quad \checkmark$$

To obtain  $R = 35k\Omega$  use 15k + 20k resistors in series for example.

$$P = i^2(2R + R_p) = \left[ \frac{24}{2R + R_p} \right]^2 (2R + R_p) = 4.8 \text{ mW}$$