

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS  
DEPARTMENT OF ELECTRICAL ENGINEERING  
Dr. Alakhdhar

Student Name: \_\_\_\_\_

Student ID# \_\_\_\_\_

Use node analysis technique to calculate the current  $i_{\Delta}$  in the circuit shown..