

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
DEPARTMENT OF ELECTRICAL ENGINEERING
Dr. Alakhdhar

Student Name: _____

Student ID# _____

Use node analysis technique to calculate the current i_{Δ} in the circuit shown..