

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS  
DEPARTMENT OF ELECTRICAL ENGINEERING  
Dr. Alakhdhar

Student Name:

Student ID#

The variable resistor in the circuit shown is adjusted for maximum power transfer to  $R_L$ .

- Find the value of  $R_L$ .
- Find the maximum power that can be delivered to  $R_L$ .

