


KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
DEPARTMENT OF ELECTRICAL ENGINEERING
Dr. Alakhdhar

Student Name: _____

Student ID# _____

The current i_0 in the circuit is 10A. Find:

- The current i_a .
- The current i_g .
- The power delivered by the current source.

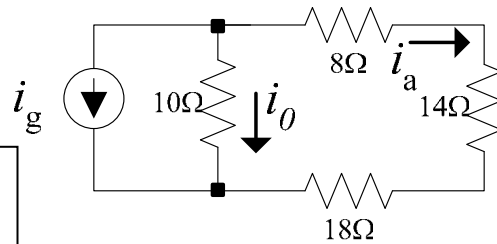**Answers:**

$i_a =$

$i_g =$

The power delivered by the current source =