

Student Name: \_\_\_\_\_

Student ID# \_\_\_\_\_

In the circuit shown, the switch has been closed for a long time before opening at  $t = 0$ .

- Find  $i(0^+)$ .
- Find  $v(0^+)$ .
- Find  $i(t)$ , for  $t \geq 0$

