

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

**Electrical Engineering Department
EE 306(071): Electromechanical Devices**

Quiz #1

Instructor: Dr. Zakariya Al-Hamouz

A balanced 3-phase Y-connected load with phase impedance of $20 + j15 \Omega$ is connected to a 400 V 3-phase, 50 Hz supply. Calculate:

- a) the line current
- b) the real and reactive power supplied by the source.

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

**Electrical Engineering Department
EE 306(071): Electromechanical Devices**

Quiz #2


Instructor: Dr. Zakariya Al-Hamouz

Student Name: _____

ID #: _____

The figure shows a ferromagnetic core with an air gap of 0.05 cm. The relative permeability of the core is 2000.

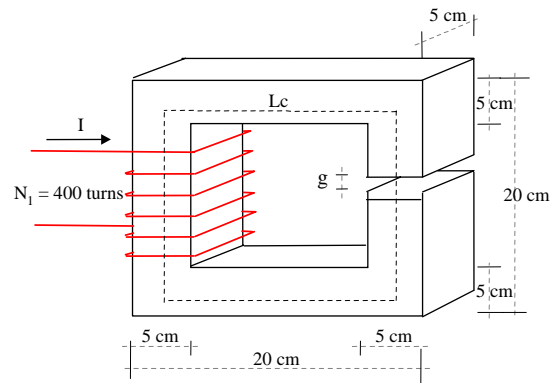- draw an equivalent magnetic circuit.
- Calculate the current I needed to produce a flux density of 0.4 Tesla in the air gap.



KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

**Electrical Engineering Department
EE 306(071): Electromechanical Devices**

Quiz #3

Instructor: Dr. Zakariya Al-Hamouz

Student Name:

ID #:

A 15-kVA 2300/230 –V single phase transformer has the following parameters referred to the high voltage side:

$$R_{eq} = R_1 + a^2 R_2 = 4.45\Omega; \quad X_{eq} = X_1 + a^2 X_2 = 6.45\Omega$$

$$X_M = 11\text{ k}\Omega; \quad R_C = 105\text{ k}\Omega$$

Using the approximate equivalent circuit, calculate the full load voltage regulation at 0.8 pf leading.

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

**Electrical Engineering Department
EE 306(071): Electromechanical Devices**

Quiz #4

Instructor: Dr. Zakariya Al-Hamouz

Student Name:

ID #:

A 220 V shunt motor having an armature resistance of 0.2Ω and a field resistance of 110Ω takes 4 A of line current while running on no load. When loaded, the motor runs at 1000 rpm while taking 42 A of line current. Calculate the no load speed.