

Name: _____

Key


ID # _____

1- In one hour, how many electrons pass between the terminals of a 12-V car battery when a 96 watts headlight is used? (Ans: 1.8×10^{23} electrons.)

$$q = I t = \frac{P}{V} t = \frac{96 \text{ W}}{12 \text{ V}} (3600 \text{ s}) = 28800 \text{ C}$$

$$\# \text{ of } e^- = \frac{q}{e} = \frac{28800}{1.6 \times 10^{-19}} = 1.8 \times 10^{23} \text{ electrons}$$

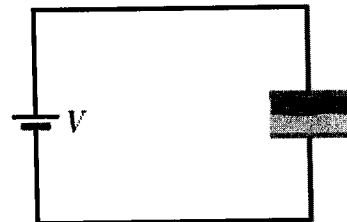2- In the figure, the parallel plate capacitor of plate area $2 \times 10^{-2} \text{ m}^2$ is filled with two dielectric slabs, each of thickness 2 mm. One slab has dielectric constant of 3 and the other 4. How much charge does a 7-V battery store on the capacitor?



We may think of this as two capacitors in series C_1 and C_2 , the former with the $\kappa_1 = 3.00$ material and the latter with the $\kappa_2 = 4.00$ material. Upon using Eq. 25-9, Eq. 25-27 and then reducing C_1 and C_2 to an equivalent capacitance (connected directly to the battery) with Eq. 25-20, we obtain

$$C_{eq} = \left(\frac{\kappa_1 \kappa_2}{\kappa_1 + \kappa_2} \right) \frac{\epsilon_0 A}{d} = 1.52 \times 10^{-10} \text{ F}$$

Therefore, $q = C_{eq} V = 1.06 \times 10^{-9} \text{ C}$.