

Name: _____

ID # _____

key


1- Calculate the emf (\mathcal{E}) of the battery shown in the figure.

3

$$R_{eq} = 5 + 3 + 2 = 10 \Omega$$

$$I = \frac{\mathcal{E}}{R_{eq}} = 2 \text{ A}$$
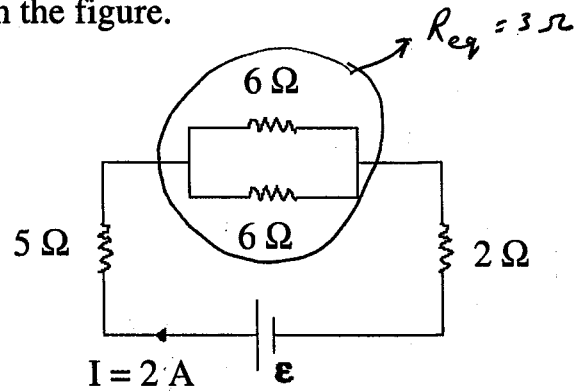
$$\Rightarrow \mathcal{E} = I R_{eq} = (2)(10) = 20 \text{ V}$$



2- Four 10- Ohm resistors are connected in **Parallel** and the combination is connected to a 12-V battery.


4

a) What is the current passing in any of the resistors?

$$\text{total current } I = \frac{\mathcal{E}}{R_{eq}} = \frac{12}{2.5} = 4.8 \text{ A}$$

$$\text{each resistor will have } i = \frac{I}{4} = \boxed{1.2 \text{ A}}$$

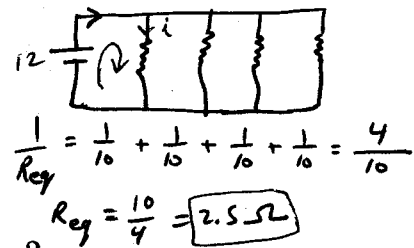or use loop rule $12 - iR = 0 \Rightarrow i = \frac{12}{10} = 1.2 \text{ A}$



b) What is the potential difference across any of the resistors?

$$V = iR = (1.2)(10) = 12 \text{ V}$$

the same as that of the battery
(because they are connected in parallel)

3- A 5- μ F capacitor is fully charged by connecting it to a 12-V battery. After disconnecting the battery, it was allowed for capacitor to discharge through a simple RC circuit, with a time constant of 4.0 s. What is the charge on the capacitor after one time constant has elapsed?

3

$$q = q_0 e^{-t/RC} \quad t = \tau = RC$$

$$q = C \mathcal{E} e^{-RC/RC}$$

$$q = C \mathcal{E} e^{-1} = (5 \times 10^{-6})(12)(e^{-1})$$

$$= 2.2 \times 10^{-5} \text{ C}$$