

Name:

Key

ID #

1- A certain capacitor (initially uncharged), is connected in series with a resistor and a battery. After being charged for 10 ms, the charge on the capacitor is half of its maximum value. What is the time constant (RC) of the circuit?

3

$$q = C\mathcal{E}(1 - e^{-t/RC}) \quad \text{put } t = 10 \text{ ms} = 10^{-2} \text{ s}$$

$$0.5 = 1 - e^{-\frac{0.01}{RC}} \quad \text{solve for } RC$$

$$-0.5 = -e^{-\frac{0.01}{RC}}$$

$$-\frac{0.01}{RC} = \ln 0.5$$

$$\Rightarrow RC = \frac{-0.01}{\ln 0.5} = 1.4 \times 10^{-2} \text{ s}$$

2- In the shown circuit, find the current passing through the 20- Ohm resistor.

left loop ↻


$$+10 - I_1(10) - 15 - I_1(20) = 0$$

$$-5 - 30(I_1) = 0$$

$$I_1 = \frac{-5}{30} = -\frac{1}{6} = -0.17 \text{ A}$$

the current  $I_1$  has a magnitude

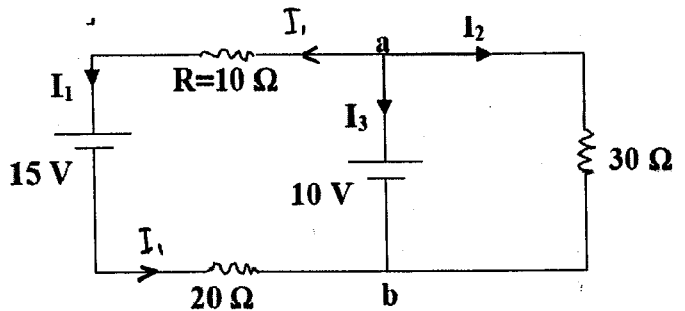of (0.17), and in a direction opposite to that drawn in the figure.



4

3- Three 20- Ohm resistors are connected in **Parallel** and the combination is connected to a 10-V battery.


a) What is the current passing in any of the resistors?

$$\text{total current } I = \frac{\mathcal{E}}{R_{eq}} = \frac{10}{(20/3)} = 1.5 \text{ A}$$

the current through each resistor

$$i = \frac{I}{3} = 0.5 \text{ A}$$

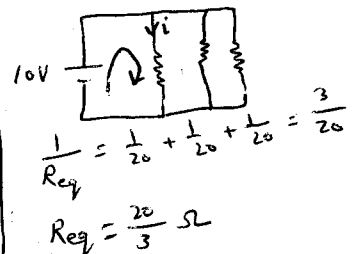or use loop rule:  $10 - iR = 0 \Rightarrow i = \frac{10}{20} = 0.5 \text{ A}$



b) What is the potential difference across any of the resistors?

$$V \text{ (across any resistor)} = iR = (0.5)(20) = 10 \text{ V}$$

the same as that of the battery

(because they are connected in parallel)