

4. In Figure 26.4, batter B supplies 12 V . (a) Find the charge on each capacitor first when only switch S_1 is closed and (b) later when switch S_2 is also closed. Take $C_1 = 1.0\ \mu\text{F}$, $C_2 = 2.0\ \mu\text{F}$, $C_3 = 3.0\ \mu\text{F}$ and $C_4 = 4.0\ \mu\text{F}$.

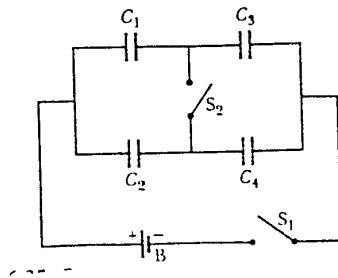


FIG. 26.4

5. A certain substance has a dielectric constant of 2.8 and a dielectric strength of 18 MV/m . If it is used as the dielectric material in a parallel-plate capacitor, what minimum area should the plates of the capacitor have to obtain a capacitance of $7.0 \times 10^{-2}\ \mu\text{F}$ and to ensure that the capacitor will be able to withstand a potential difference of 4.0 kV ?

Chapter 27

- Near Earth, the density of protons in the solar wind is 8.70 cm^{-3} and their speed is 470 km/s . (a) Find the current density of these protons. (b) If Earth's magnetic field did not deflect them, the protons would strike the planet. What total current would Earth then receive?
- A wire with a resistance of $6.0\ \Omega$ is drawn out through a die so that its new length is three times its original length. Find the resistance of the longer wire, assuming that the resistivity and density of the material are unchanged.
- A common flashlight bulb is rated at 0.30 A and 2.9 V (the values of the current and voltage under operating conditions). If the resistance of the bulb filament at room temperature (20°C) is $1.1\ \Omega$, what is the temperature of the filament when the bulb is on? The filament is made of tungsten.
- A cylindrical resistor of radius 5.0 mm and length 2.0 cm is made of material that has a resistivity of $3.5 \times 10^{-5}\ \Omega\text{ m}$. What are (a) the current density and (b) the potential difference when the energy dissipation rate in the resistor is 1.0 W ?
- A 100 W lightbulb is plugged into a standard 120 V outlet. (a) How much does it cost per month to leave the light turned on continuously? Assume electric energy costs 6c/kWh . (b) What is the resistance of the bulb? (c) What is the current in the bulb? (d) Is the resistance different when the bulb is turned off?

Chapter 28

- A wire of resistance $5.0\ \Omega$ is connected to a battery whose emf E is 2.0 V and whose internal resistance is $1.0\ \Omega$. In 2.0 min , (a) How much energy is transferred from chemical to electrical form? (b) How much energy appears in the wire as thermal energy? (c) Account for the difference between (a) and (b).
- In Figure 28.2, if the potential at point P is 100 V , what is the potential at point Q ?

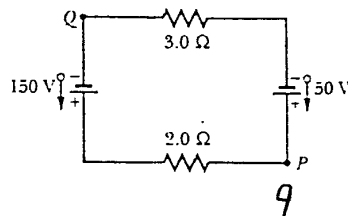


FIG. 28.2