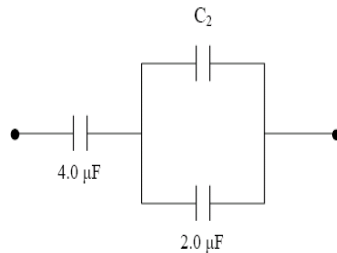


Old Exam. Questions Chapter 25


T071:

Q1. The three capacitors in the figure 1 have an equivalent capacitance of $2.77 \mu\text{F}$. What is C_2 ? (Ans: $7 \mu\text{F}$).



Q2. When the potential difference across a $5 \mu\text{F}$ capacitor is increased by 2 V , the energy stored increases by 10% . What was the original potential difference? (Ans: 40 V).

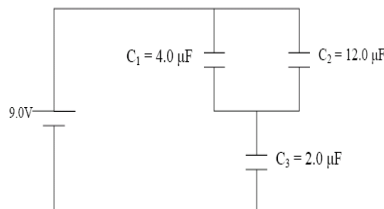
Q3. What is the charge on C_3 in the figure 2? (Ans: $16 \mu\text{C}$).



Q4. A parallel-plate capacitor is completely filled with a dielectric of dielectric constant 6 , has a capacitance of 50 pF . If the plate separation is 0.1 mm , find the plate area. (Ans: 0.94 cm^2)


T062:

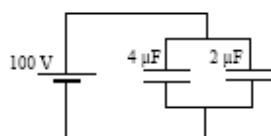Q14. How much energy is stored in the combination of capacitors shown figure (5)? (Ans: 0.03 mJ)




Q15. Consider three identical capacitors. Their equivalent capacitance when connected in parallel is C_p , and their equivalent capacitance when connected in series is C_s . Which of the following statements is **CORRECT**? ($C_p=9C_s$)

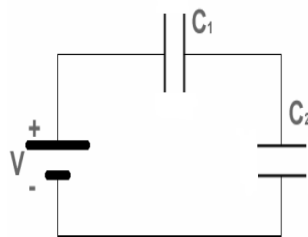Q16. Two parallel-plate capacitors are connected in series to a battery as shown in figure (6). A dielectric is inserted in capacitor C_1 . (The charge on C_2 increases)



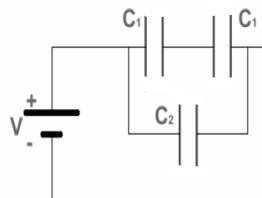Q17.: Figure (7) shows three capacitors connected to a battery of voltage $V = 6$ Volts. The charges on the capacitors are known to be $Q_1 = 24 \mu\text{C}$ for C_1 and $Q_2 = 96 \mu\text{C}$ for C_2 . What are the values of the capacitances C_1 and C_2 ? (Ans: $C_1=8 \mu\text{F}$, $C_2= 16 \mu\text{F}$)




T061:

Q#15. A parallel plate capacitor has square shaped plates with an area $= 4.1 \times 10^{-3} \text{ m}^2$ and $1.6 \times 10^{-3} \text{ m}$ separation. What charge will appear on the plates of such capacitor if a potential difference of 80 V is applied? (Ans: $1.8 \times 10^{-9} \text{ C}$)

Q#16. An air filled parallel-plate capacitor has a capacitance of 3.0×10^{-12} F. The plate separation is then doubled and a wax dielectric is inserted, completely filling the space between the plates. As a result the, capacitance becomes 7.5×10^{-12} F . The dielectric constant of the wax is: **(Ans: 3)**

Q#15. A parallel plate capacitor has square shaped plates with an area = 4.1×10^{-3} m² and 1.6×10^{-3} m separation. What charge will appear on the plates of such capacitor if a potential difference of 80 V is applied? **(Ans: 1.8×10^{-9} C)**

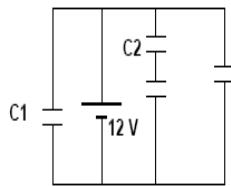Q#17. A battery having potential difference $V = 12$ V and four capacitors, each having a capacitance of $12 \mu\text{F}$, are connected as shown in the figure 1. What is the charge on C2? **(Ans: $72 \mu\text{C}$)**



Q#18. Consider the combination of capacitors as shown in the Figure 2. The energy stored in the $8.0 \mu\text{F}$ capacitor is 0.40 J. The energy stored in the $5.0 \mu\text{F}$ capacitor is: **(Ans: 0.25 J)**

