

94 In Fig. 27-80, $R_1 = 5.00 \, \Omega$, $R_2 = 10.0 \, \Omega$, $R_3 = 15.0 \, \Omega$, $C_1 = 5.00 \, \mu\text{F}$, $C_2 = 10.0 \, \mu\text{F}$, and the ideal battery has emf $\mathcal{E} = 20.0 \, \text{V}$. Assuming that the circuit is in the steady state, what is the total energy stored in the two capacitors?

