

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
 PHYSICS DEPARTMENT
 QUIZ #10- CHAPTER 27


NAME: Key ID# _____ SECTION# _____

a. What is the value and direction of the current in the $8\ \Omega$ resistor?

Kirchhoff's for the big loop

$$-4 \times 3 + 6 \times 5 - 8i = 0$$

$$\boxed{i = 2.25\text{ A}}$$

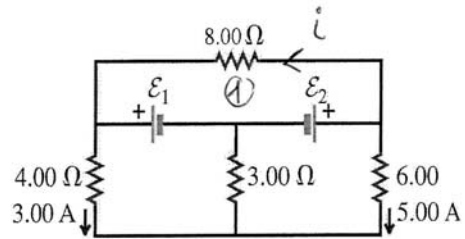

T042-Fig. 5

If $\mathcal{E}_2 = 30\text{ V}$, What is the value of \mathcal{E}_1 ?

Kirchhoff's for loop 1

$$-\mathcal{E}_1 + \mathcal{E}_2 - 8 \times 2.25 = 0$$

$$\mathcal{E}_1 = -18 + 30 = 12\text{ V}$$



$$\boxed{\mathcal{E}_1 = 12\text{ V}}$$

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
 PHYSICS DEPARTMENT
 QUIZ #10- CHAPTER 27

NAME: Key ID# _____ SECTION# _____

The potential difference between points Va-Vb = 24 V.

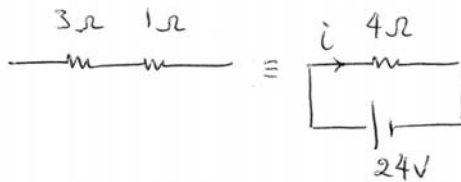
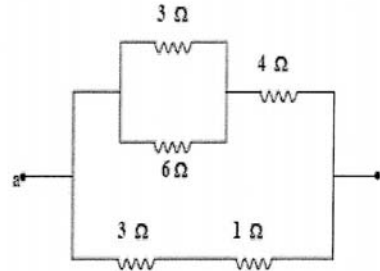
a. Calculate the current in the 1 Ω resistor.



$$i = \frac{24}{4} = 6 \text{ A}$$

$$\boxed{i = 6 \text{ A}}$$

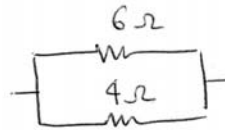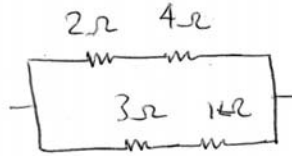
b. Calculate the power dissipated in the ~~resistor~~ resistors.



$$P = i^2 R$$

$$= (10)^2 \times 2.4$$

$$\underline{10 \quad 240 \text{ W}}$$

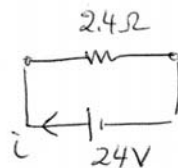

$$i = \frac{24}{2.4} = 10 \text{ A}$$


KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
 PHYSICS DEPARTMENT
 QUIZ #10- CHAPTER 27

NAME: Key ID# _____ SECTION# _____

In the circuit shown in the figure, the capacitor is initially uncharged. At $t = 0$, switch S is closed.

$\mathcal{E} = 9 \text{ V}$, $R = 15 \Omega$ and $C = 60 \mu\text{F}$.

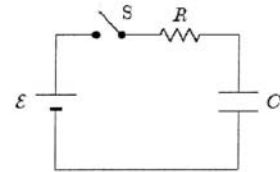- a. What is the **voltage** across the **resistor** $50 \mu\text{s}$ after the switch is closed?



$$\begin{aligned}
 V &= iR = \frac{\mathcal{E}}{R} e^{-t/RC} \times R \\
 &= \mathcal{E} e^{-t/RC} \\
 &= 9 e^{-\frac{50 \times 10^{-6}}{15 \times 60 \times 10^{-6}}} = 9 e^{-0.056} = 8.5 \text{ V}
 \end{aligned}$$

$$\boxed{V = 8.5 \text{ V}}$$

- b. At what time is the **charge** on the **capacitor** one-third its maximum value?

$$\begin{aligned}
 q &= q_{\text{max}} (1 - e^{-t/RC}) \\
 \frac{q_{\text{max}}}{3} &= q_{\text{max}} (1 - e^{-t/RC}) \\
 \frac{1}{3} &= 1 - e^{-t/RC} \Rightarrow e^{-t/RC} = 0.666
 \end{aligned}$$

$$\begin{aligned}
 -\frac{t}{RC} &= -0.41 \\
 \boxed{t = 3.6 \times 10^{-4} \text{ s}}
 \end{aligned}$$