


Physics 102-Rec  
Quiz#8-Sect.23  
Chapter 27

Instructor: Dr. A. Mekki

Name: Key

Id:

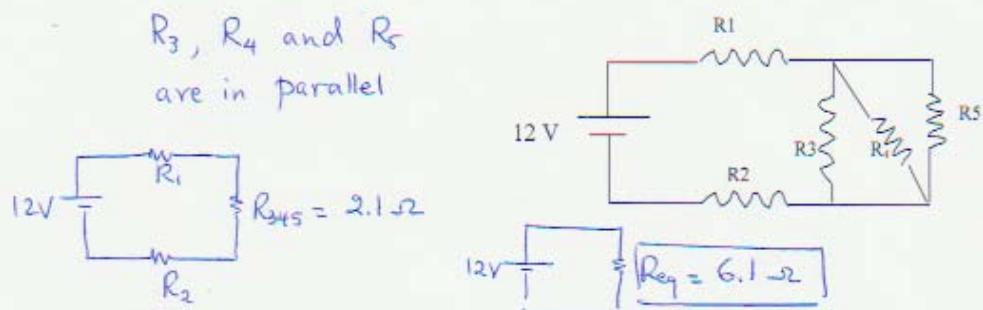- (a) Find the equivalent resistance for the circuit shown in the figure with  $R_1 = R_2 = 2 \Omega$ ,  $R_3 = R_4 = 7 \Omega$ ,  $R_5 = 5 \Omega$  and  $\epsilon = 12 \text{ V}$ .



- (b) What is the current in the resistance  $R_5$ ?

$$I = \frac{12}{6.1} = 1.96 \text{ A}$$

$$V_{R_1} = IR_1 = 3.93 \text{ V} = V_{R_2}$$

$$V_{R_{345}} = 12 - 2 \times 3.93 = 4.14 \text{ V}$$

$\Rightarrow R_3, R_4$  and  $R_5$  are in parallel

$$\Rightarrow V_{R_5} = 4.14 \text{ V} \Rightarrow I_{R_5} = \frac{V_{R_5}}{R_5} = \frac{4.14}{5} = 0.82 \text{ A}$$