

**Physics 102.13**  
**Quiz# 9&10**  
**Chapters 26 & 27**

Instructor: Dr. A. Mekki

Name: \_\_\_\_\_

**Key**

Id: \_\_\_\_\_

1. A tungsten light bulb has a resistance of  $12 \Omega$  when cold ( $20^\circ\text{C}$ ) and  $100 \Omega$  when on (hot). Calculate the temperature coefficient of resistance is  $0.0045^\circ\text{C}^{-1}$ .

$$R = R_0 (1 + \alpha \Delta T) \Rightarrow \frac{R}{R_0} = 1 + \alpha \Delta T$$







$$\Rightarrow \Delta T = \frac{\frac{R}{R_0} - 1}{\alpha} = \frac{\frac{8.33}{1} - 1}{0.0045} = 1629.6^\circ\text{C}$$

$$T_f - 20 = 1629.6^\circ\text{C} \Rightarrow \boxed{T_f = 1650^\circ\text{C}}$$

2. In the circuit shown, each resistance is  $100 \Omega$ .


- (a) Find the equivalent resistance.  
 (b) Find the voltage drop across  $R_1$ .

a)

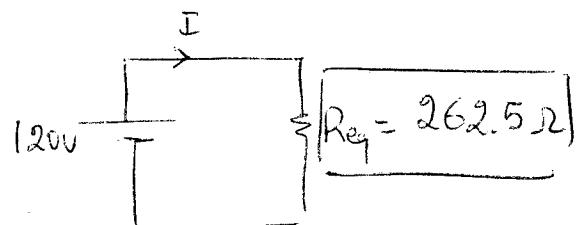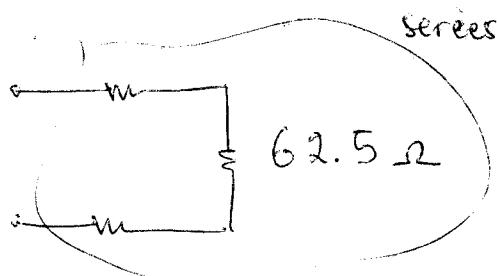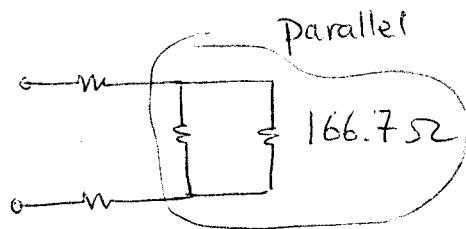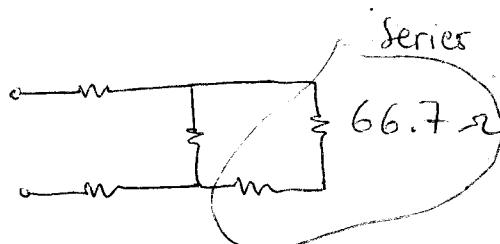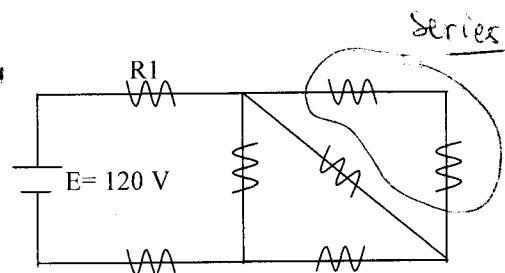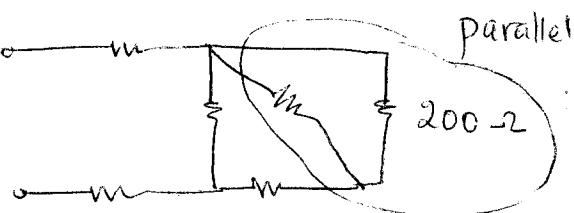

b)
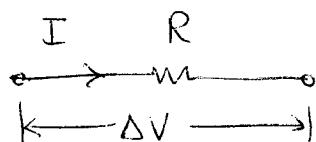
$$I = \frac{120}{262.5} = \boxed{0.457 \text{ A}}$$



$$\Delta V = I R$$

$$= 0.457 \times 100$$

$$\boxed{\Delta V = 45.7 \text{ V}}$$

Instructor: Dr. A. Mekki

Name:

Key

Id:

1. A wire with a resistance of  $10 \Omega$  is lengthened to 1.25 times its original length by pulling it through a small hole. Find the resistance of the wire after it is stretched.

$$R_0 = \rho \frac{L_0}{A_0} = 10 \Omega$$

since  $V = \text{constant}$

$$A_0 k_0 = AL$$

$$= A \times 1.25 k_0$$

$$A = \frac{A_0}{1.25}$$

$$R = \rho \frac{L}{A} = \rho \frac{1.25 L_0}{A}$$

$$R = \rho \frac{\frac{1.25 L_0}{A_0}}{1.25} = (1.25)^2 \rho \frac{L_0}{A_0}$$

$$= (1.25)^2 R_0 = (1.25)^2 \times 10 = \boxed{15.6 \Omega}$$


2. Consider the circuit shown in the figure.

- (a) Calculate the current  $I_3$  passing through  $R_3$ .  
(b) Calculate  $V_B - V_A$  using two different paths.

a) loop II :

$$20 - 5 - 10 I_3 = 0$$

$$\Rightarrow \boxed{I_3 = 1.5 A}$$

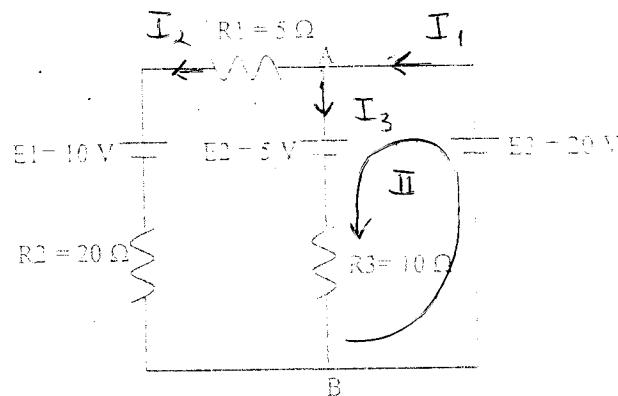

b)  $V_B - V_A = -20 V$  (through  $E_3$ ).

$$V_B - V_A = -5 - I_3 R_3 = -5 - 1.5 \times 10 = -20 V$$

(through the middle branch).

**Physics 102.15**  
**Quiz# 9&10**  
**Chapter 27**

Instructor: Dr. A. Mekki


Name: Key Id: \_\_\_\_\_

1. The current through the  $10\ \Omega$  resistor is 1 A to the right. What is the value of  $E_2$ ?

$$E_1 - 10I - 5I + E_2 - 20I = 0$$

$$10 + E_2 - 35I = 0$$

$$10 + E_2 - 35 = 0$$

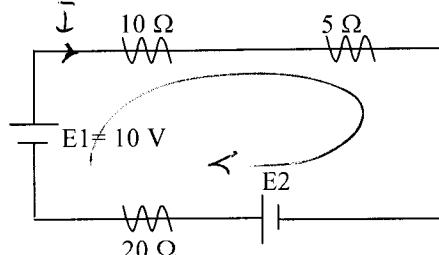

$$E_2 = 35 - 10 = \boxed{25\text{ V}}$$

2. A resistance of  $15\text{ k}\Omega$  is connected to an emf of 24 V and to a capacitor of capacitance  $C$ . If the time constant is measured to be  $55\text{ }\mu\text{s}$ , calculate

- (a) the capacitance of the capacitor

$$\tau = RC \Rightarrow C = \frac{\tau}{R} = \boxed{3.67 \times 10^{-9}\text{ F}}$$

- (b) the time it takes for the voltage across the resistor to reach 16 V.

The voltage across the capacitor is  $24 - 16 = 8\text{ V}$

$$V_C = V_0 (1 - e^{-\frac{t}{RC}}) \Rightarrow$$

$$8 = 24 \left(1 - e^{-\frac{t}{55 \times 10^{-6}}}\right)$$

$$0.33 = 1 - e^{-\frac{t}{55 \times 10^{-6}}}$$

$$e^{-\frac{t}{55 \times 10^{-6}}} = 0.67$$

$$t = -55 \times 10^{-6} \ln(0.67) = \boxed{2.2 \times 10^{-5}\text{ s}}$$