

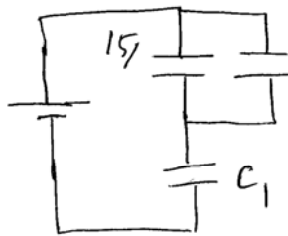
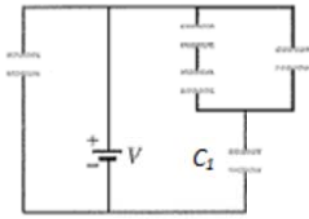


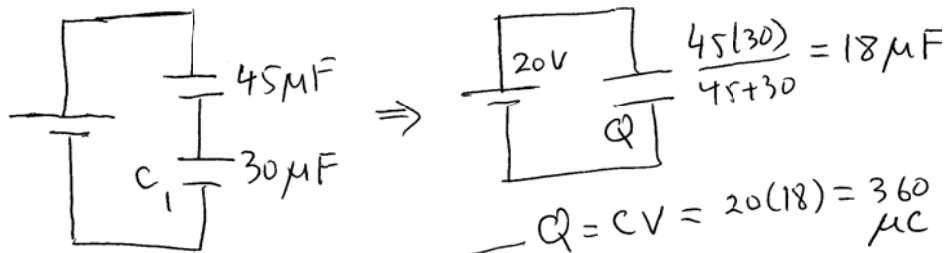In the figure below, the battery has a potential difference of  $V = 20\text{ V}$  and the five capacitors each has a capacitance of  $30\text{ }\mu\text{F}$ . What is the voltage across capacitor  $C_1$ ?


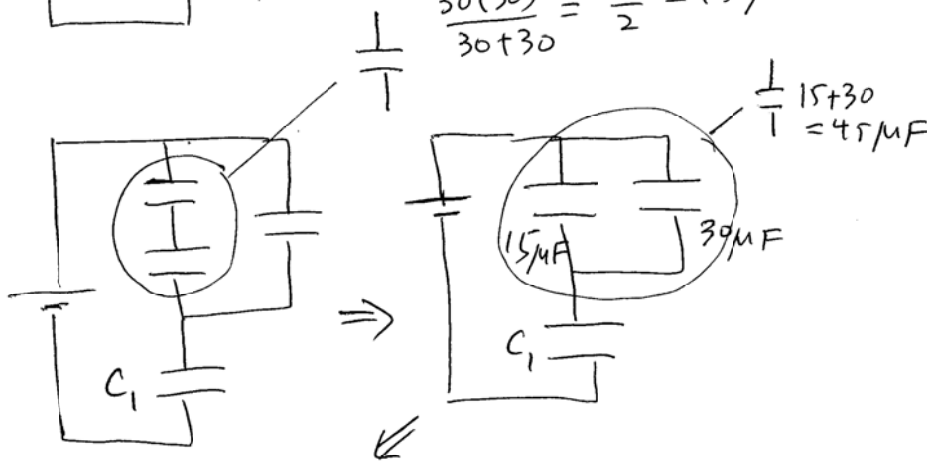
$$\frac{30(30)}{30+30} = \frac{30}{2} = 15\text{ }\mu\text{F}$$



$$Q = CV = 20(18) = 360\text{ }\mu\text{C}$$

$$Q_1 = Q = 360\text{ }\mu\text{C}$$

$$V_1 = \frac{Q_1}{C_1} = \frac{360}{30} = 12\text{ V}$$

04 Sep	11 Sep	18 Sep	25 Sep	2 Oct	9 Oct	23 Oct	30 Oct	6 Nov	13 Nov	20 Nov	27 Nov	4 Dec	11 Dec	18 Dec