

CHAPTER 26

10E. A spherical drop of mercury of radius R has a capacitance given by $C = 4\pi\epsilon_0 R$. If two such drops combine to form a single larger drop, what is its capacitance?

26-10 The volume of each drop is $V = \frac{4\pi}{3} R^3$

After combination, the volume of the drop will be $\frac{4\pi}{3} R'^3$. But


$$\frac{4\pi}{3} R'^3 = 2 \left(\frac{4\pi}{3} \right) R^3$$

$$\Rightarrow R' = 2^{\frac{1}{3}} R$$

the new capacitance will be

$$C' = 4\pi\epsilon_0 R' = \underline{\underline{2^{\frac{1}{3}} C}}$$

one drop

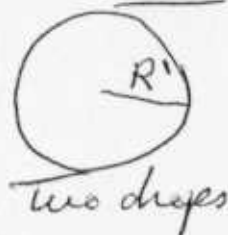

17E. Each of the uncharged capacitors in Fig. 26-28 has a capacitance of $25.0 \mu\text{F}$. A potential difference of 4200 V is established when the switch is closed. How many coulombs of charge then pass through meter A?


26-17

$$C_{eq} = C + C + C = 3C$$

$$q = C_{eq} V = 3CV$$

$$= 3(25 \mu\text{F})(4200 \text{ V})$$

$$= 0.315 \text{ C}$$

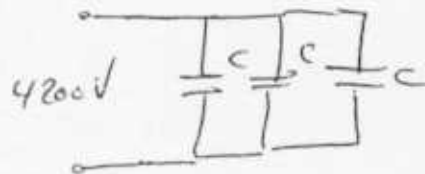


29P. In Fig. 26-33, capacitors $C_1 = 1.0 \mu\text{F}$ and $C_2 = 3.0 \mu\text{F}$ are each charged to a potential difference of $V = 100 \text{ V}$ but with opposite polarity as shown. Switches S_1 and S_2 are now closed. (a) What is now the potential difference between points a and b ? What are now the charges on (b) C_1 and (c) C_2 ?

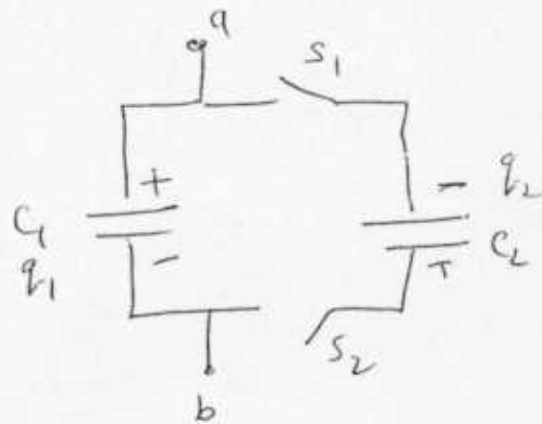26-29 before connection

$$q_1 = C_1 V = (1 \mu\text{F})(100) = 10^{-4} \text{ C}$$

$$q_2 = C_2 V = (3 \mu\text{F})(100) = 3 \times 10^{-4} \text{ C}$$



(a) after connection

$$q_{\text{total}} = q_2 - q_1 = 2 \times 10^{-4} \text{ C.}$$

for parallel connection $C_{\text{eq}} = C_1 + C_2 = 4 \mu\text{F}$

$$\therefore V_{ab} = \frac{q_{\text{total}}}{C_{\text{eq}}} = \frac{2 \times 10^{-4}}{4 \times 10^{-6}} = \underline{\underline{50 \text{ Volts}}}$$

(b) The charge on $C_1 \Rightarrow q_1' = C_1 V_{ab} = (1 \mu\text{F})(50) = \underline{\underline{5 \times 10^{-5} \text{ C}}}$


(c) on $C_2 = q_2' = C_2 V_{ab} = (3 \mu\text{F})(50) = \underline{\underline{1.5 \times 10^{-4} \text{ C}}}$

31P. In Fig. 26-35, battery B supplies 12 V. (a) Find the charge on each capacitor first when only switch S_1 is closed and (b) later when switch S_2 is also closed. Take $C_1 = 1.0 \mu\text{F}$, $C_2 = 2.0 \mu\text{F}$, $C_3 = 3.0 \mu\text{F}$, and $C_4 = 4.0 \mu\text{F}$.

$C_1 = 1 \mu\text{F}$
 $C_2 = 2 \mu\text{F}$

$C_3 = 3 \mu\text{F}$, $C_4 = 4 \mu\text{F}$
 $V = 12 \text{ Volts}$

26-31

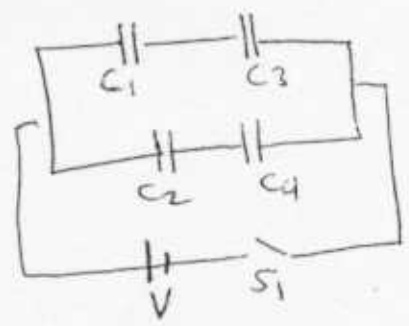

(a) If S_1 is closed

$$q_1 = q_3 = C_{13} V = \left(\frac{C_1 C_3}{C_1 + C_3} \right) V = \left[\frac{1 \times 3}{(1+3)} \right] 12 \times 10^{-6}$$

$= 9 \mu\text{C}$

$$q_2 = q_4 = \left(\frac{C_2 C_4}{C_2 + C_4} \right) V = \left[\frac{2 \times 4}{(2+4)} \right] 12 \times 10^{-6}$$

$= 16 \mu\text{C}$

(b) when S_2 is closed


$C_{12} = C_1 + C_2$, $C_{34} = C_3 + C_4$

$C_{eq} = \frac{(C_1 + C_2)(C_3 + C_4)}{(C_1 + C_2) + (C_3 + C_4)}$, $q_{total} = V C_{eq}$

$$V_1 = \frac{q_{total}}{C_{12}} = \frac{(C_3 + C_4)}{(C_1 + C_2 + C_3 + C_4)} V = \frac{(3 + 4)}{(1 + 2 + 3 + 4)} (12) \text{ V}$$

$= 8.4 \text{ Volts} \Rightarrow V_2 = 12 - 8.4 = 3.6 \text{ Volts}$

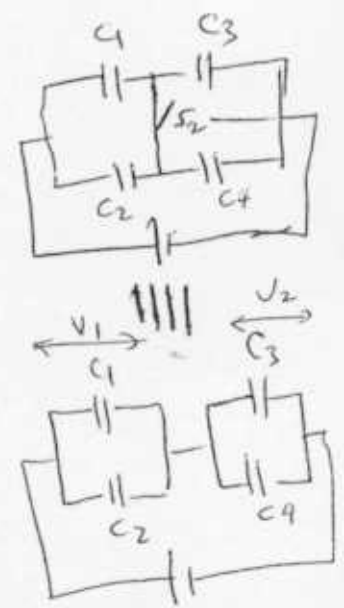
$q_1 = C_1 V_1 = (1 \mu\text{F})(8.4) = 8.4 \mu\text{C}$
 $q_2 = C_2 V_1 = (2 \mu\text{F})(8.4) = 16.8 \mu\text{C}$
 $q_3 = C_3 V_2 = (3 \mu\text{F})(3.6) = 10.8 \mu\text{C}$
 $q_4 = C_4 V_2 = (4 \mu\text{F})(3.6) = 14.4 \mu\text{C}$



check on results

$q_{total} = (12) \left[\frac{(1+2)(3+4)}{1+2+3+4} \right]$
 $= 25.2 \mu\text{C}$
 $q_1 + q_2 = 25.2 \mu\text{C}$
 $q_3 + q_4 = 25.2 \mu\text{C}$

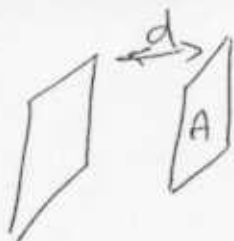38E. A parallel-plate air-filled capacitor having area 40 cm^2 and plate spacing 1.0 mm is charged to a potential difference of 600 V . Find (a) the capacitance, (b) the magnitude of the charge on each plate, (c) the stored energy, (d) the electric field between the plates, and (e) the energy density between the plates.



$$A = 40 \text{ cm}^2 = 40 \times 10^{-4} \text{ m}^2$$

$$d = 1 \text{ mm} = 10^{-3} \text{ m}$$

$$V = 600 \text{ Volt}$$

$$\text{26-38} \text{ (a) } C = \frac{\epsilon_0 A}{d} = \frac{(8.85 \times 10^{-12})(40 \times 10^{-4})}{10^{-3} \text{ m}}$$

$$= \underline{\underline{3.5 \times 10^{-11} \text{ F}}} = \underline{\underline{35 \text{ pF}}}$$

$$\text{(b) } q = CV = (35 \times 10^{-12})(600) = \underline{\underline{21 \text{ nC}}}, (\text{n} = 10^{-9})$$


$$\text{(c) } U = \frac{1}{2} CV^2 = \frac{1}{2} (35 \times 10^{-12})(600)^2$$

$$= \underline{\underline{6.3 \times 10^{-6} \text{ J}}}$$

$$\text{(d) } E = \frac{V}{d} = \frac{600}{10^{-3}} = 6 \times 10^5 \text{ V/m}$$

$$\text{(e) } u = \frac{U}{\text{Volume}} = \frac{6.3 \times 10^{-6}}{(40 \times 10^{-4})(10^{-3})} = 1.6 \frac{\text{J}}{\text{m}^3}$$

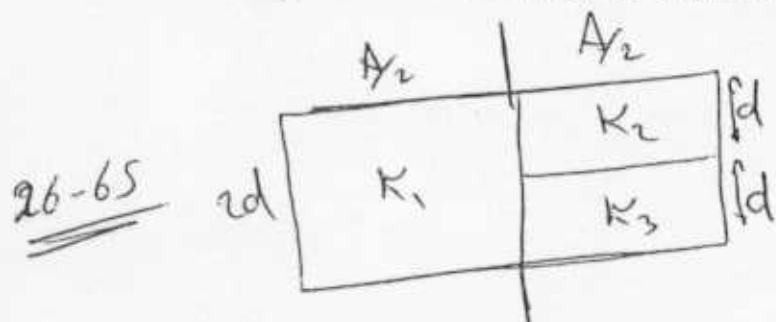65P. What is the capacitance of the capacitor, of plate area A , shown in Fig. 26-39? (Hint: See Problems 63 and 64.)



Consider $C_0 = \frac{\epsilon_0 A}{2d}$

$$C_1 = K_1 \epsilon_0 \frac{A/2}{2d} = \frac{K_1 C_0}{2}, \quad C_2 = K_2 \epsilon_0 \frac{A/4}{d} = K_2 C_0$$

$$C_3 = K_3 C_0$$

$$C_{23} = \frac{C_2 C_3}{C_2 + C_3}$$

$$C_{123} = C_1 + C_{23}$$

$$= \frac{K_1 C_0}{2} + \frac{K_2 C_0 K_3 C_0}{(K_2 + K_3) C_0}$$

$$= \frac{C_0}{2} \left[K_1 + \frac{2K_2 K_3}{K_2 + K_3} \right]$$

