






Chapter 26 (Dr. M.A. Gondal, Phys102-10-12)

T-041-Q#1 A parallel-plate capacitor (with plates A and B) has circular shape of radius 6.0 cm separated by 2.0 mm. Find the total charges on both plates (A and B) when a 12 V battery is connected. (Ans: zero)

HW **Q#2** The three capacitors in figure 5 have an equivalent capacitance of 12.4 micro-F, find the capacitance of C1. (Ans: 6.0 micro-F)

HW **Q#3**: In figure 6, a capacitor of capacitance $C = 9.0$ micro-F is charged to a potential difference $V_0 = 10.0$ volts. The charging battery is disconnected and the capacitor is connected to uncharged capacitor of unknown capacitance C_x . The potential difference across the combination is reduced to $V = 3.0$ volts. Find the value of C_x . (Ans: 21 micro-F)

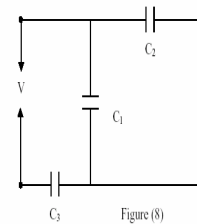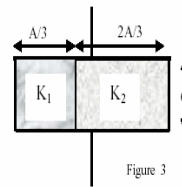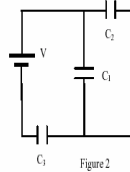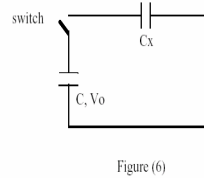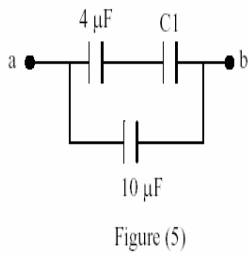Q#4 A parallel-plate capacitor has plates of area A and separation d and is charged by a battery of a potential difference V . If the charging battery is disconnected, then the work required, by external agent, to separate the plates of the capacitor to infinite distance is: [Take $A = 2.0 \text{ m}^2$, $V = 12$ Volts, $d = 3.0$ cm] (Ans: 42 nano-J.)



-----Figures T041-----

-----Figures Final-032-----

-----Figure8- Term-031

Final. Exam 032: HW **Q#1**: In figure (2), find the charge stored by the capacitor C3 if the potential difference across the battery is 10.0 V. Use the values $C_1 = C_2 = 2.0$ micro-F and $C_3 = 4.00$ micro-F. (Ans: A1 20 micro-C.)





HW **Q#2**: Two concentric spherical shells of radii 10 cm and 5.0 cm are charged to a potential difference of 20 V. How much energy is stored in this spherical capacitor? (Ans: 2.2×10^{-9} J.)

Q#3: A parallel-plate air-filled capacitor, of area 25 cm^2 and plate separation of 1.0 mm, is charged to a potential difference of 600 V. Find the energy density between the plates. (Ans: 1.6 J/m^3 .)

HW **Q#4**: A parallel-plate capacitor has an area A and a separation d . Find its capacitance if it is filled with two dielectrics as shown in figure 3. [C_0 is the capacitance of the air-filled parallel-plate capacitor. $K_1 = 3$ and $K_2 = 1.5$ are the dielectric constants] (Ans: $2 \cdot C_0$, $6 \cdot C_0$.)

T031: Q#1: Find the equivalent capacitance of three capacitors connected in series. Assume the three capacitors are: $C_1 = 2.00$ micro-F, $C_2 = 4.00$ micro-F and $C_3 = 8.00$ micro-F. (A: 1.14 micro-F.)

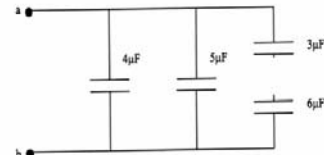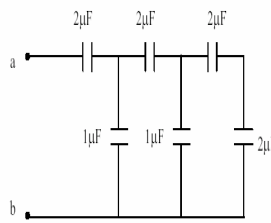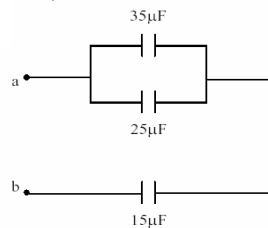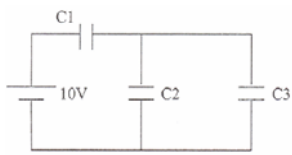HW **Q#2**: In figure (8), find the total charge stored by the three capacitors if the potential difference “V” is 10.0 volts. Assume $C_1 = 10.0$ micro-F, $C_2 = 5.00$ micro-F and $C_3 = 4.00$ micro-F (Ans: 31.6 micro-C.)



-----Fig.-5-Term-011-----

-----Fig.-5-Term-002-----

-----Fig.-6-Term-002-----

-----Fig.-3-Term-992-----

HW **Q#3:** An air filled parallel-plate capacitor has a capacitance of 1.00×10^{-12} F. The plate separation is then doubled and a wax dielectric is inserted, completely filling the space between the plates. As a result the, capacitance becomes 2.00×10^{-12} F. The dielectric constant of the wax is: (Ans: 4.00.)

Q#4: Two capacitors, C1 and C2, are connected in series and a potential difference is applied to the combination. If the capacitor that is equivalent to the combination has the same potential difference, then the charge on the equivalent capacitors is the same as: (Ans: The charge on C1 or C2.)

T-012: **Q#1** A parallel-plate capacitor has a plate area of 0.2 m^2 and a plate separation of 0.1 mm. If the charge on each plate has a magnitude of 4.0×10^{-6} C the electric field between the plates is approximately: (Ans: 2.3×10^6 V/m.)

Q#2: A 2 micro-F and a 1 micro-F capacitor are connected in series and a potential difference is applied across the combination. The 2 micro-F capacitor has: (Ans: half the potential difference of the 1 micro-F capacitor.)

HW **Q#3:** Capacitors A and B are identical. Capacitor A is charged so it stores 4 J of energy and capacitor B is uncharged. The capacitors are then connected in parallel. The total stored energy in the capacitors is now: (Ans: 2 Joules.)

T-011 **Q#1:** A 2.5 micro F capacitor, C1, is charged to a potential difference $V_1 = 10$ V using a 10 V battery. The battery is then removed and the capacitor is connected to an uncharged capacitor, C2, with capacitance of 10 micro F. What is the potential difference across C1 and C2, respectively? (Ans: 6 V, 6 V.)

Q#2: Consider an isolated capacitor of capacitance C_0 and charge Q . Which of the following statements is true when a dielectric slab is inserted between the plates of the capacitor? (Ans: The capacitance goes to zero.)

HW **Q#3:** Consider the circuit shown in figure (5). If $C_1 = 1$ micro F, $C_2 = 6$ micro F and $C_3 = 3$ micro F, what is the charge on C_3 ? (Ans: 5 micro C.)

T-002:HW **Q#1:** If V_{ab} is equal to 50 V, find the charge stored and the potential difference across the 25 micro-F capacitor shown in Figure 5 (Ans: 250 micro-C and 10 V.)

HW **Q#2:** The equivalent capacitance between points a and b in the combination of capacitors in figure 6 is: (Ans: 1.0×10^{-6} F.)

HW **Q#3:** A parallel-plate capacitor, of capacitance 1.0×10^{-9} F, is charged by a battery to a potential difference of 12.0 volts. The charging battery is then disconnected and oil with dielectric constant = 4.0 fills the inside space between the plates. The resulting potential difference, in volts, between the plates is (Ans: 3.)

T-001: **Q#1:** An isolated capacitor, $C_1 = 20.0$ micro-F has a potential difference of 26.0 V. When an uncharged capacitor C_2 , of unknown value, is connected across C_1 , the potential difference becomes 16.0 V for both. What is the value of C_2 ? (Ans: 12.5×10^{-6} F.)

Q#2: A parallel plate capacitor of capacitance C has a charge of magnitude q when connected to a battery of potential difference v . After being fully charged, the capacitor is disconnected from the battery and the separation between the plates is doubled. Which one of the following statements is TRUE? (Ans: The voltage across the plates doubles.)

T-992- HW **Q#1:** Consider the combination of capacitors in Fig. (3). The energy stored in the 5 micro-F capacitor is 0.20 J. The energy stored in 4 micro-F capacitor is: (Ans: 0.16 J.)

Q#2: An isolated capacitor, $C_1 = 20.0$ micro-F has a potential difference of 26.0 V. When an uncharged capacitor C_2 , of unknown value, is connected across C_1 , the potential difference becomes 16.0 V for both. What is the value of C_2 ? (Ans: 12.5×10^{-6} F.)

Q#3: A parallel plate capacitor of capacitance C has a charge of magnitude q when connected to a battery of potential difference V . After being fully charged, the capacitor is disconnected from the battery and the separation between the plates is doubled. Which one of the following statements is TRUE? (Ans: The voltage across the plates doubles.)