

ELECTROMOTIVE FORCE

102 ²⁸/₁

(a) What is the current in a 5.6Ω resistor connected to a battery with an 0.2Ω internal resistance if the terminal voltage of the battery is 10 V . (b) What is the \mathcal{E} of the battery?

Given $V_{\text{term}} = 10 \text{ V}$

$$R = 5.6 \Omega$$

$$r = 0.2 \Omega$$

$$I = ?$$

$$\mathcal{E} = ?$$

(a)

$$V_{\text{term}} = IR$$

$$10 = I \times 5.6$$

$$\therefore I = 10/5.6 = \boxed{1.79 \text{ A}}$$

(b)

$$I = \frac{\mathcal{E}}{R+r} \quad \text{OR} \quad V = \mathcal{E} - IR \quad \text{Eq. 28.1}$$

$$IR + IR = \mathcal{E}$$

$$V + IR = \mathcal{E}$$

$$V = \mathcal{E} - IR$$

$$10 = \mathcal{E} - 1.79(0.2)$$


$$\mathcal{E} = 10 + 0.36$$

$$\mathcal{E} = \boxed{10.36} \text{ V}$$

RESISTORS IN SERIES AND IN PARALLEL 102-28

Calculate the power dissipated in each resistor in the circuit shown in fig.

From the fig

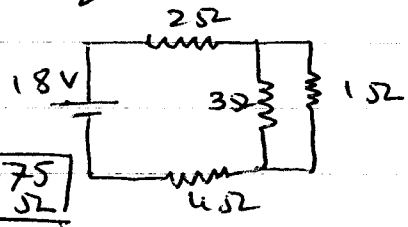

$$R_p = \frac{1}{\frac{1}{3} + \frac{1}{1}} = \frac{1+3}{3} = \frac{4}{3} = \boxed{0.75 \Omega}$$

Resistors

but $R_s = 2 + 0.75 + 4 = \underline{6.75 \Omega}$

Now $V = IR \Rightarrow I_{\text{circuit}} = \frac{V}{R_{\text{eq}}} = \frac{18}{6.75} = \boxed{2.67 \text{ A}}$

$\Rightarrow P = IV, \Rightarrow P = I^2 R$

$\Rightarrow P_{2\Omega} = (2.67)^2 (2) = \boxed{14.25 \text{ W}}$ This is power dissipated across 2Ω resistor.

$P_{4\Omega} = (2.67)^2 (4) = \boxed{28.5 \text{ W}}$ Power across 4Ω resistor.

Now to find power for 3Ω and 1Ω resistors, which are in parallel. In this case first find voltage for series resistors, since for series resistors I is same but V is different, and vice versa for parallel resistors.

$V_2 = IR = 2.67 \times 2 = \underline{5.34 \text{ V}}$

$V_4 = IR = 2.67 \times 4 = \underline{10.68 \text{ V}} \Rightarrow V_2 + V_4 = 16 \text{ V}$

\Rightarrow Voltage across 3Ω and 1Ω resistors

$18 - 16 = 2 \text{ V} = V_3 \text{ and } = V_1$, since for parallel resistors

I across 3Ω and 1Ω V is the same.

$V = IR \Rightarrow 2 = I_3 \times 3 \Rightarrow I_3 = \underline{0.67 \text{ A}}$

And $2 = I_1 \times 1 \Rightarrow I_1 = \underline{2 \text{ A}}$

P.T.O

$$P = I^2 R$$

$$\Rightarrow P_3 = (0.67)^2 (3) = \boxed{1.33 \text{ W}} \text{ through } 3 \Omega$$

$$P_1 = I_1^2 R = (2)^2 (1) = \boxed{4.0 \text{ W}} \text{ through } 1 \Omega$$


$$P_{\text{Total power}} = P_1 + P_2 + P_3 + P_4 = 4.0 + 14.25 + 1.33 + 28.5$$

$$P_{\text{Tot.}} = 48 \text{ W}$$

$$\text{Now } P = IV = 2.67 \times 18 = \boxed{48 \text{ W}}$$

RESISTORS IN SERIES AND IN PARALLEL 28 102 - 2

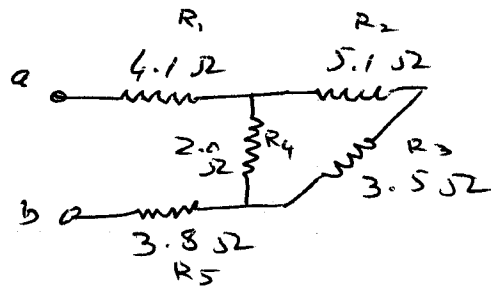Find the equivalent resistance between points a and b in given figure 28.29



Sol let $R_s = R_2 + R_3$

$$R_s = 5.1 \Omega + 3.5 \Omega = 8.6 \Omega$$

Now $R_p = \frac{2 \times 8.6}{2 + 8.6} = \frac{1}{R_4} + \frac{1}{R_s}$

$$R_p = \frac{17.2}{10.6} = \boxed{1.62}$$

Therefore $R_{\text{net}} = 3.8 + 4.1 + 1.62$

$$= \boxed{9.52 \Omega}$$

$$\begin{aligned} \frac{1}{R_p} &= \frac{1}{R_4} + \frac{1}{R_s} \\ &= \frac{1}{2.0} + \frac{1}{8.6} \\ &= \frac{8.6 + 2}{2 \times 8.6} \\ \frac{1}{R_p} &= \frac{10.6}{17.2} \\ R_p &= \frac{17.2}{10.6} = 1.62 \end{aligned}$$

$$V = IR$$


$$I = \frac{V}{R} = \frac{10}{9.52} = 1.05 \text{ A}$$

$$W = IV = 1.05 \times 10 = 10.5 \text{ W}$$

KIRCHHOFF'S RULES

102 $\frac{28}{3}$

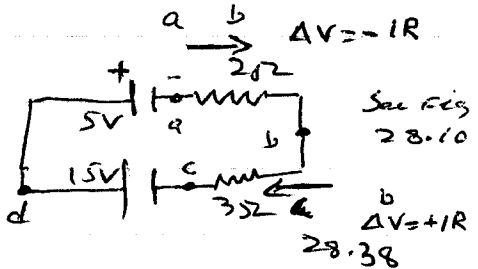Two batteries and two resistors are connected in the single loop shown in figure 28.38. Given that the potential at point 'd' equals zero, determine the potentials at points (a) a, (b) b, (c) c.



Using Kirchhoff's law, calculate around the loop.

$$-5V - I(2\Omega) - I(3\Omega) + 15V = 0$$

$$I = \frac{10V}{5\Omega} = \boxed{2A}$$

$$-(-15V) + 15V = 0$$

$$(a) \quad V_a = -5V$$

$$(b) \quad V_b = -5V - 2A \times 2\Omega = -9V$$

$$(c) \quad V_c = -5V - 2A \times 2\Omega - 2A \times 3\Omega = \boxed{-15V}$$

RC CIRCUITS

102 $\frac{28}{4}$

A 4-M Ω resistor and a 3- μ F capacitor are connected in series with a 12-V power supply.

- (a) What is the time constant for the circuit?
 (b) Express the current in the circuit and charge on the capacitor as a function of time.

$$R = 4 \text{ M}\Omega = 4 \times 10^6 \Omega$$

$$C = 3 \times 10^{-6} \text{ F}$$

$$\mathcal{E} = 12 \text{ V}$$

(a) $\tau = RC = 4 \times 10^6 \times 3 \times 10^{-6} = \boxed{12 \text{ s}}$

(b)

$$i(t) = \frac{\mathcal{E}}{R} e^{-t/RC} \quad \text{eq. 28.13}$$

$$= \frac{12}{4 \times 10^6} e^{-t/12}$$

$$\boxed{i = 3 \times 10^{-6} e^{-t/12} \text{ A}}$$

$$q(t) = C\mathcal{E} (1 - e^{-t/RC}) \quad \text{eq. 28.14}$$

$$= 3 \times 10^{-6} \times 12 (1 - e^{-t/12})$$

$$\boxed{q(t) = 36 \times 10^{-6} (1 - e^{-t/12}) \text{ C}}$$