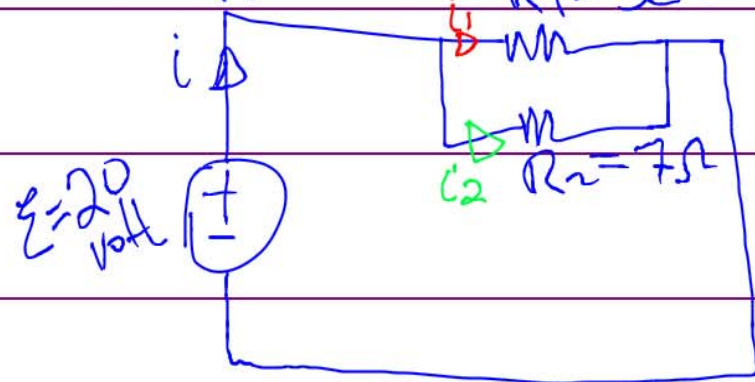


$$i_k = \left( \frac{G_k}{\sum_{j=1}^n G_{ij}} \right) i$$

conductance  
 $G_k = \frac{1}{R_k}$



$$i_1 = \frac{7}{10} \times i = 0.7 \times 9.5 = 6.65 \text{ A}$$

$$i_2 = \left( \frac{3}{3+7} \right) i$$

$$= 0.3 \times 9.5 = 2.85 \text{ A}$$

parallel

KCL  $i_1 + i_2 - i = 0$


$$i_1 = i - i_2 = 9.5 - 2.85 = 6.65 \text{ A}$$

$$R_p = \frac{R_1 R_2}{R_1 + R_2} = \frac{3 \times 7}{3 + 7} = 2.1 \Omega$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_p} = \frac{R_2 + R_1}{R_1 R_2}$$

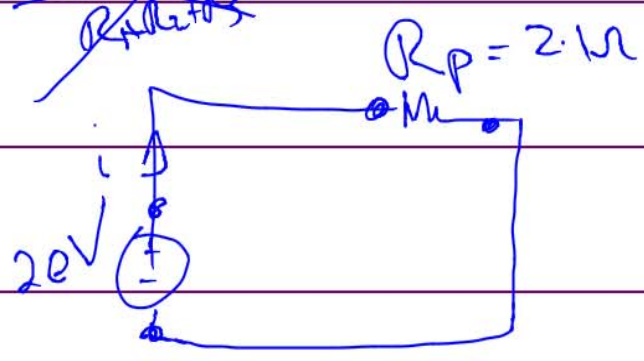
~~$R_p = \frac{R_1 R_2 R_3}{R_1 + R_2 + R_3}$~~



$$R_p i = V$$

$$2.1 \times i = 20$$

$$i = \frac{20}{2.1} = 9.5 \text{ A}$$

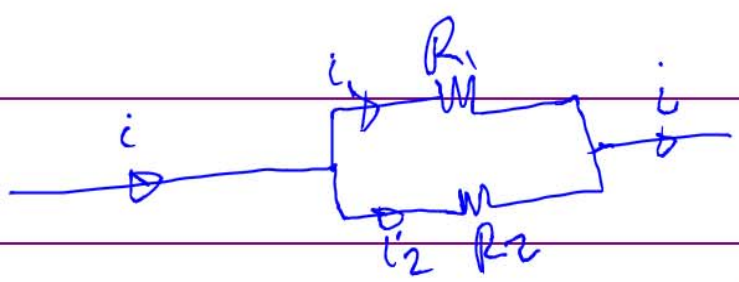

$$i_2 = \left( \frac{R_1}{R_1 + R_2} \right) i$$

$$i_1 = \left( \frac{R_2}{R_1 + R_2} \right) i$$