

parallel plate capacitor


$$C = \frac{\epsilon_0 A}{d}$$

$$\frac{V}{A} \equiv U$$

النفاذية permeability  $\mu_0 = 4\pi \times 10^{-7}$


$\epsilon_0 = 8.85 \times 10^{-12}$  Permittivity

$$\frac{P \cdot S}{J} = U$$

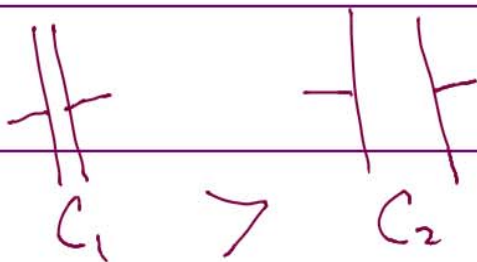

$$C_1 = \frac{\epsilon_0 A}{d_1}$$

$$C_2 = \frac{\epsilon_0 A}{d_2}$$

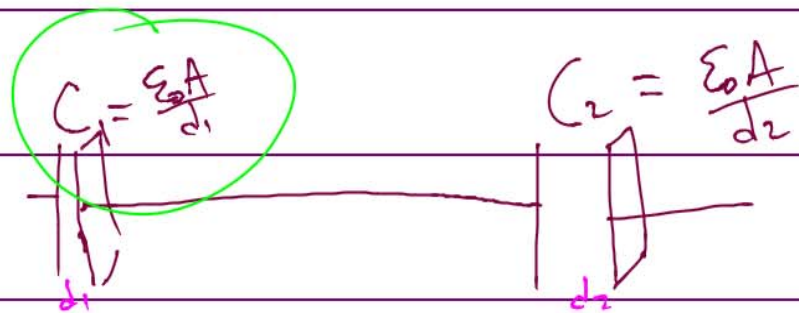

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$


$$\frac{1}{C_{eq}} = \frac{C_1 + C_2}{C_1 C_2}$$

$$C_{eq} = \frac{\epsilon_0 A / d_1 + \epsilon_0 A / d_2}{\epsilon_0 A / d_1 + \epsilon_0 A / d_2} = \frac{\epsilon_0 A}{d_1 + d_2}$$

$$\frac{1}{d_1 + d_2}$$

$$\frac{1}{d_1} + \frac{1}{d_2} = \frac{1}{d_1 d_2}$$
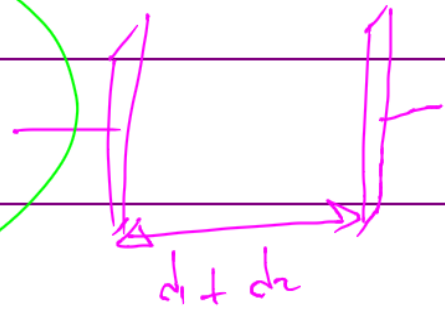
$$C_{eq} = \frac{\epsilon_0 A}{d_1 + d_2}$$




S, ϕ

$$C_s^{-1} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$R_s^{-1} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$C_p = C_1 + C_2$$



$$R_s = R_1 + R_2$$

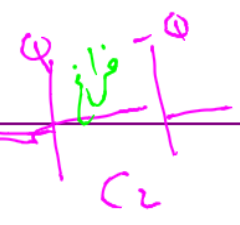

$$C = \frac{\epsilon_0 A}{d}$$



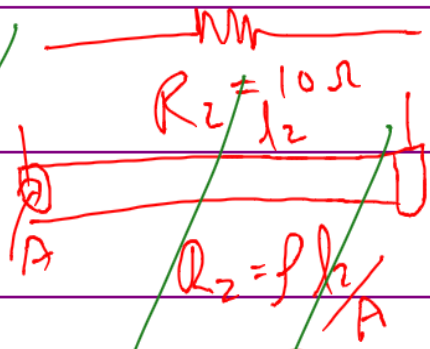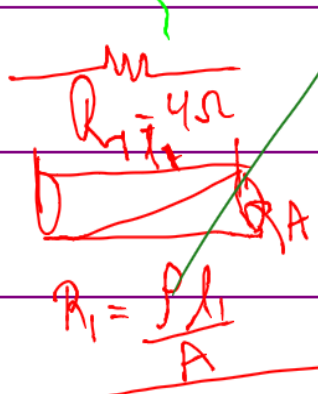
$$C_{eq} = \frac{\epsilon_0 A}{d_1 + d_2}$$




$$R_1 = \frac{\rho l_1}{A}$$

$$R_2 = \frac{\rho l_2}{A}$$

$$R_{eq} = R_1 + R_2$$

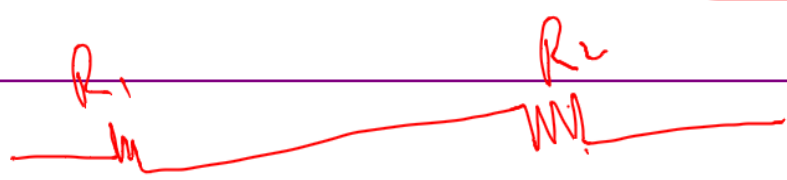


$$C = \frac{\epsilon_0 A}{d}$$

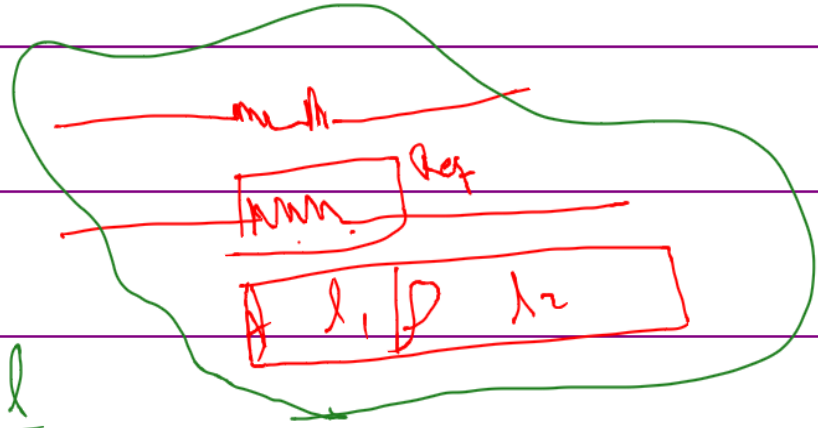


$$R = \frac{\rho l}{A}$$

ρ(A, l)    ρ(A, l)
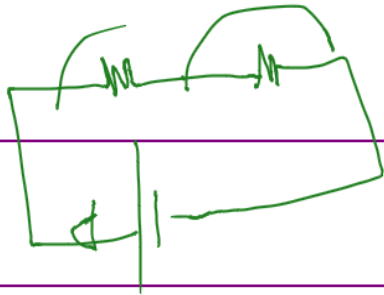
$$R_{eq} = \frac{f(d_1 + d_2)}{A} \equiv \frac{f d_1}{A} + \frac{f d_2}{A} = R_1 + R_2$$



$$R_{eq} = R_1 + R_2$$

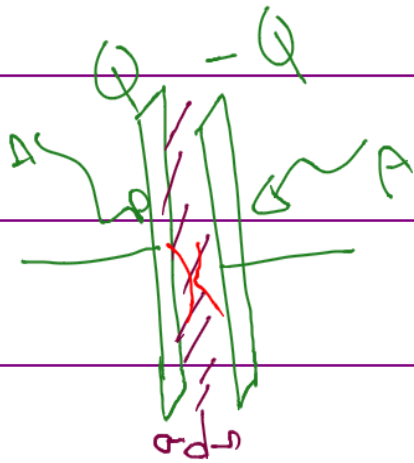

dielectric  $\chi$   
constant

$$C = \frac{\chi \epsilon_0 A}{d}$$

$$\chi_{vacuum} \equiv 1$$


$$\chi_{air} \approx 1.000293$$

$$\approx 1$$

$$\chi > 1$$



$$C = \chi \epsilon_0 A$$

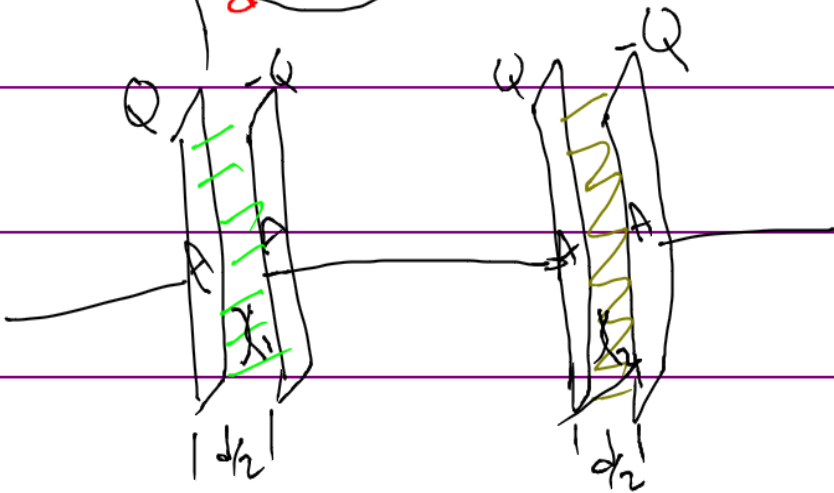

$$C_1 = \frac{K_1 \epsilon_0 A}{d/2}$$

$$C_2 = \frac{K_2 \epsilon_0 A}{d}$$


$$C_{eq} = \frac{C_1 \times C_2}{C_1 + C_2}$$

$$= \frac{2K_1 \epsilon_0 A}{d} \times \frac{2K_2 \epsilon_0 A}{d}$$

$$\frac{2K_1 K_2 \epsilon_0 A}{d (K_1 + K_2)}$$

$$C_{eq} = \frac{2K_1 K_2}{K_1 + K_2} \left( \frac{\epsilon_0 A}{d} \right) \equiv C_0$$
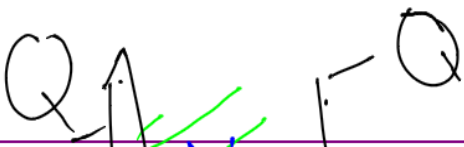
$$C_{eq} = \frac{2K_1 K_2}{K_1 + K_2} \times C_0$$






$$C_1 = \frac{\epsilon_1 \epsilon_0 A}{d}$$



$$\epsilon_0 A / d \equiv C_0$$

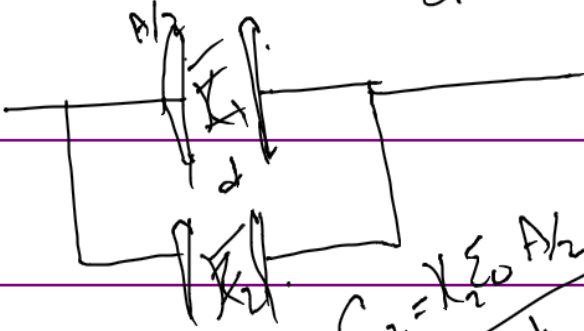

$$C_2 = \frac{\epsilon_2 \epsilon_0 A}{d}$$

$$\begin{aligned} C_{eq} &= C_1 + C_2 \\ &= \frac{\epsilon_0 A}{2d} (\epsilon_1 + \epsilon_2) \\ &= \frac{(\epsilon_1 + \epsilon_2)}{2} \frac{\epsilon_0 A}{d} \\ &= \frac{\epsilon_1 + \epsilon_2}{2} * C_0 \end{aligned}$$