

Physics-305
Homework Set (1)

This homework set is due on Monday, 16th Dhul-Qi'dah, 1436 (Aug. 31st, 2015) at 10.00 p.m. [slip under my Office (15-3100) door, if needed]

For this homework set in particular, please do not discuss with your colleagues; rather, e-mail me or call me if you need help

Start each question on a new page. Please solve fully and clearly, state assumptions, circle final answers, and comment wisely (when applicable).

Question #1:

Two point charges, $q_1 = +4 \mu\text{C}$ and $q_2 = -2 \mu\text{C}$, are fixed on the x axis, as shown in **Figure 1**. Which of the following statements regarding the electric field produced by the two charges on the x axis is CORRECT?

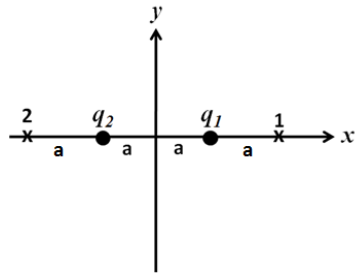


Figure 1

In which direction does the electric field point at point-1, at point-2 and in between?

Question #2:

Two charged particles are fixed in the xy plane as shown in **Figure 2**. Take $q_1 = 10 \text{ nC}$, $q_2 = -30 \text{ nC}$, and $a = 1.0 \text{ m}$. What is the electric potential due to these two particles at the origin?

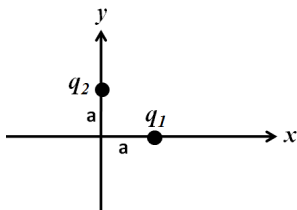


Figure 2
Question #3:

A certain resistor dissipates 0.50 W when connected to a 3.0-V potential difference. How much will the same resistor dissipate when connected to a 1.0-V potential difference?

Question #4:

In order to store a total of 0.040 J of energy in the two identical capacitors shown in **Figure 3**. What should the capacitance (C) be?

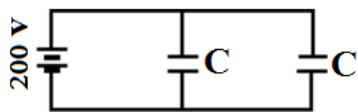


Figure 3

Question #5:

A $10\text{-}\Omega$ resistor has a constant current passing through it. If 1200 C of charge flow through it in 4.0 minutes, what is the potential difference across the resistor?

Question #6:

Resistor 1 has twice the resistance of resistor 2. They are connected in parallel to a battery. If the power dissipated in R_1 is P_1 and the power dissipated in R_2 is P_2 , what is P_1/P_2 ?

Question #7:

Find the current in $8.00\text{-}\Omega$ resistor in the circuit shown in **Figure 4**?

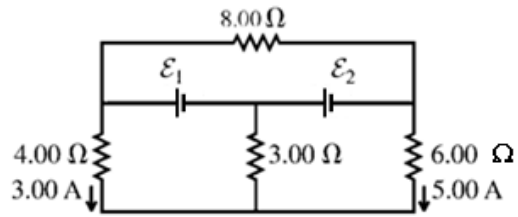


Figure 4

Question #8:

The capacitor shown in **Figure 5** is initially charged. Switch S is closed at time $t = 0$. At the end of $10.0\ \text{ms}$, the charge on the capacitor is one third the initial value. If the resistor $R = 910\ \text{ohm}$, what must the capacitance be?

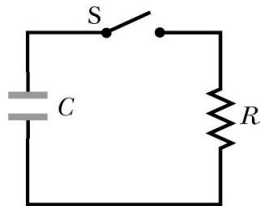


Figure 5