

**Systems Engineering Department**  
**SE 311: Design of Digital Systems**  
**Term 041 Dr. Al-Amer Quiz 1**

Name : \_\_\_\_\_ ID#: \_\_\_\_\_

**Instructions: Answer all questions and show all details**

Obtain a simplified Boolean expression for the outputs F and G in terms of the input variables.

