

SE311: Design of Digital Systems

Lecture 10: XOR

Dr. Samir Al-Amer
(Term 041)

Outlines

- NAND and NOR Implementations
- two level Implementations
- Multi-level NAND circuits
- NOR Implementations
- Other Two level implementations
- Exclusive OR Function
- Parity Checking

NAND and NOR Implementations

- Digital circuits are often implemented using NAND or NOR gates rather than AND-OR gates
- NAND or NOR gates are
 - Easier to manufacture
 - Universal gates (can be used to implement to logic function)
 - They are the basic gates in IC digital families




NAND Gate is a Universal Gate

- We can use NAND gates to implement any Boolean function
- We can implement any function using AND, OR, NOT and we will show that we can implement them using NAND gates





We often use this symbol to represent the single input NAND gate

NAND Gate is a Universal Gate

   

AND operation can be implemented using NAND gated

NAND Gate is a Universal Gate

  

OR operation can be implemented using NAND gated




NOR Gate is a Universal Gate

- We can use NOR gates to implement any Boolean function
- We can implement AND, OR, NOT using NOR gates





We often use this symbol to represent the single input NOR gate

NOR Gate is a Universal Gate

   


OR operation can be implemented using NOR gates

NAND Gate is a Universal Gate

  


AND operation can be implemented using NOR gates

NAND Circuits

 

 Standard symbol for
NAND gate
(AND-Invert)



Alternative symbol for
NAND gate
(Invert-OR)

NAND gate Implementations

- Any Boolean function can be implemented using 2-level NAND gates

Procedure:

1. Simplify $F(\cdot)$ as the sum of product form
2. Draw NAND gate for each term that has two literals or more.
3. Draw a single gate using AND-invert or Invert-OR in the second levels with inputs coming from first level.
4. A single literal term needs inverter in the first level (unless it appears in the complement form)

Summary

- NAND and NOR Implementations
- two level Implementations
- Multi-level NAND circuits
- NOR Implementations
- Other Two level implementations
- Exclusive OR Function
- Parity Checking