

# SE311: Design of Digital Systems

## Lecture 9: NAND and NOR Implementations

---

Dr. Samir Al-Amer  
(Term 041)

# Outlines

---

- NAND and NOR Implementations
- two level Implementations
- Multi-level NAND circuits
- NOR Implementations
- Other Two level implementations
- Exclusive OR Function
- Parity Checking

# NAND and NOR Implementations

---

- Digital circuits are often implemented using NAND or NOR gates rather than AND-OR gates
- NAND or NOR gates are
  - Easier to manufacture
  - Universal gates ( can be used to implement to logic function)
  - They are the basic gates in IC digital families

# NAND Gate is a Universal Gate




- We can use NAND gates to implement any Boolean function
- We can implement any function using AND, OR, NOT and we will show that we can implement them using NAND gates



We often use this symbol to represent the single input NAND gate

# NAND Gate is a Universal Gate



---

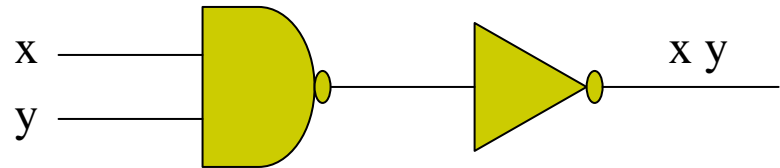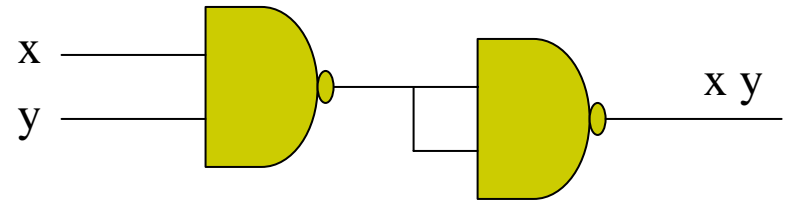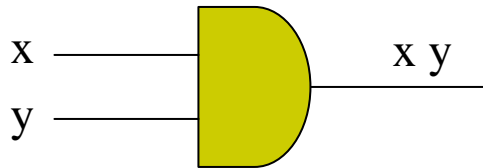

AND operation can be implemented using NAND gated

# NAND Gate is a Universal Gate

---

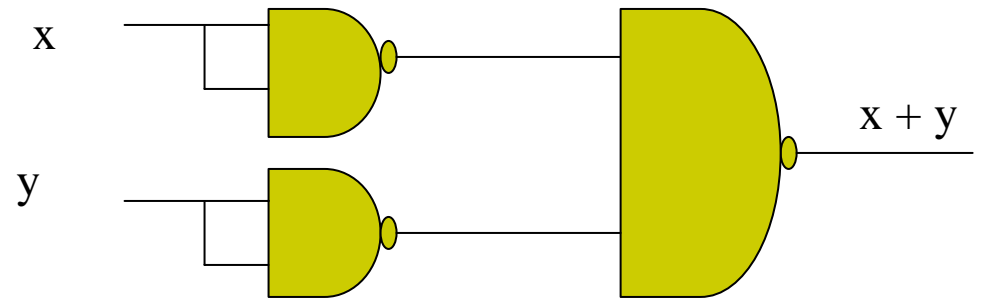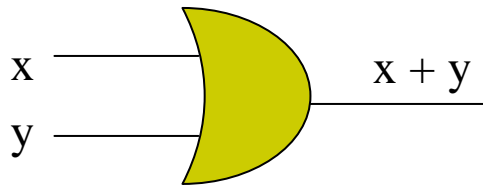

OR operation can be implemented using NAND gated

# NOR Gate is a Universal Gate




- We can use NOR gates to implement any Boolean function
- We can implement AND, OR, NOT using NOR gates



We often use this symbol to represent the single input NOR gate

# NOR Gate is a Universal Gate

---

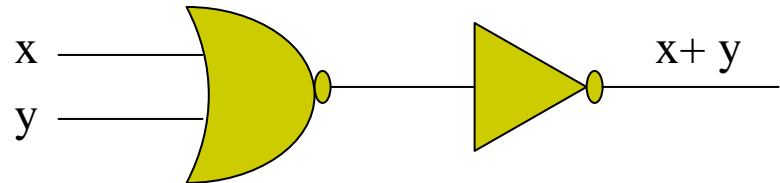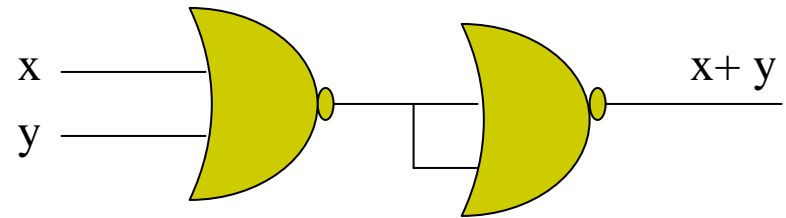
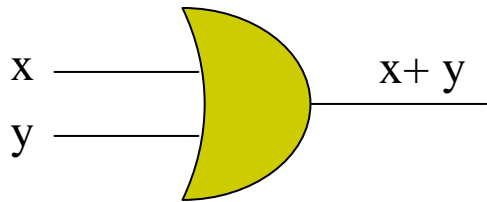


OR operation can be implemented using NOR gates



# NAND Gate is a Universal Gate


---

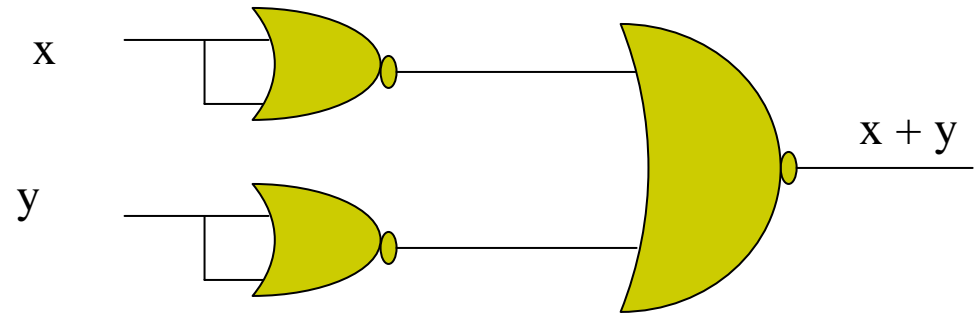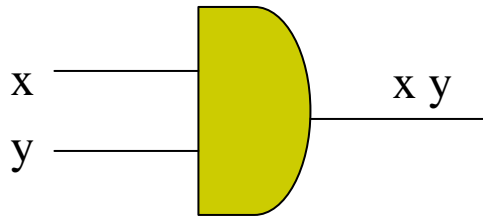


AND operation can be implemented using NOR gates

# NAND Circuits

---

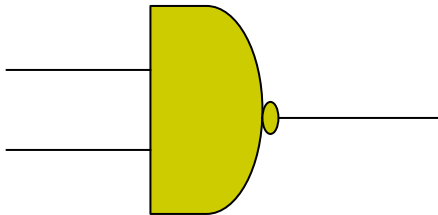

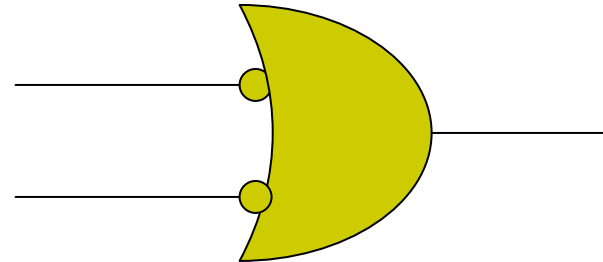Standard symbol for  
NAND gate  
(AND-Invert)



Alternative symbol for  
NAND gate  
(Invert-OR)

# NAND gate Implementations

---


- Any Boolean function can be implemented using 2-level NAND gates

Procedure:

1. Simplify  $F(\cdot)$  as the sum of product form
2. Draw NAND gate for each term that has two literals or more.
3. Draw a single gate using AND-invert or Invert-OR in the second levels with inputs coming from first level.
4. A single literal term needs inverter in the first level (unless it appears in the complement form)


# Implement using NAND gates

---

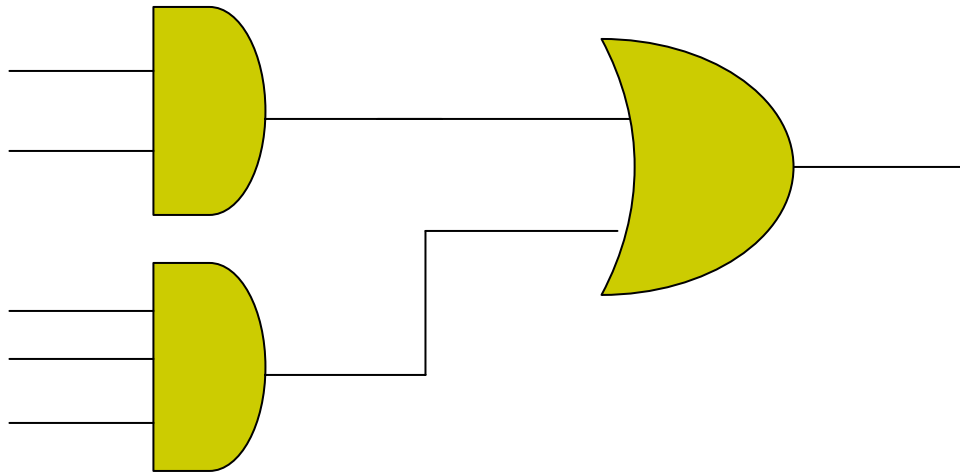


# NAND Circuits

---

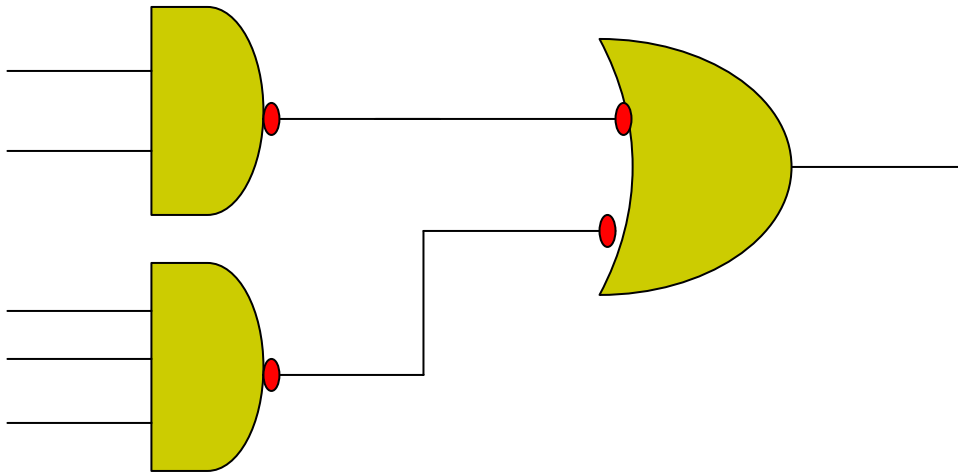


# NAND Circuits

---

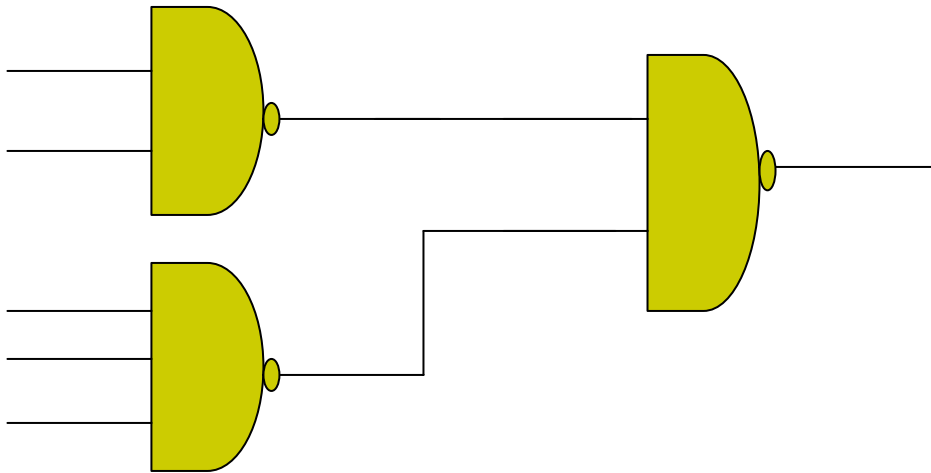


# Implement using NAND gates

---

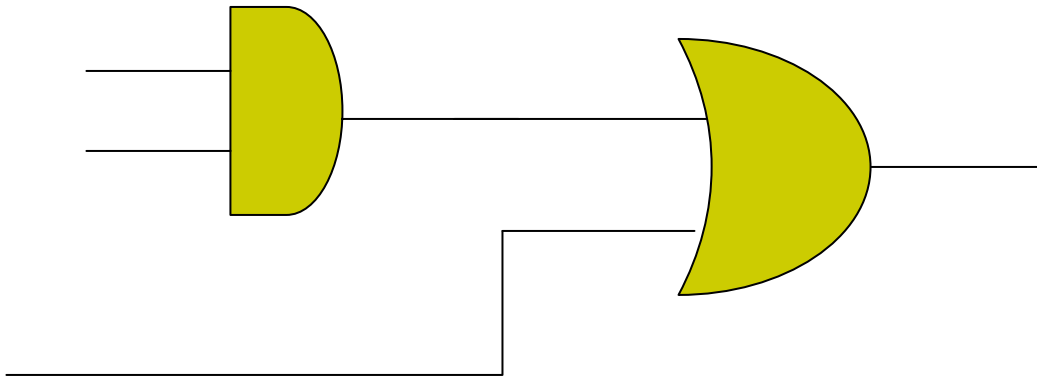

# Implement using NAND gates

---

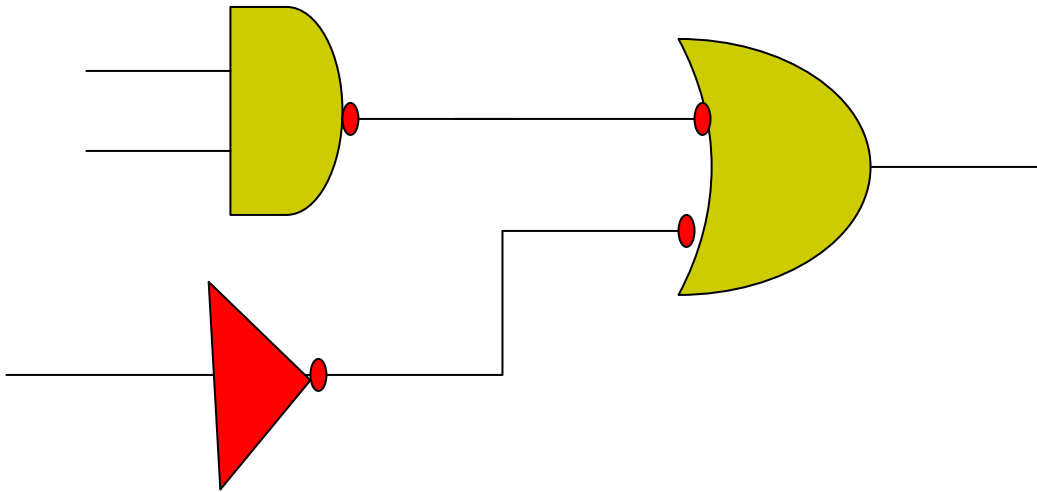



# Summary

---

- NAND and NOR Implementations
- two level Implementations
- Multi-level NAND circuits
- NOR Implementations
- Other Two level implementations
- Exclusive OR Function
- Parity Checking