 


# 6.111 Lecture 10

## Today: Memories

1. Static RAMs
2. Interfacing: Bus & Protocol
3. Synchronous Memories
4. EPROMs and DRAMs
5. Memory Mapped Peripherals



*Acknowledgement: Nathan Ickes, Rex Min*


J. Rabaey, A. Chandrakasan, B. Nikolic, "Digital Integrated Circuits: A Design Perspective"  
Prentice Hall, 2003 (Chapter 10)

# Memories of a Digital World

**Why need memories?** State machines...
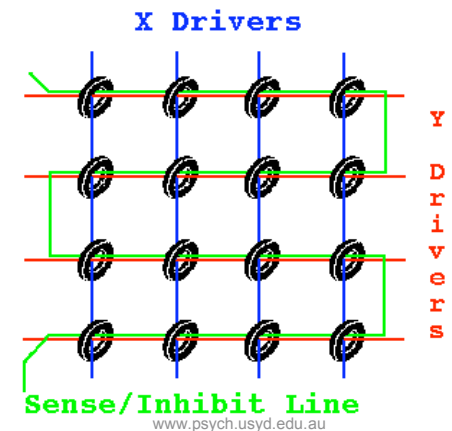
## Memories:

- **Flip Flips, Registers, FIFO** (first-in-first-out)
- **Core memory!**
- **Random Access** (static/dynamic, read/write)
- **Slow / Non-volatile** (hard drive/eeprom/eprom)
- **Content-addressable**
- **Concept of a BUS and use of TRISTATE!**



## Key Design Metrics:

1. **Memory Density** (number of bits/ $\mu\text{m}^2$ ) and **Size**
2. **Access Time** (time to read or write) and **Throughput**
3. **Power Dissipation**

# Memory Classification & Metrics


Read-Write Memory		Non-Volatile Read-Write Memory	Read-Only Memory (ROM)
Random Access	Non-Random Access	EPROM E <sup>2</sup> PROM	Mask-Programmed
SRAM DRAM	FIFO LIFO	FLASH	

## Key Design Metrics:


1. Memory Density (number of bits/ $\mu\text{m}^2$ ) and Size
2. Access Time (time to read or write) and Throughput
3. Power Dissipation

# 1. Static RAMs: Latch Based Memory

## Set Reset Flip Flop

 


## Register Memory

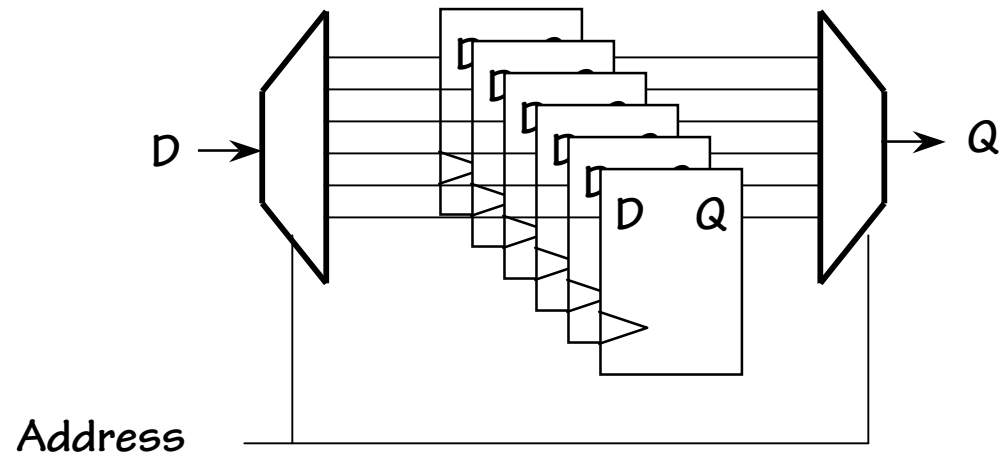


- Works fine for small memory blocks (e.g., small register files)
- Inefficient in area for large memories
- Density is the key metric in large memory circuits

*How do we minimize cell size?*

# Memory Array Architecture

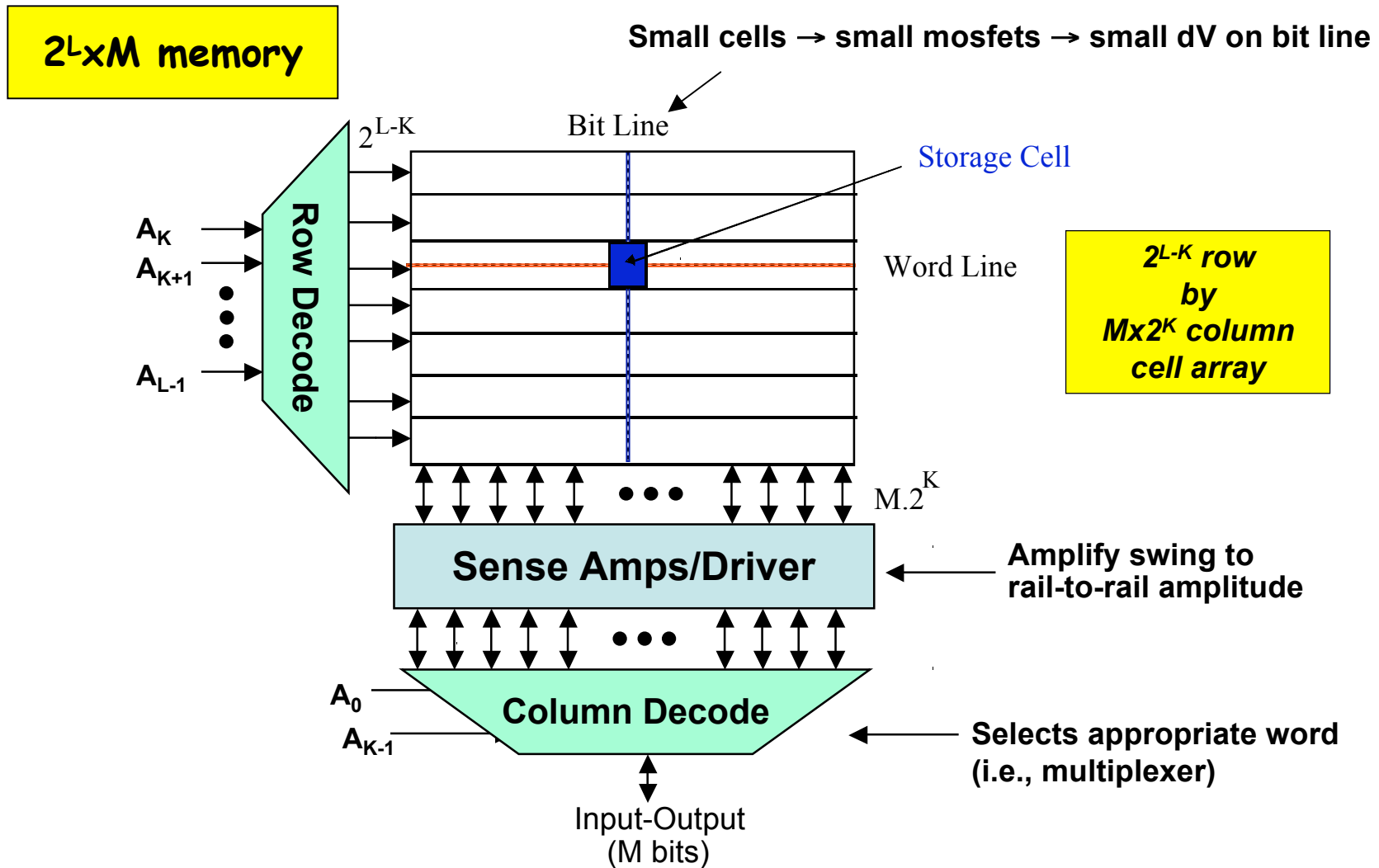

# Static RAM (SRAM) Cell (The 6-T Cell)

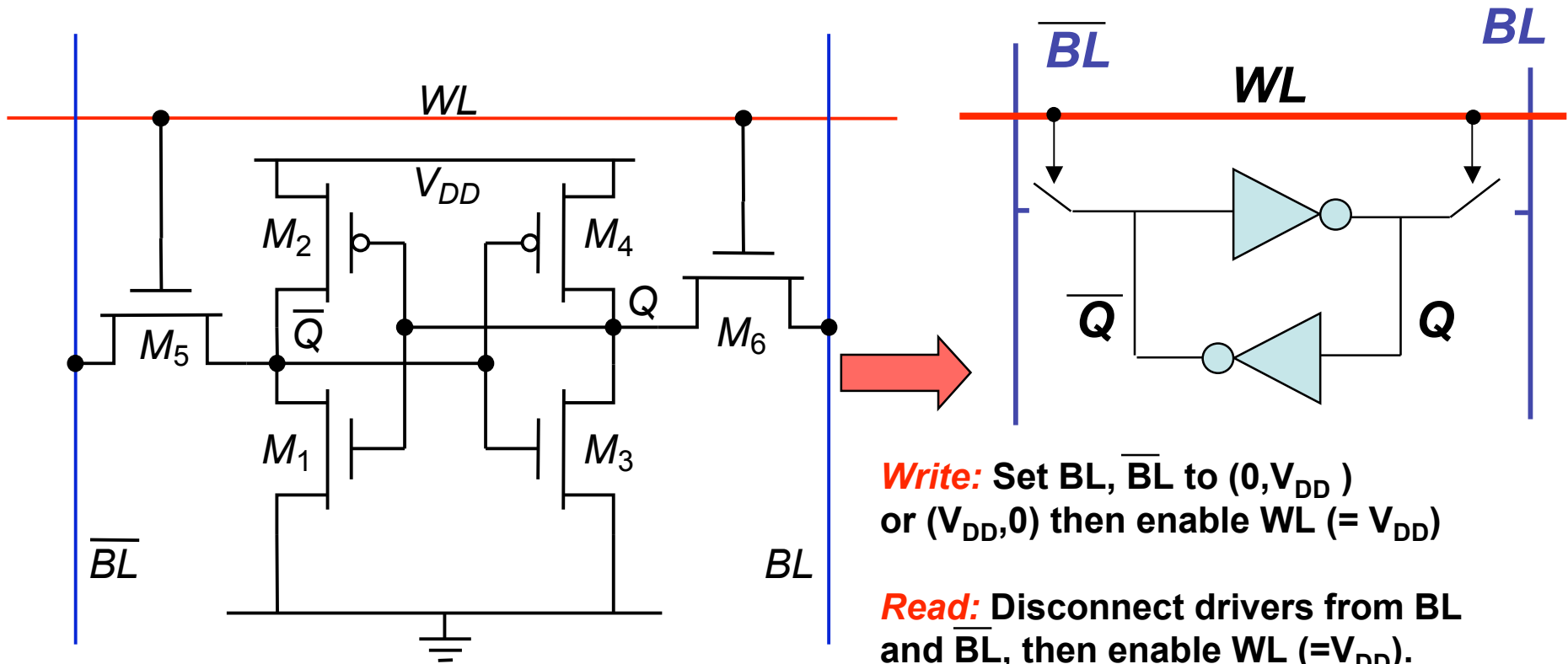


**Write:** Set  $BL, \overline{BL}$  to  $(0, V_{DD})$  or  $(V_{DD}, 0)$  then enable  $WL (= V_{DD})$

**Read:** Disconnect drivers from  $BL$  and  $\overline{BL}$ , then enable  $WL (= V_{DD})$ . Sense a small change in  $BL$  or  $\overline{BL}$

- **State held by cross-coupled inverters (M1-M4)**
- **Retains state as long as power supply turned on**
- **Feedback must be overdriven to write into the memory**


## 2. Using External Memory Devices

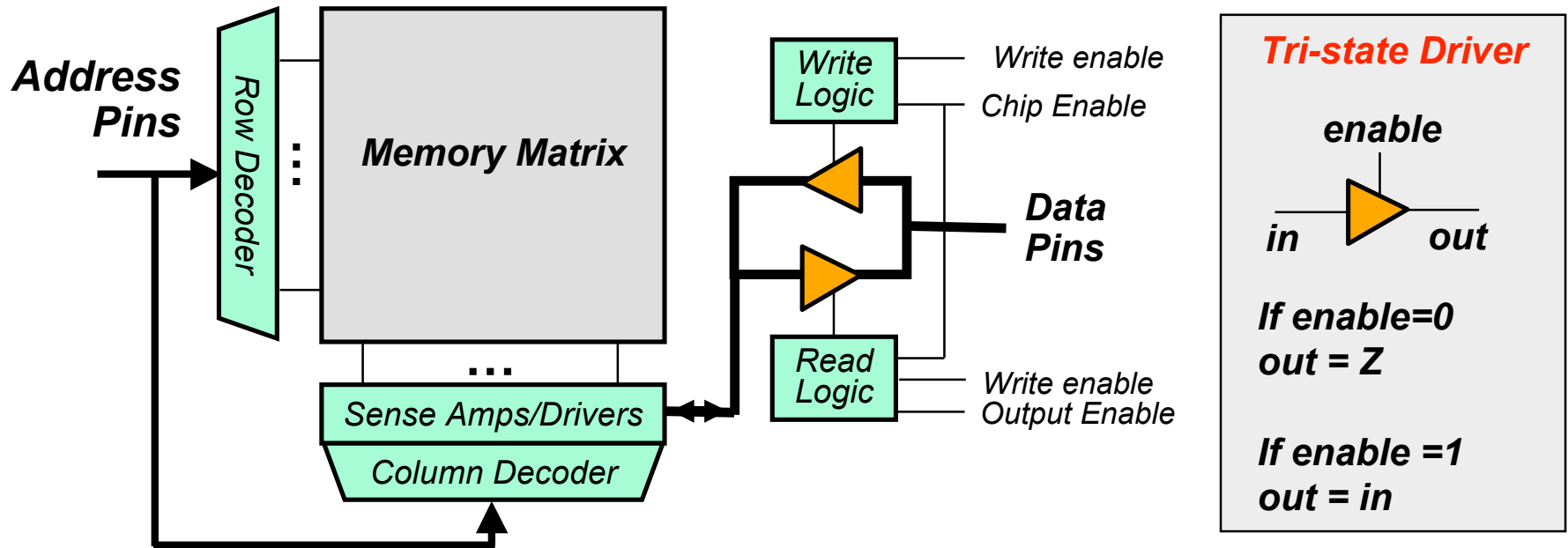

- **Address** pins drive row and column decoders
  - **Data** pins are **bidirectional**: shared by reads and writes
  - **Output Enable** gates the chip's tristate driver
  - **Write Enable** sets the memory's read/write mode
  - **Chip Enable/Chip Select** acts as a "master switch"
- Concept of "Data Bus"

# MCM6264C 8K x 8 Static RAM

**On the outside:**

 

Same (bidirectional) data bus used for reading and writing

**Chip Enables ( $\overline{E1}$  and  $\overline{E2}$ )**

$\overline{E1}$  must be low and  $\overline{E2}$  must be high to enable the chip


**Write Enable ( $\overline{WE}$ )**

When low (and chip enabled), values on data bus are written to location selected by address bus


**Output Enable ( $\overline{OE}$  or  $\overline{G}$ )**

When low (and chip is enabled), data bus is driven with value of selected memory location

**On the inside:**

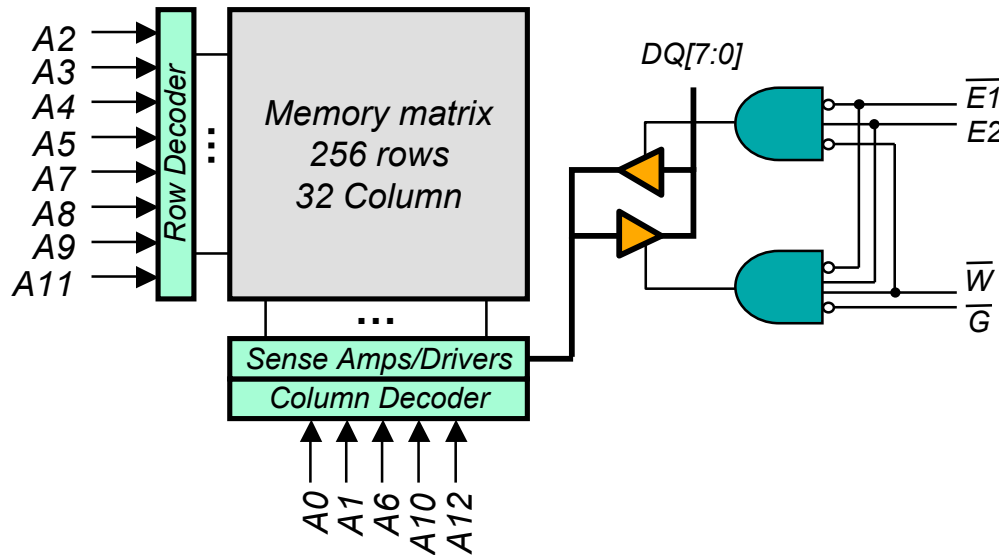


**Pinout**

 




# Reading an Asynchronous SRAM

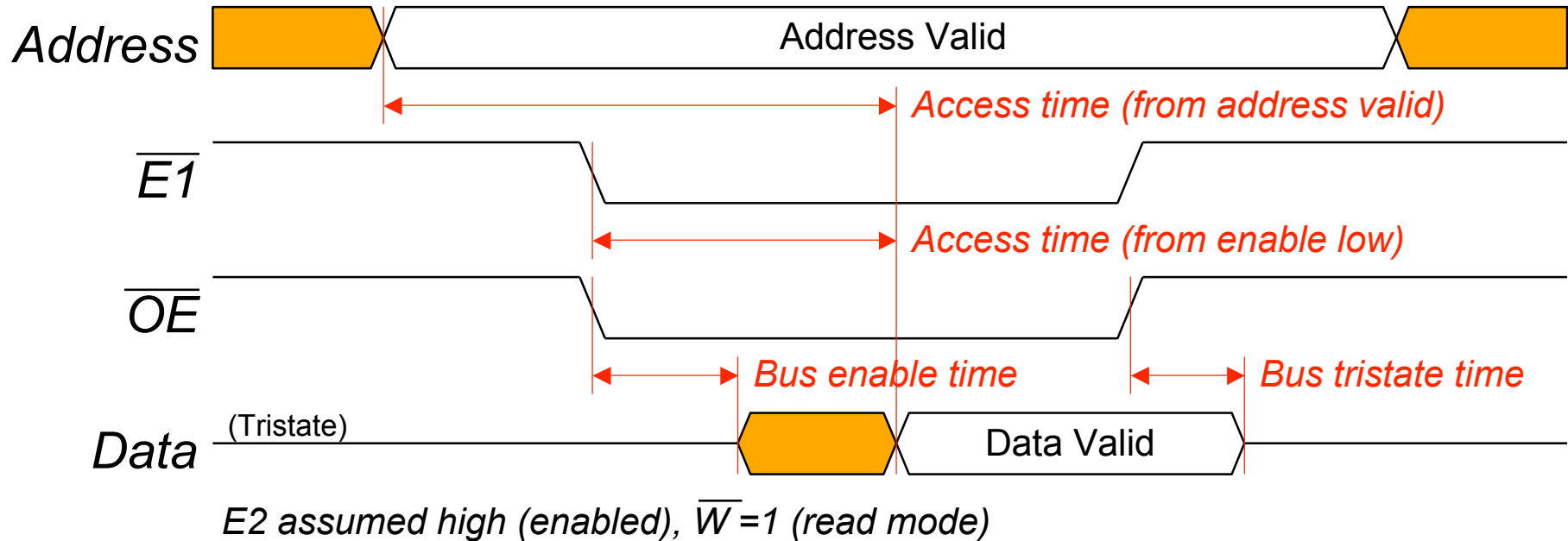


- Read cycle begins when all enable signals ( $\overline{E1}$ ,  $\overline{E2}$ ,  $\overline{OE}$ ) are active
- Data is valid after read access time
  - Access time is indicated by full part number: *MCM6264CP-12* → 12ns
- Data bus is tristated shortly after  $\overline{OE}$  or  $\overline{E1}$  goes high

# Address Controlled Reads

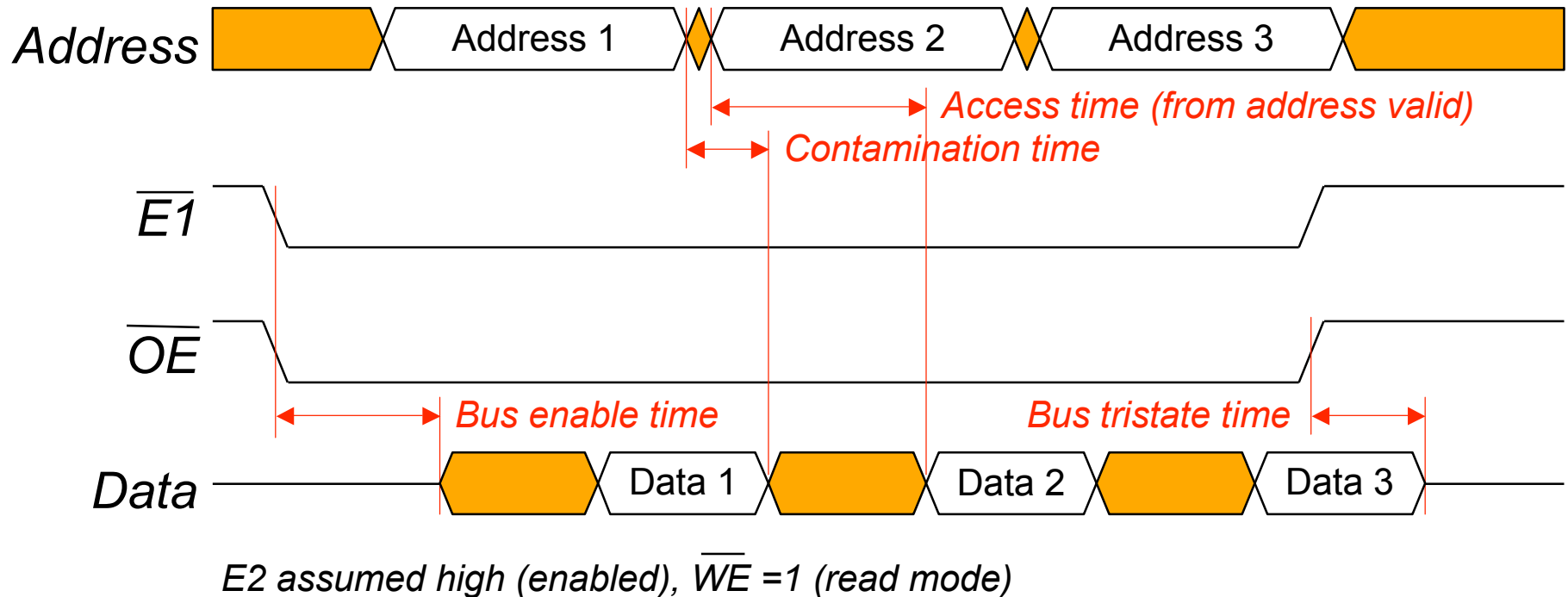


- Can perform multiple reads without disabling chip
- Data bus follows address bus, after some delay

# Writing to Asynchronous SRAM

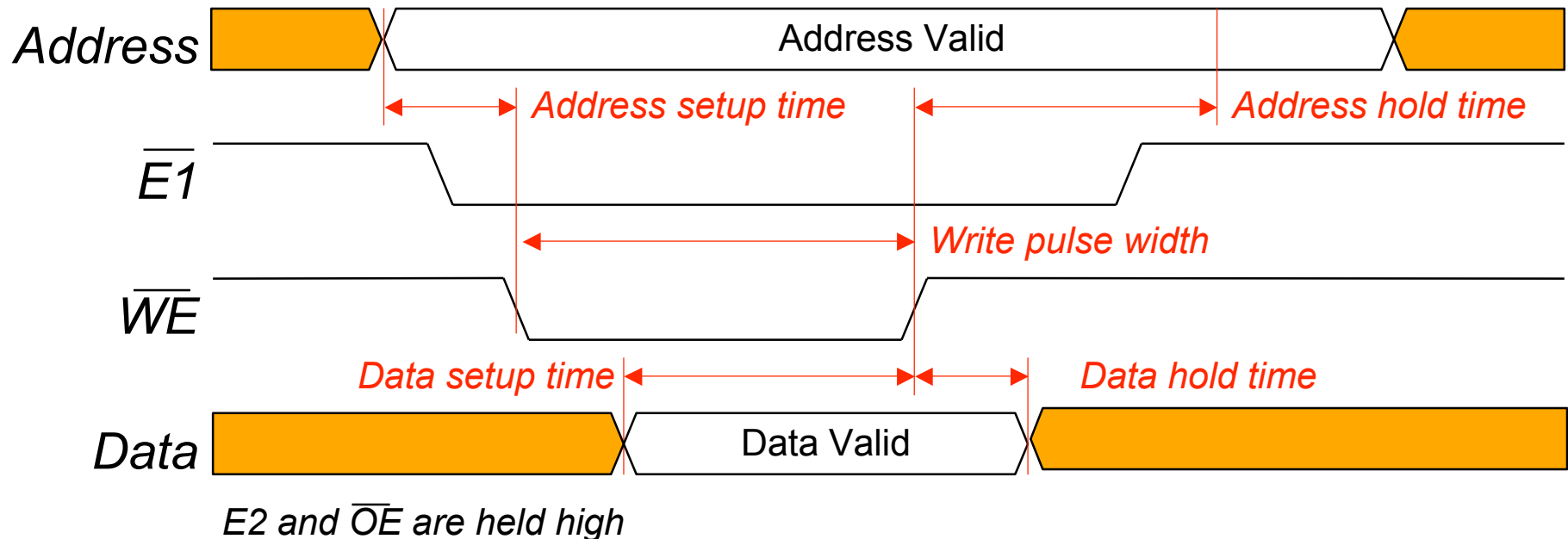


- **Data latched when  $\overline{WE}$  or  $\overline{E1}$  goes high (or E2 goes low)**
  - Data must be stable at this time
  - Address must be stable before  $\overline{WE}$  goes low
- **Write waveforms are more important than read waveforms**
  - **Glitches to address can cause writes to random addresses!**

# Sample Memory Interface Logic

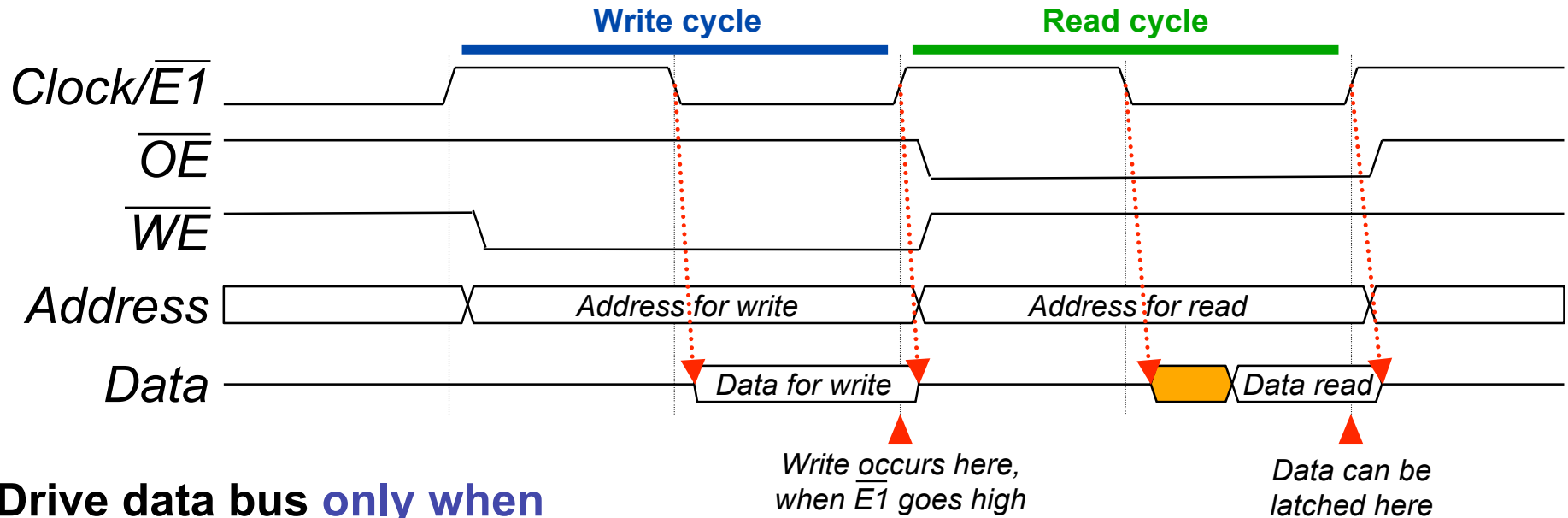


Drive data bus **only when clock is low**

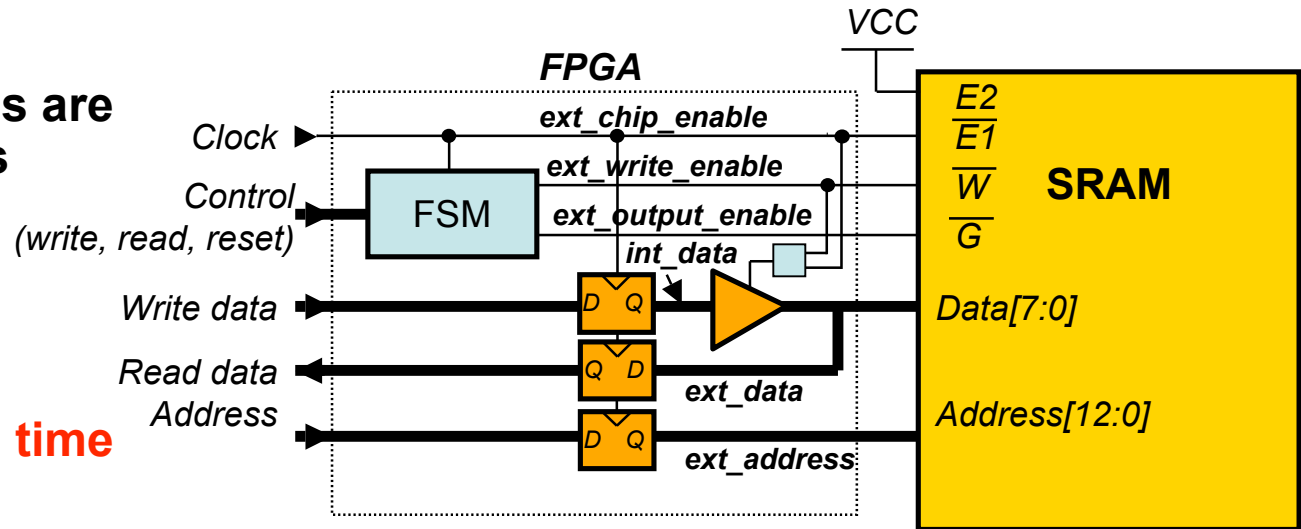- Ensures address are stable for writes
- Prevents bus contention
- **Minimum clock period is twice memory access time**



# Tristate Data Buses in Verilog

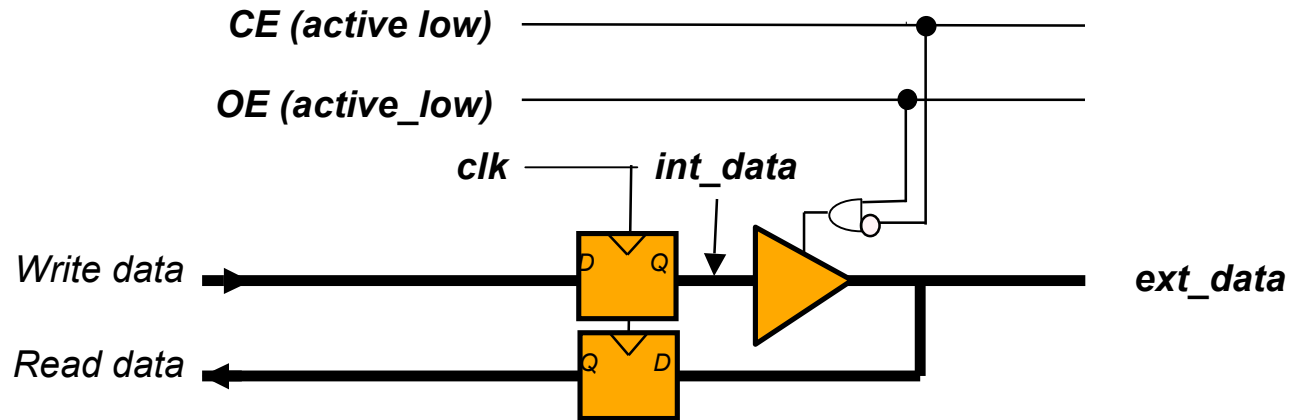


```
output CE,OE; // these signals are active low
inout [7:0] ext_data;
reg [7:0] read_data,int_data
wire [7:0] write_data;

always @ (posedge clk) begin
    int_data <= write_data;
    read_data <= ext_data;
end

// Use a tristate driver to set ext_data to a value
assign ext_data = (~CE & OE) ? int_data : 8'hZZ;
```

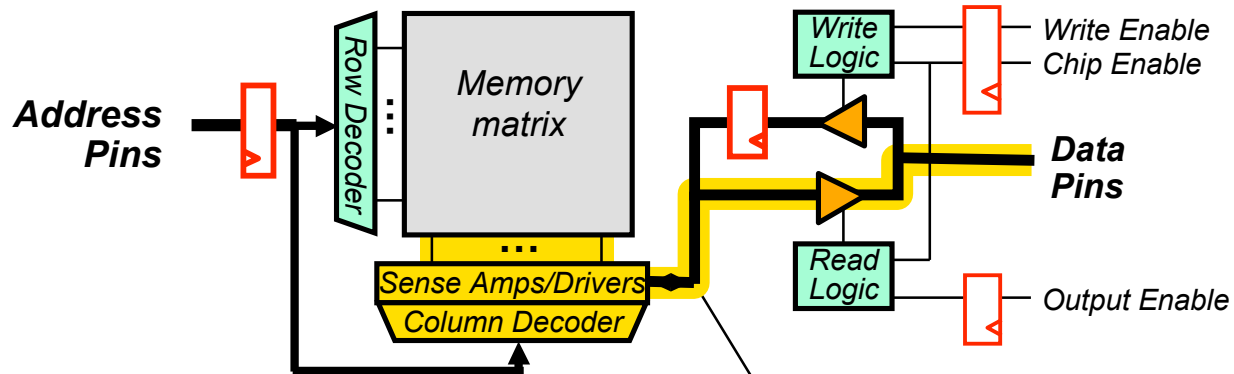
# 3. Synchronous SRAM Memories

- **Clocking** provides input synchronization and encourages more reliable operation at high speeds




*difference between read and write timings creates wasted cycles ("wait states")*

 *long "flow-through" combinational path creates high CLK-Q delay*



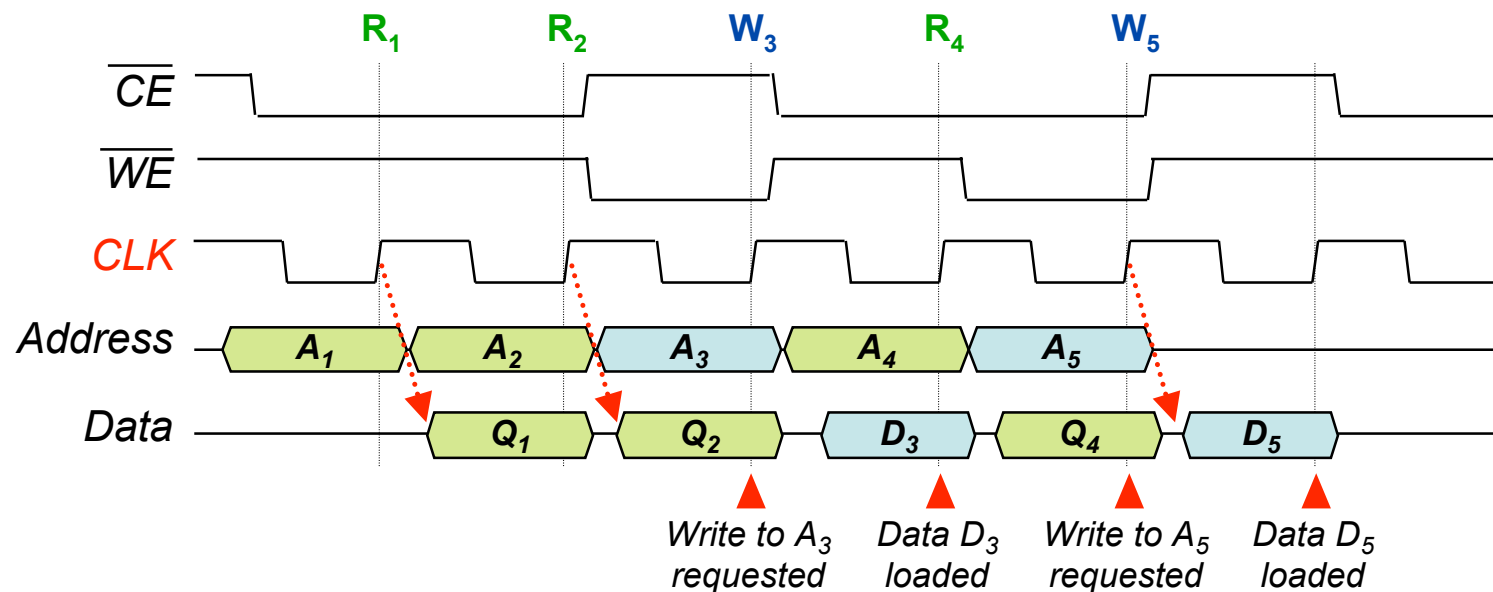
# ZBT Eliminates the Wait State

- The wait state occurs because:
  - On a read, data is available *after* the clock edge
  - On a write, data is set up *before* the clock edge
- ZBT (“zero bus turnaround”) memories **change the rules for writes**
  - On a write, data is set up **after** the clock edge (so that it is read on the following edge)
  - Result: no wait states, higher memory throughput



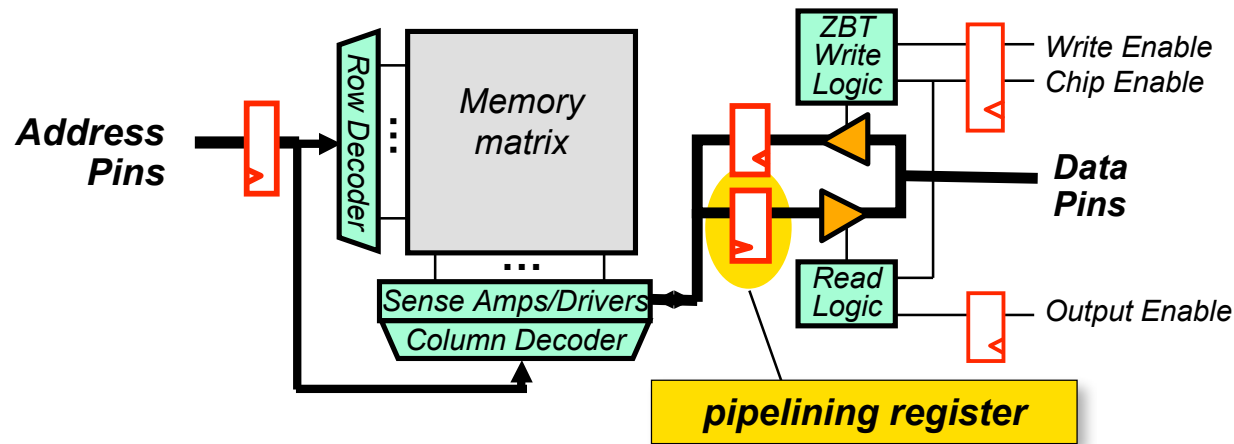
# Pipelining Allows Faster CLK

- Pipeline the memory by registering its output
  - Good: Greatly reduces CLK-Q delay, allows higher clock (more throughput)
  - Bad: Introduces an extra cycle before data is available (more latency)



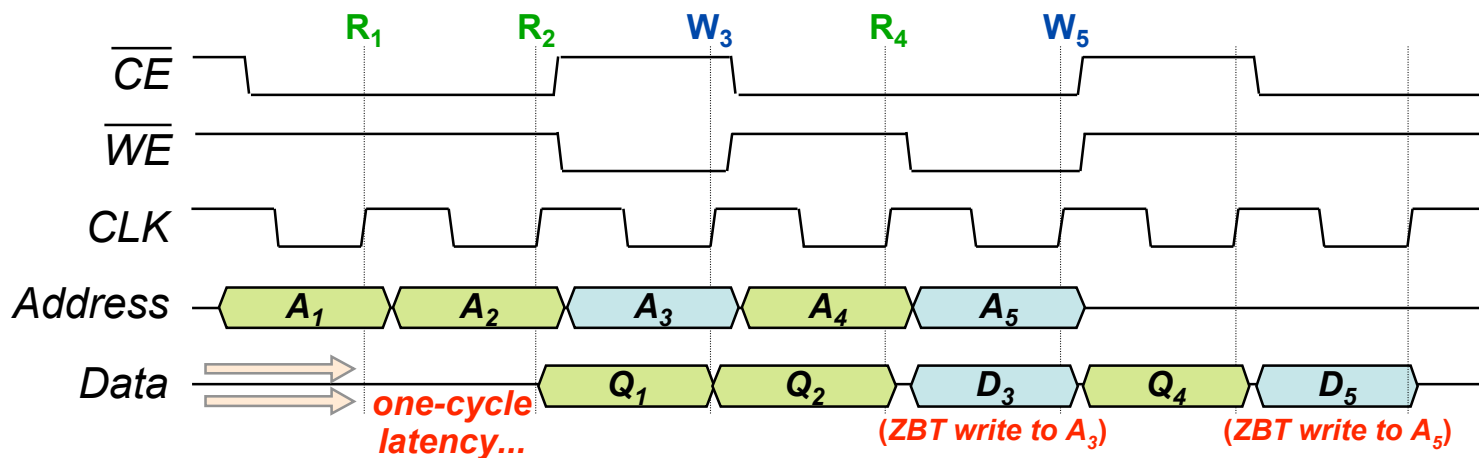As an example,  
see the *CY7C147X*  
ZBT Synchronous  
SRAM








# 4. EPROMs and DRAMs
  
## EEPROM - The Floating Gate Transistor

Electrically Erasable Programmable Read-Only Memory



Avalanche injection

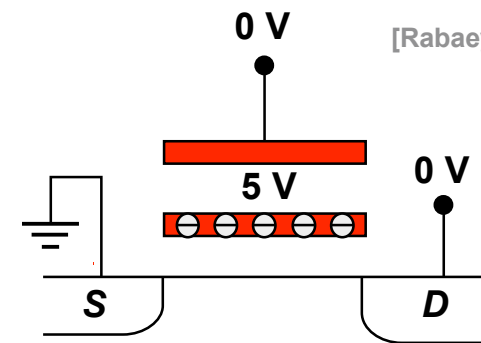

[Rabaey03]

Removing programming voltage leaves charge trapped


**This is a non-volatile memory (retains state when supply turned off)**

Usage: Just like SRAM, but **writes are much slower** than reads  
( write sequence is controlled by an FSM internal to chip )



**Common application: configuration data (serial EEPROM)**
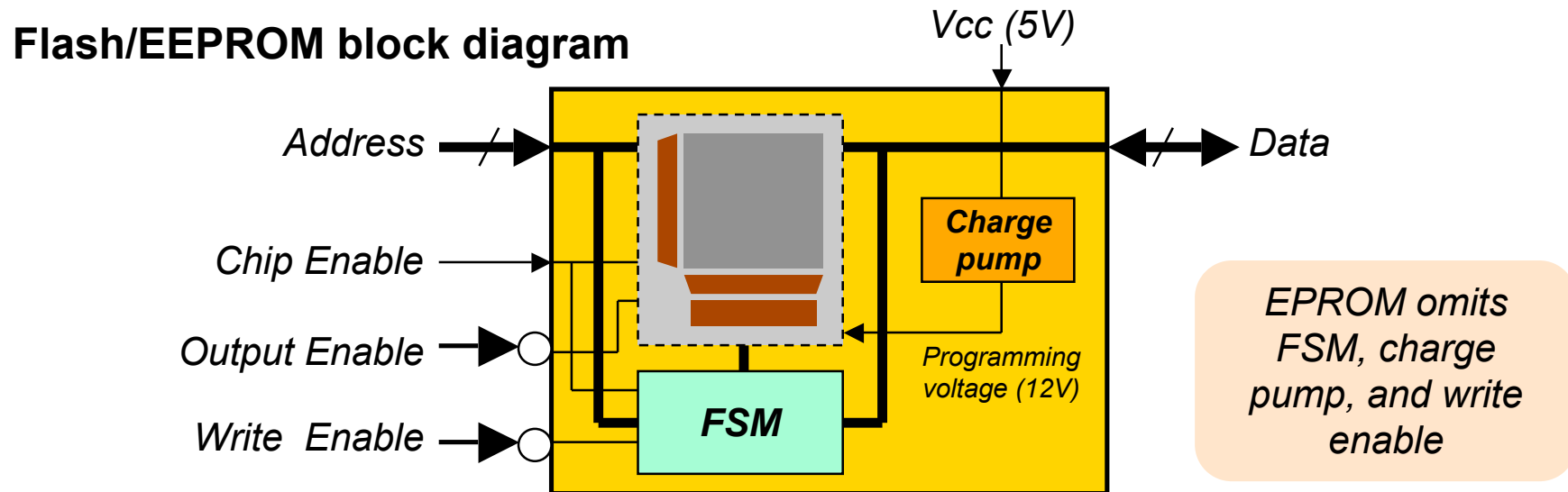
# Interacting with Flash and (E)EPROM

- Reading from flash or (E)EPROM is the same as reading from SRAM
- $V_{pp}$ : input for programming voltage (12V)
  - EPROM:  $V_{pp}$  is supplied by programming machine
  - Modern flash/EEPROM devices generate 12V using an on-chip charge pump
- EPROM lacks a write enable
  - Not in-system programmable (must use a special programming machine)
- For flash and EEPROM, write sequence is controlled by an internal FSM
  - Writes to device are used to send signals to the FSM
  - Although the same signals are used, one can't write to flash/EEPROM in the same manner as SRAM




# Dynamic RAM (DRAM) Cell

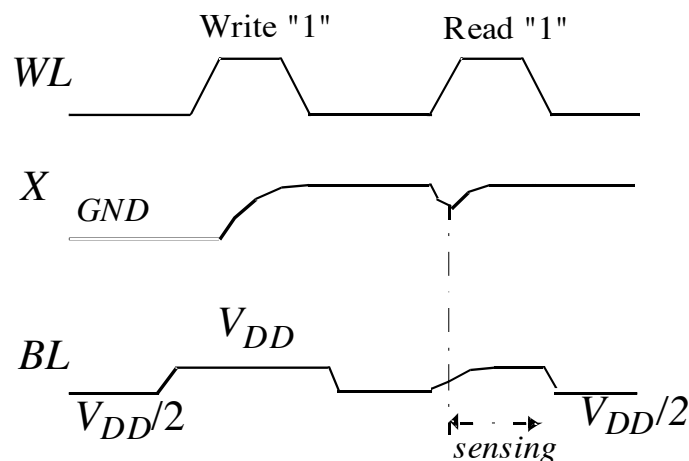 

[Rabaey03]

 **DRAM uses Special Capacitor Structures**




**To Write:** set Bit Line (BL) to 0 or  $V_{DD}$  & enable Word Line (WL) (i.e., set to  $V_{DD}$ )

**To Read:** set Bit Line (BL) to  $V_{DD}/2$  & enable Word Line (i.e., set it to  $V_{DD}$ )

- **DRAM relies on charge stored in a capacitor to hold state**
- Found in all high density memories (one bit/transistor)
- Must be “refreshed” or state will be lost – high overhead



# Asynchronous DRAM Operation

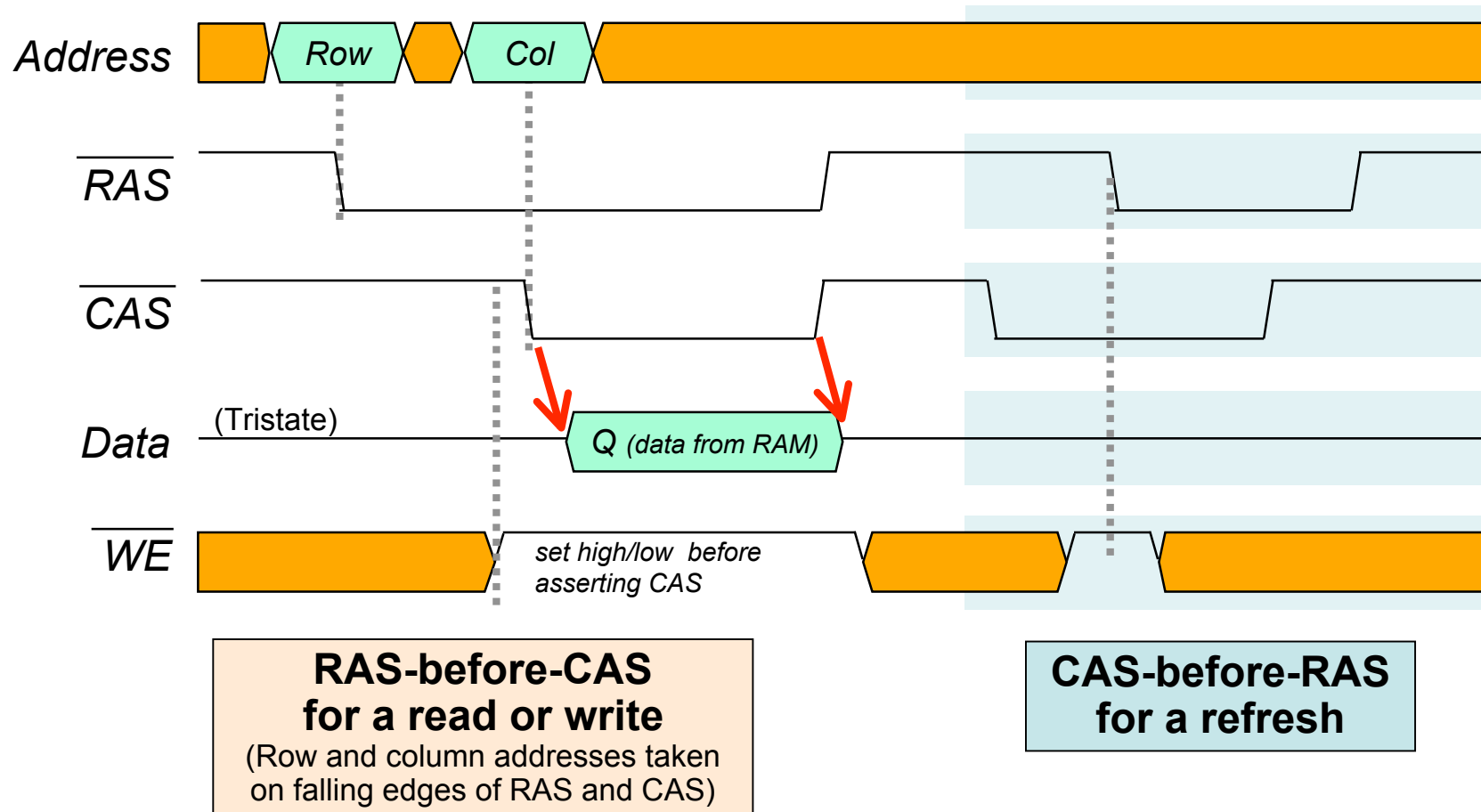

- **Clever manipulation of RAS and CAS after reads/writes provide more efficient modes: early-write, read-write, hidden-refresh, etc.**  
(See datasheets for details)
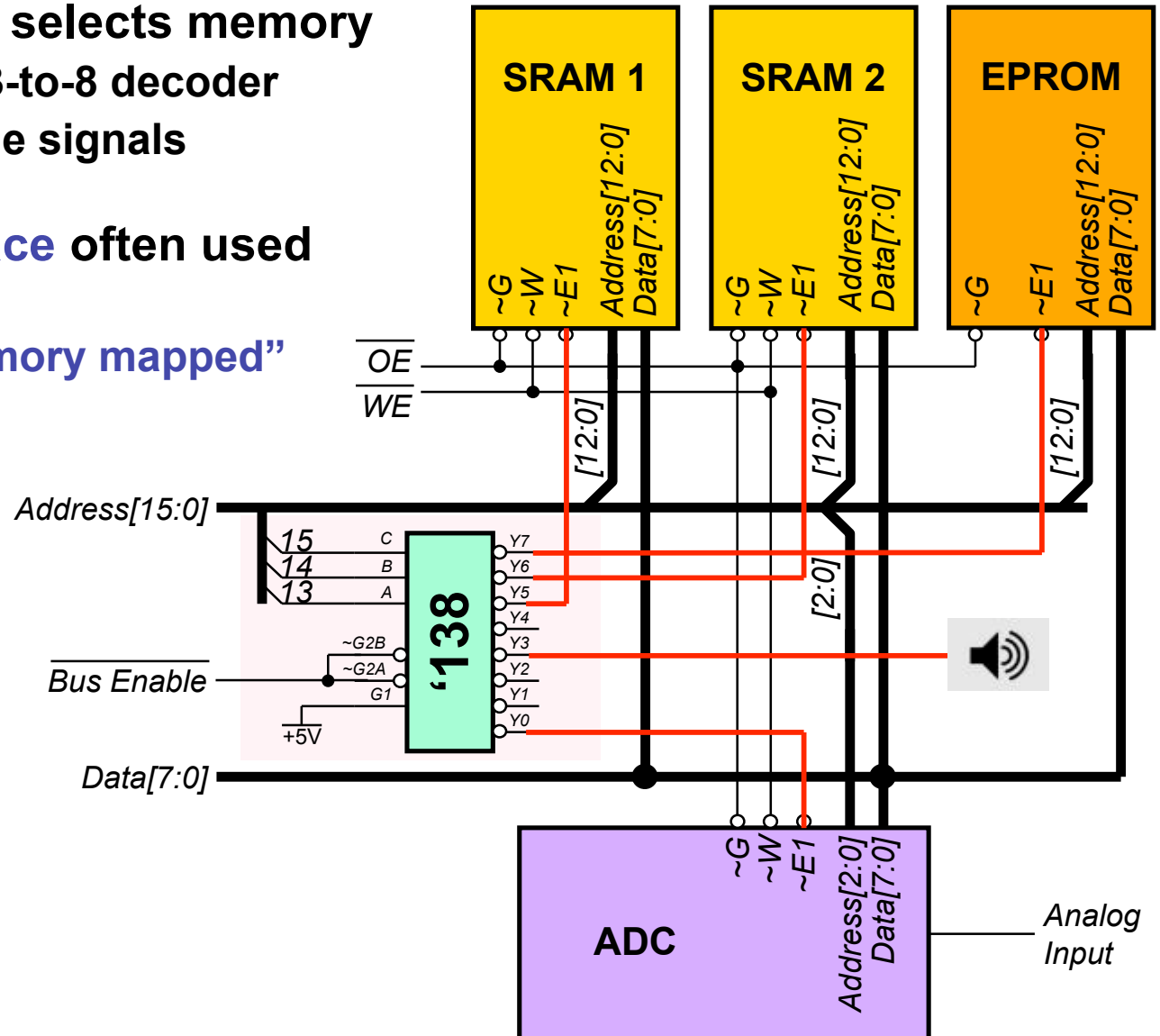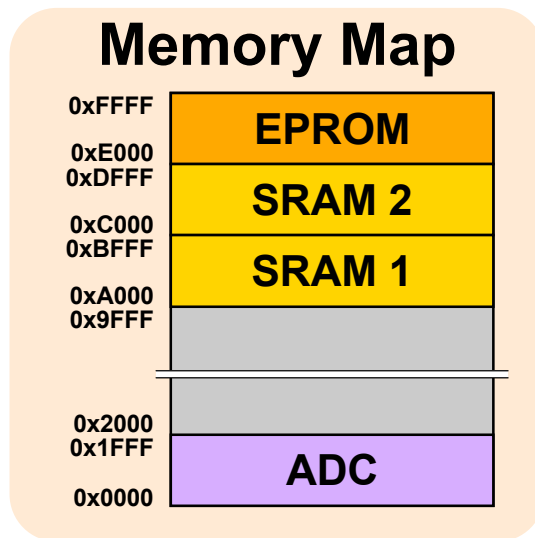
# 5. Addressing with Memory Maps

- Address decoder selects memory
  - Example: '138 3-to-8 decoder
  - Produces enable signals
- SRAM-like interface often used for peripherals
  - Known as “memory mapped” peripherals



# Memory Devices: Helpful Knowledge

- **SRAM vs. DRAM**
  - SRAM holds state as long as power supply is turned on. DRAM must be "refreshed" - results in more complicated control
  - DRAM has much higher density, but requires special capacitor technology.
  - FPGA usually implemented in a standard digital process technology and uses SRAM technology
- **Non-Volatile Memory**
  - Fast Read, but very slow write (EPROM must be removed from the system for programming!)
  - Holds state even if the power supply is turned off
- **Memory Internals**
  - Has quite a bit of analog circuits internally -- pay particular attention to noise and PCB board integration
- **Device details**
  - Don't worry about them, wait until 6.012 or 6.374

# You Should Understand Why...

- control signals such as *Write Enable* should be registered
- a multi-cycle read/write is safer from a timing perspective than the single cycle read/write approach
- it is a bad idea to enable two tri-states driving the bus at the same time
- an SRAM does not need to be “refreshed” while a DRAM requires refresh
- an EPROM/EEPROM/FLASH cell can hold its state even if the power supply is turned off
- a synchronous memory can result in higher throughput

# Summary

- **SRAMs:**

- Use synchronous FSM for interfacing
- Faster than DRAM, no refresh required

- **Data bus:**

- Tri-state (Z) used when not driving bus
- Multiple devices can share one bus

- **EEPROM:**

- Useful for config. data, long-term storage

- **Memory-Mapping:**

- Interact with peripheral as if it were an SRAM

