

Jan. 1, 2014

COMPUTER ENGINEERING DEPARTMENT

COE 405

DESIGN & MODELING OF DIGITAL SYSTEMS

Final Exam

First Semester (131)

Time: 7:00-10:00 PM

OPEN BOOK EXAM

Student Name : _KEY_____


Student ID. : _____

Question	Max Points	Score
Q1	20	
Q2	14	
Q3	13	
Q4	13	
Q5	40	
Total	100	


Dr. Aiman El-Maleh

(Q1) Determine possible circuits that will be synthesized by each of the following modules:

- (i) module FinalQ1_1 (output reg Dout1, Dout2, input A, B, C, D, sel, clk);
 always @ (posedge clk) begin
 Dout1 <= A & B; Dout2 <= Dout1 ^ C;
 if (sel) Dout1 <= Dout2 | D;
end
endmodule

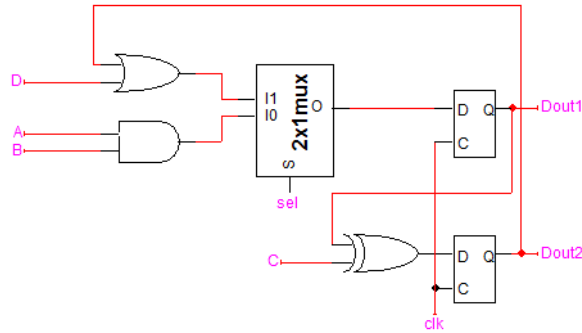

 - (ii) module FinalQ1_2 (output reg [3:0] DOUT, input DIN, clock, reset);
 always @ (posedge clock, posedge reset) begin
 if (reset) DOUT <= 0;
 else begin
 DOUT[0]<=DIN;
 DOUT[1]<=DOUT[0];
 DOUT[2]<=DOUT[1];
 DOUT[3]<=DOUT[2];
 end
end
endmodule




(iii) module FinalQ1_3 (output reg E, input A, B, C, D);

```

always @(A,B, C, D) begin
    case ({A,B})
        2'b10: E = C & D;
        2'b01: E = C | D;
    endcase
end
endmodule

```

 


(iv) module FinalQ1_4 #(parameter n=3)(output reg C, D, output E, input [n-1:0] A, B);

```

integer k;
assign E = ~(C | D);
always @ (A, B) begin
    C = 0; D = 0;
    for (k=n-1; k>=0; k=k-1) begin
        C = C | A[k] & ~B[k] & ~D;
        D = D | ~A[k] & B[k] & ~C;
    end
end
endmodule


```

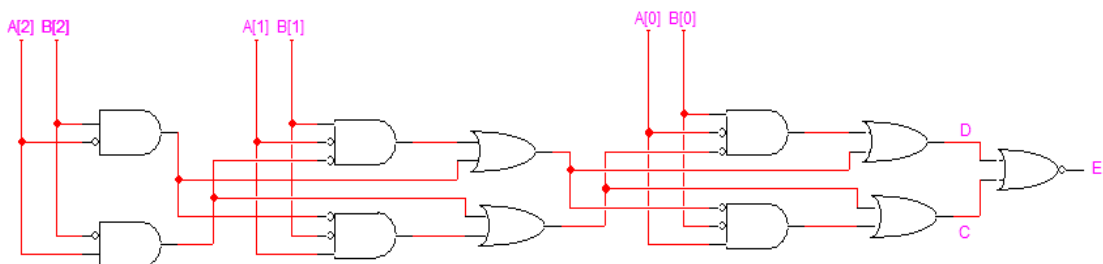

```

(v) module FinalQ1_5 #(parameter n=4) (output reg [n-1:0] R1, R2, R3, input CLK,
RST, R1in, R2in, R3in, R1out, R2out, R3out, Dout, input [n-1:0] Data);
  wire [n-1:0] Cbus;
  always @ (posedge CLK, posedge RST) begin
    if (RST) begin R1 <= 0; R2 <= 0; R3 <= 0; end
    else begin
      if (R1in) R1 <= Cbus;
      if (R2in) R2 <= Cbus;
      if (R3in) R3 <= Cbus;
    end
  end
  end
  assign Cbus = R1out? R1:{n{1'bz}};
  assign Cbus = R2out? R2:{n{1'bz}};
  assign Cbus = R3out? R3:{n{1'bz}};
  assign Cbus = Dout? Data:{n{1'bz}};
endmodule


```

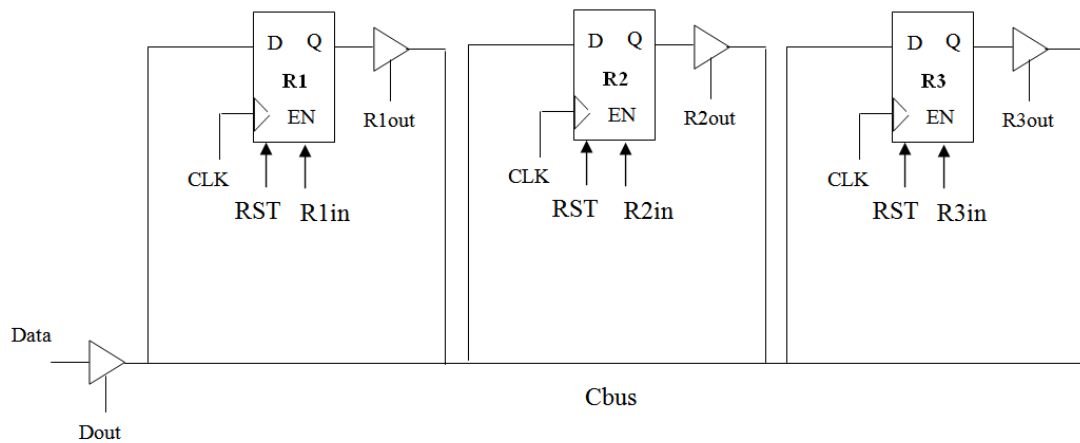

(Q2) It is required to design a circuit to compute the equation $Y=(A+B)-(C+D)$ using only a single adder. Assume that the 4-bit inputs will hold their values until the end of the operation. Also, assume that the inputs will be ready when a **Start** input is asserted. Assume that a **Done** signal will be set when the result is ready and the result will remain held until the next Start operation.


- (i) Show a schedule of the operations with minimum latency (i.e., clock cycles) satisfying the area constraints.
- (ii) Show the DataPath design of your circuit indicating all the control signals and the adder size.
- (iii) Show the ASMD diagram of your control unit.

(i) Schedule :

 


(ii)

Data Path

 


(iii) ASMD Chart:

 


[13 Points]

 (Q3) It is required to design a **Vending Machine Controller**. The machine takes one Riyal only. For each one Riyal inserted, the input signal **Ri** is asserted. The machine can dispense: Water: 2 Riyals (input **W**), Cola: 2 Riyals (input **C**), Juice: 3 Riyals (input **J**). A product is dispensed in one clock cycle after an input selection. The machine has a money return button (input **R**). When this button is pressed, all the inserted money is returned. It is assumed that only one input may be active at a time. If more than 3 Riyals are inserted, the extra money is automatically returned. If 3 Riyals are inserted and the user selects Water or Cola, the requested product is dispensed along with the return of one Riyal. Outputs are as follows: **MRo**: Money Return Out (all inserted money in the machine), **Wo**: Water Out, **Co**: Cola Out, **Jo**: Juice Out, **Ro**: One Riyal Out. Show a state diagram for modeling the Vending Machine Controller.



Note that all unspecified transitions are assumed to keep the state as is.

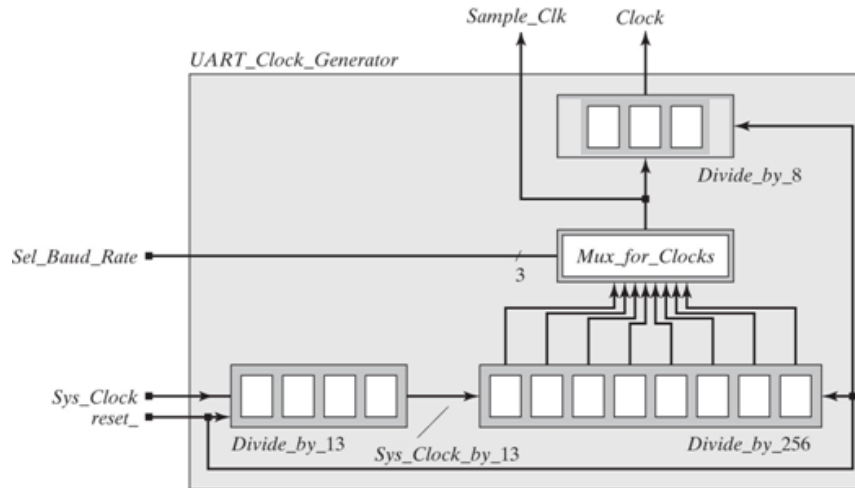(Q4) The functional unit UART_Clock_Generator given below can be used to generate a set of baud rate signal pairs for use in UART.



The table below shows the clock frequency pairs that are generated if Sys_Clock is 8 MHZ.

Sel_Baud_Rate	Sample_Clk (HZ)	Clock (HZ)
000	307,692	38,462
001	153,846	19,231
010	76,923	9,615
011	38,463	4,808
100	19,231	2,404
101	9,615	1,202
110	4,808	601
111	2,404	301

Write a synthesizable Verilog model for the UART_Clock_Generator. The signal **reset_** is an asynchronous active low reset.

```
module UART_Clock_Generator (output Clock, Sample_Clk, input [2: 0] Sel_Baud_Rate,
input Sys_Clock, reset_);
```

```
reg [3: 0] temp;
reg [7: 0] temp_by_256;
reg [2: 0] Divide_by_8;
```

```
assign Sys_Clock_by_13 = (temp == 4'b1100);
assign Clock = (Divide_by_8 == 3'b111);
```



```
always @(posedge Sys_Clock, negedge reset_)  
    if (reset_ == 0) temp <= 0;  
    else if (temp == 4'b1100) temp <= 0;  
    else temp <= temp + 1;
```

```
always @(posedge Sys_Clock_by_13, negedge reset_)  
    if (reset_ == 0) temp_by_256 <= 0;  
    else temp_by_256 <= temp_by_256 + 1;
```

```
always @(posedge Sample_Clk, negedge reset_)  
    if (reset_ == 0) Divide_by_8 <= 0;  
    else Divide_by_8 <= Divide_by_8 + 1;
```

```
assign Sample_Clk = temp_by_256[Sel_Baud_Rate] ; // for the MUX
```

```
endmodule
```

[40 Points]

(Q5) Bubble Sort is a well known sorting algorithm. The psuedo code for the sorting algorithm is given below:

```

for i=2 to N
  for j=N downto i
    if [A[j-1] > A[j] then
      begin
        Temp = A[j-1];
        A[j-1] = A[j];
        A[j] = Temp;
      end
    end
  end
end

```

It is required to write a synthesizable Verilog model for implementing the Bubble Sort algorithm. The ASMD chart and block diagram of a machine that executes the Bubble Sort algorithm is given below.

The machine is parametrizable with the number of words to be sorted as **N** and the word size as **word_size**. It is assumed that once the user sets the **Load** signal to 1, a set of **N** words will be sent through **Data_in** input serially in the next **N** clock cycles and loaded into an internal memory. Then when the signal **Sort** is asserted, the algorithm starts sorting. Once sorting is finished and the user asserts **Send** signal, the sorted data will be sent serially through **Data_out** in the next **N** clock cycles.

The bubble sort module is given below:

```

module Bubble_Sort # ( parameter N = 8, word_size = 4)(

  output [word_size -1: 0] Data_out,
  output Ready, Busy, Waiting,
  input [word_size -1: 0] Data_in,
  input Load, Sort, Send, clk, rst);


  Controller M0 (Ready, Busy, Waiting, ld, set_i, incr_i, set_j, decr_j, clr_k, incr_k,
  swap, snd, Load, Sort, Send, gt, i_lte_N, j_gte_i, done, clk, rst);

  Datapath M1 (Data_out, gt, i_lte_N, j_gte_i, done, Data_in,
  ld, set_i, incr_i, set_j, decr_j, clr_k, incr_k, swap, snd, clk);

endmodule

```

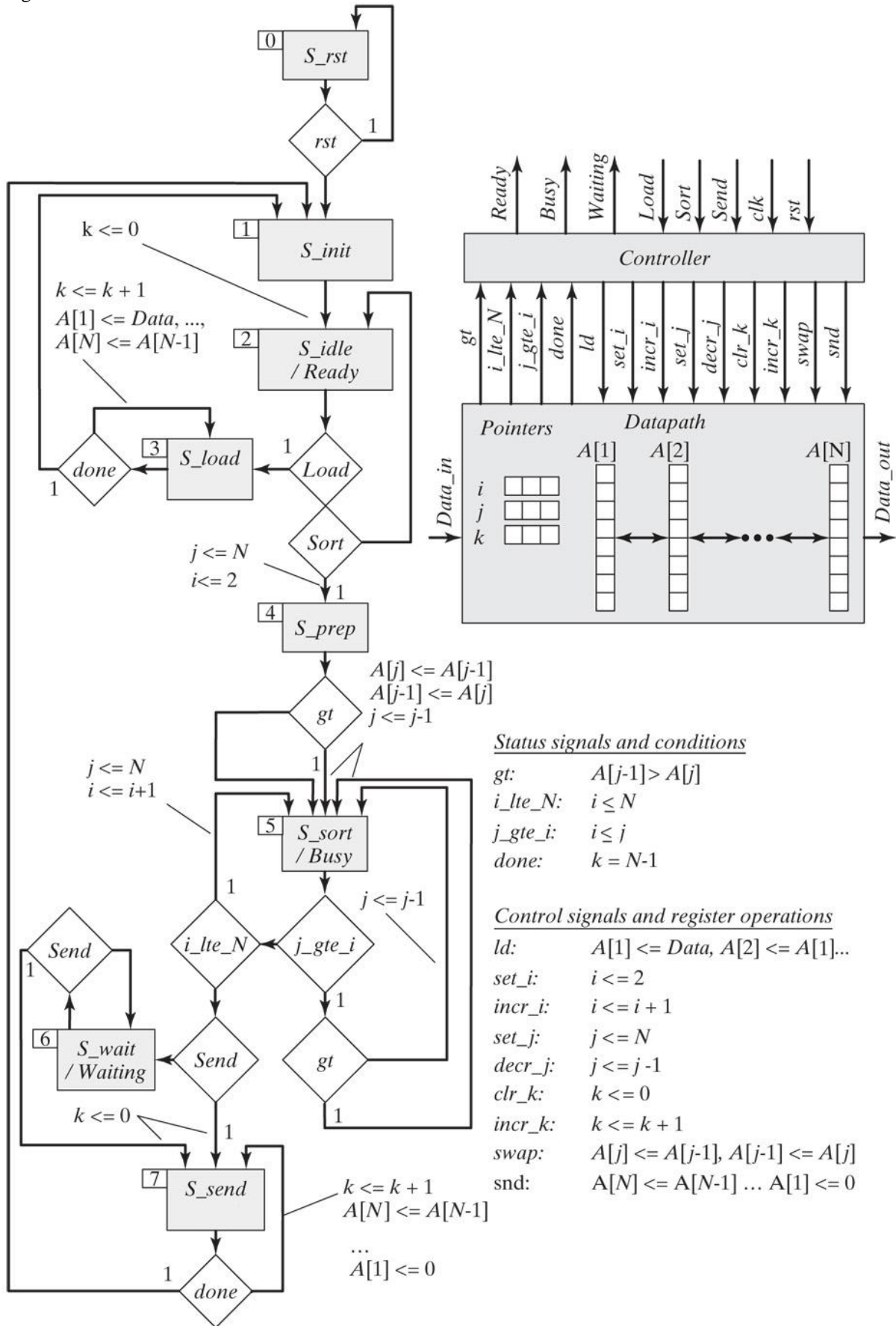- (i) Write a parametrizable Verilog model **BSDatapath** to model the datapath of the Bubble_Sort module. The parameters are the number of words to be sorted **N** and the word size **word_size**.
- (ii) Write a Verilog model **BSController** to model the control unit of the Bubble_Sort module.
- (iii) Write a Verilog **test bench** for the Bubble_Sort module to sort 8 words of test data sent serially as 1 followed by 2, 3, 4, 5, 6, 7 and 8. Assume a CLK of 10 ns period with 50% duty cycle. Your test bench should generate the CLK.



(i) DataPath Unit:

```

module BSDatath # (parameter N = 8, word_size = 4) (
output [word_size -1: 0] Data_out,
output gt, i_lte_N, j_gte_i, done,
input [word_size -1: 0] Data_in,
input ld, set_i, incr_i, set_j, decr_j, clr_k, incr_k, swap, snd, clk);

reg [word_size -1: 0] A [N: 1]; // Array of words
reg [log2(N): 0] i, j;
reg [log2(N)-1: 0] k;
integer ptr;

assign Data_out = A[N];
assign done = (k == N-1);
assign gt = (A[j-1] > A[j]); // compares words
assign i_lte_N = (i <= N);
assign j_gte_i = (i <= j);

always @ (posedge clk) // Datath and pointers
begin
if (ld) begin A[1] <= Data_in; for (ptr = 1; ptr < N; ptr = ptr + 1) A[ptr+1] <= A[ptr]; end
if (swap) begin A[j] <= A[j-1]; A[j-1] <= A[j]; end
if (decr_j) j <= j-1;
if (incr_i) i <= i+1;
if (set_j) j <= N;
if (set_i) i <= 2;
if (clr_k) k <= 0;
if (incr_k) k <= k + 1;
if (snd) begin A[1] <= 0; for (ptr = 1; ptr < N; ptr = ptr + 1) A[ptr+1] <= A[ptr]; end
end

function integer log2 (input integer n);
integer i;
begin
log2 = 1;
for (i=0; 2**i<n; i=i+1)
log2 = i+1;
end
endfunction

endmodule

```

(ii) Control Unit:

```

module BSController (
output Ready, Busy, Waiting,
output reg ld, set_i, incr_i, set_j, decr_j, clr_k, incr_k, swap, snd,
input Load, Sort, Send, gt, i_lte_N, j_gte_i, done, clk, rst);

```

```
parameter S_rst = 0, S_init = 1, S_idle = 2, S_load = 3, S_prep = 4;
parameter S_sort = 5, S_wait = 6, S_send = 7;
reg [2: 0] state, next_state;
```

```
assign Ready = (state == S_idle);
assign Busy = (state == S_sort);
assign Waiting = (state == S_wait);
```

```
always @ (posedge clk) if (rst) state <= S_rst; else state <= next_state;
```

```
always @ (state, Load, Sort, Send, gt, i_lte_N, j_gte_i, done ) begin
    next_state = S_rst;
    ld = 0;
    set_i = 0; incr_i = 0;
    set_j = 0; decr_j = 0;
    clr_k = 0; incr_k = 0;
    swap = 0; snd = 0;
    case (state)
        S_rst: next_state = S_init;
        S_init: begin next_state = S_idle; clr_k = 1; end
        S_idle:    if (Load) next_state = S_load;
                  else if (Sort) begin next_state = S_prep; set_j = 1; set_i = 1; end
                  else next_state = S_idle;
        S_load:    if (done) next_state = S_init;
                  else begin next_state = S_load; incr_k = 1; ld = 1; end
        S_prep:    begin next_state = S_sort; if (gt) swap = 1; decr_j = 1; end
        S_sort:    if (j_gte_i) begin next_state = S_sort; decr_j = 1; if (gt) swap = 1; end
                  else if (i_lte_N) begin next_state = S_sort; set_j = 1; incr_i = 1; end
                  else if (Send) begin next_state = S_send; clr_k = 1; end
                  else next_state = S_wait;
        S_wait:    if (Send) begin next_state = S_send; clr_k = 1; end
                  else next_state = S_wait;
        S_send:    if (done) next_state = S_init;
                  else begin next_state = S_send; snd = 1; incr_k = 1; end

        default: next_state = S_rst;
    endcase
end
endmodule
```

(iii) Test Bench:

```
module t_Bubble_Sort ();
parameter word_size = 4;
wire [word_size -1: 0] Data_out;
wire Ready, Busy, Waiting;
reg Load, Sort, Send, clk, rst;
reg [word_size -1: 0] Data_in;
wire [word_size -1: 0] A1, A2, A3, A4, A5, A6, A7, A8;
```

```

assign A1 = M0.M1.A[1];
assign A2 = M0.M1.A[2];
assign A3 = M0.M1.A[3];
assign A4 = M0.M1.A[4];
assign A5 = M0.M1.A[5];
assign A6 = M0.M1.A[6];
assign A7 = M0.M1.A[7];
assign A8 = M0.M1.A[8];
Bubble_Sort M0 (Data_out, Ready, Busy, Waiting, Data_in, Load, Sort, Send, clk,
rst);

```

```

initial #700 $finish;
initial begin clk = 0; forever #5 clk = ~clk; end
initial fork
rst = 1; Load = 0; Sort = 0; Send = 0;
#20 rst = 0;
Data_in = 8'h0;
#55 Data_in = 8'h1;
#65 Data_in = 8'h2;
#75 Data_in = 8'h3;
#85 Data_in = 8'h4;
#95 Data_in = 8'h5;
#105 Data_in = 8'h6;
#115 Data_in = 8'h7;
#125 Data_in = 8'h8;
#40 Load = 1;
#50 Load = 0;
#150 Sort = 1;
#160 Sort = 0;
#550 Send = 1;
#560 Send = 0;
join
endmodule

```

