

COE 405, Term 131

Design & Modeling of Digital Systems

HW# 2 Solution

Due date: Wednesday, October 9


- Q.1.** It is required to design a sequential circuit that has a single input X and a single output Y. The circuit receives an unsigned number serially through the input X from the least significant bit (LSB) to the most significant bit (MSB), and computes the equation $5 * X$ and generates the output serially from the least significant bit to the most significant bit. The circuit has an additional reset input R which resets the circuit into an initial state. The following are examples of input and output data:

Examples:

		LSB			MSB		
Input	X	0	1	1	0	0	Input=6
Output	Y	0	1	1	1	1	Output=30

		LSB			MSB		
Input	X	1	1	0	0	0	Input=3
Output	Y	1	1	1	1	0	Output=15

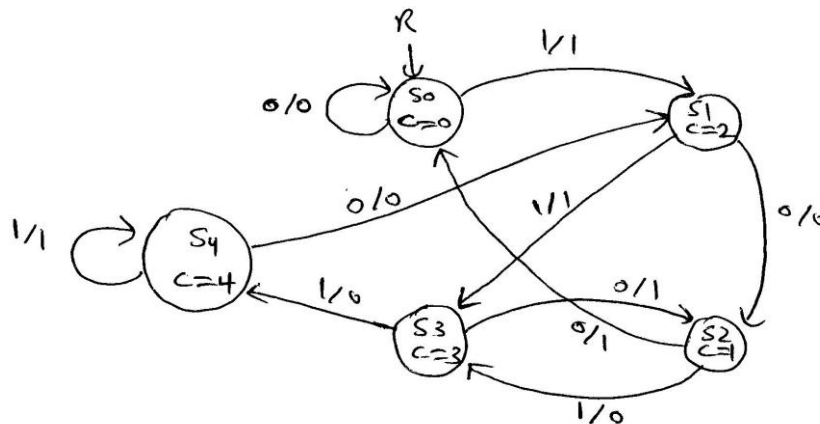- (i) Draw the state diagram of the circuit assuming a **Mealy** model.



(ii) Implement the circuit using D-FFs.

We implement the circuit using the following state assignment:

$$S_0 = 100, S_1 = 110, S_2 = 101, S_3 = 111, S_4 = 011$$

C: S:	input			N: S			output
	F_2	F_1	F_0	F_2^+	F_1^+	F_0^+	
S_0	1	0	0	0	1	0	0
	1	0	0	1	1	0	1
S_1	1	1	0	0	1	0	1
	1	1	0	1	1	1	1
S_2	1	0	1	0	1	0	0
	1	0	1	1	1	1	0
S_3	1	1	1	0	1	0	1
	1	1	1	1	0	1	0
S_4	0	1	1	0	1	1	0
	0	1	1	1	0	1	1

$F_2 F_1$	$F_0 X$	00	01	11	10
00	F_2^+	X	X	X	X
01	F_1^+	X	X	0	1
11	F_0^+	1	1	0	1
10	Y	1	1	1	1

$$F_2^+ = \bar{F}_1 + \bar{F}_0 + \bar{X}$$

$F_2 F_1$	$F_0 X$	00	01	11	10
00	F_2^+	X	X	X	X
01	F_1^+	X	X	1	1
11	F_0^+	0	1	1	0
10	Y	0	1	1	0

$$F_1^+ = \bar{F}_2 + X$$



$F_2 F_1$	$F_0 X$	00	01	11	10
00	F_2^+	X	X	X	X
01	F_1^+	X	X	1	0
11	F_0^+	1	1	1	1
10	Y	0	0	1	0

$$F_0^+ = F_2 F_1 + F_0 X$$

$F_2 F_1$	$F_0 X$	00	01	11	10
00	F_2^+	X	X	X	X
01	F_1^+	X	X	1	0
11	F_0^+	0	1	0	1
10	Y	0	1	0	1

$$\begin{aligned} Z &= \bar{F}_2 X + \bar{F}_0 X + F_2 F_0 \bar{X} \\ &= X (\bar{F}_2 + \bar{F}_0) \\ &\quad + \bar{X} (F_2 F_0) \\ &= X \oplus F_2 F_0 \end{aligned}$$

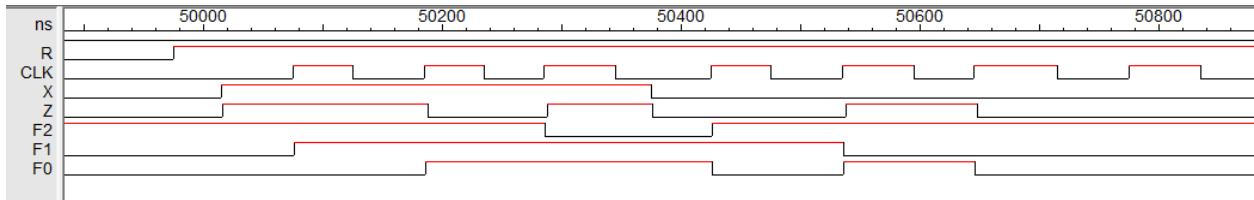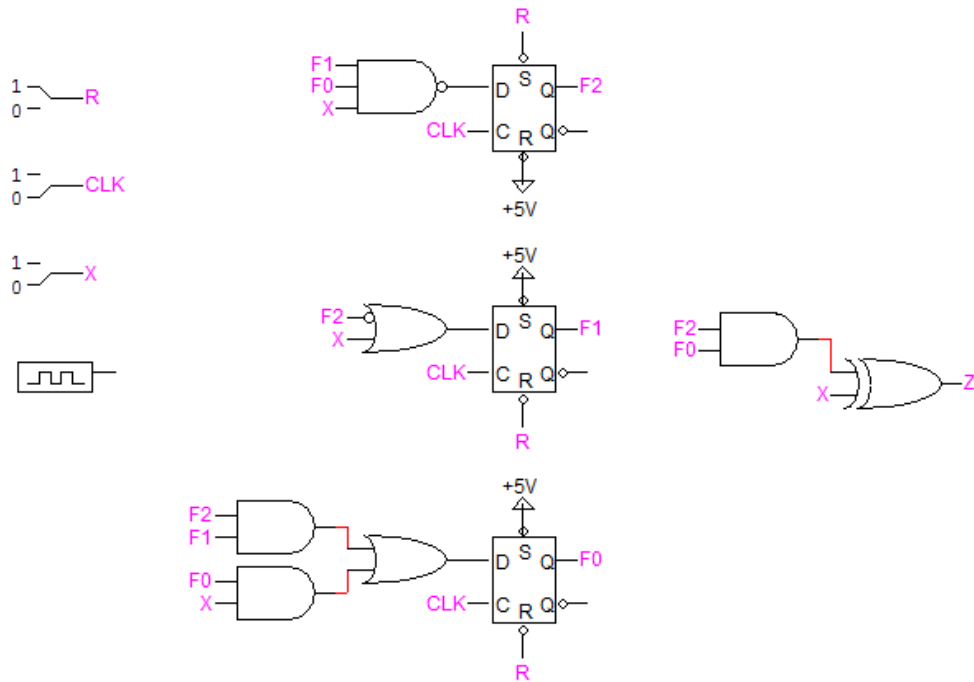(iii) Verify the correctness of your circuit by simulation.




It is clear from simulations that the circuit is working properly as for the input $X=111=7$, the output produced is $Y=110001=35$.

Q.2. Consider the given FSM that has 5 states, one input (X) and one output (Z), represented by the following state table:

Present State	Next State, Z	
	X=0	X=1
S1	S3, 1	S5, 0
S2	S3, 0	S5, 1
S3	S2, 0	S1, 1
S4	S4, 0	S5, 1
S5	S4, 1	S1, 0

(i) Determine the equivalent states.

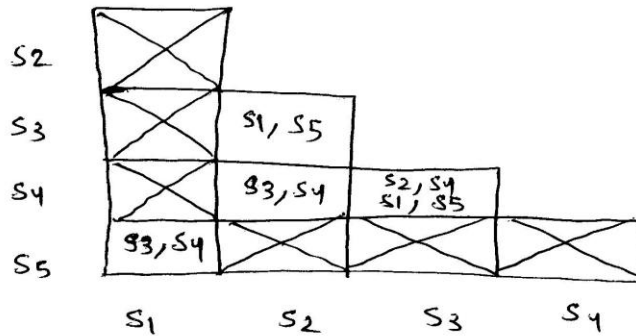

Equivalent states : (S_1, S_5) , (S_2, S_3)
 (S_2, S_4) , (S_3, S_4)
 $\Rightarrow (S_1, S_5)$, (S_2, S_3, S_4)

(ii) Reduce the state table into the minimum number of states and show the reduced state table.

Reduced State table:

Pr.S.	N.S, Z	
	X=0	X=1
S15	S234, 1	S15, 0
S234	S234, 0	S15, 1

Q.3. Consider the given FSM that has 4 states, one input (X) and one output (Z), represented by the following state table:

Present State	Next State, Z	
	X=0	X=1
S0	S0, 0	S1, 0
S1	S2, 0	S3, 0
S2	S0, 0	S1, 1
S3	S2, 0	S3, 0

- (i) Implement the FSM using the following state assignment: S0=00, S1=10, S2=01, S3=11.

$$S_0 = 00, S_1 = 10, S_2 = 01, S_3 = 11$$

P.S.	N.S., z	
	x=0	x=1
00	00, 0	10, 0
10	01, 0	11, 0
01	00, 0	10, 1
11	01, 0	11, 0

		F ₁ F ₀			
		00	01	11	10
x	0	0	0	0	0
	1	1	1	1	1

$$F_1^+ = x$$

		F ₀ F ₁			
		00	01	11	10
x	0	0	0	1	1
	1	0	0	1	1

$$F_0^+ = F_1$$

		F ₁ F ₀			
		00	01	11	10
x	0	0	0	0	0
	1	0	1	0	0

$$z = x \bar{F}_1 F_0$$

- (ii) Implement the FSM using the following state assignment: S0=11, S1=01, S2=00, S3=10.

$$S_0 = 11, S_1 = 01, S_2 = 00, S_3 = 10$$

P.S. F ₁ F ₀	N.S., Z	
	x=0	x=1
11	11, 0	01, 0
01	00, 0	10, 0
00	11, 0	01, 1
10	00, 0	10, 0

x \ F ₁ F ₀	00	01	11	10
0	1	0	1	0
1	0	1	0	1

$$F_1^+ = \overline{x \oplus F_1 \oplus F_0}$$

$$= x \oplus \overline{F_1 \oplus F_0}$$

x \ F ₁ F ₀	00	01	11	10
0	1	0	1	0
1	1	0	1	0

$$F_0^+ = \overline{F_1 \oplus F_0}$$

x \ F ₁ F ₀	00	01	11	10
0	0	0	0	0
1	1	0	0	0

$$Z = x \overline{F_1} \overline{F_0}$$

